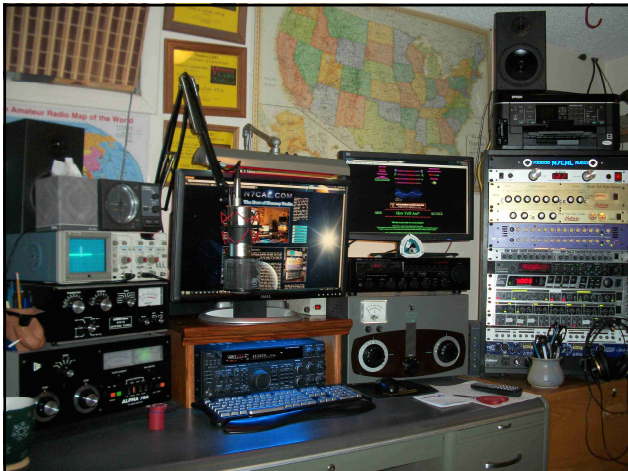


1



3




2



4





5



**LARC BASIC AMATEUR RADIO COURSE - 2019**

**CURRENT, VOLTAGE, RESISTANCE, POWER, OHM'S LAW (Chapters 2 & 3)**

Mike Cook<sup>©</sup> VE3ZMC

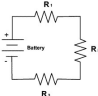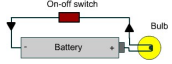7



6



**London Amateur Radio Club, 2019 Ham License Course**

Date	Chapter	Topic	Location	Instructor
Sep 07	1	Introduction and Overview	Trinity Lutheran Church	Doug Elliott, & guests
Sep 14	2	Current, Voltage, Resistance	Trinity Lutheran Church	Mike Cook
	3	Ohms Law, Power		
Sep 21	4	Inductors, Capacitance, transformers, reactance, impedance, resonance	Trinity Lutheran Church	Mike Cook
Sep 28	5	Waves, wavelength, frequency & bands	Trinity Lutheran Church	Mike Cook
	6	Propagation		
Oct 05	7	Transmission Lines	Trinity Lutheran Church	Mitch Powell
	8	Antennas		
Oct 12	*no class*	No Class - Thanksgiving Weekend	NO CLASS	
Oct 17	9	active devices, diodes, transistors, and tubes	Trinity Lutheran Church	Mark Brammeil
Oct 26	10	Power Supplies	Trinity Lutheran Church	Mark Brammeil
	11	Establishing & equipping a ham station		
Nov 02	12	Routine Operation of an amateur station	Trinity Lutheran Church	Jim Spicer Tom Pillon Dave Lambert
Nov 09	13	Modulation and Transmitters	Trinity Lutheran Church	Dave McCarter
Nov 16	14	Receivers	Trinity Lutheran Church	Dave McCarter
Nov 23	16	Safety	Trinity Lutheran Church	Mike Watts
	17	Regulations		
Nov 30	15	Radio Frequency Interference	Trinity Lutheran Church	Mike Watts
Dec 07	Exam	100 Multiple Choice Questions	Trinity Lutheran Church	Examiners

Notes:  
 - Labour Day is Monday Sept 2  
 - Thanksgiving is Monday October 14  
 - Trinity Lutheran Church is at 746 Coborne St

8

Radio is a consequence of a very fundamental property of matter  
 That property is called "Charge"  
 We think about a charge generating a "field" around it

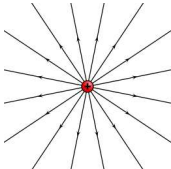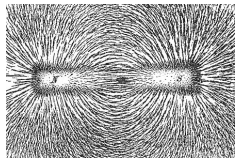
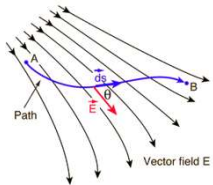
Magnets generate a "field" too

9

We don't really know what charge is.  
 But we have learned how to use it  
 We need to understand something about "Charge" and "Electricity" in order to understand how radio works.  
*Electricity is all around us, and within us....*

11

Charges create an electric field, which is a vector field

Path

Vector field E


10



12




13

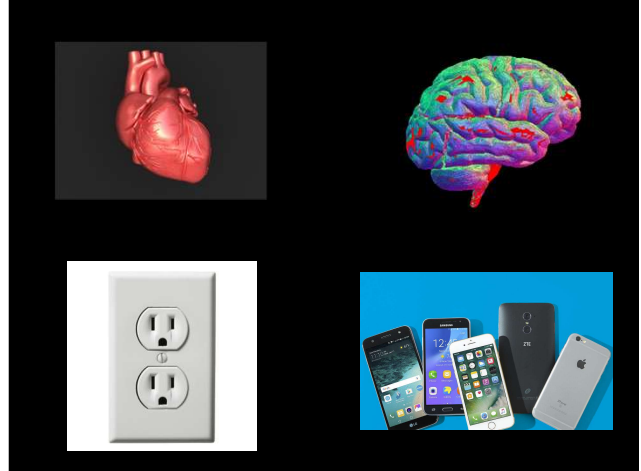

15



14

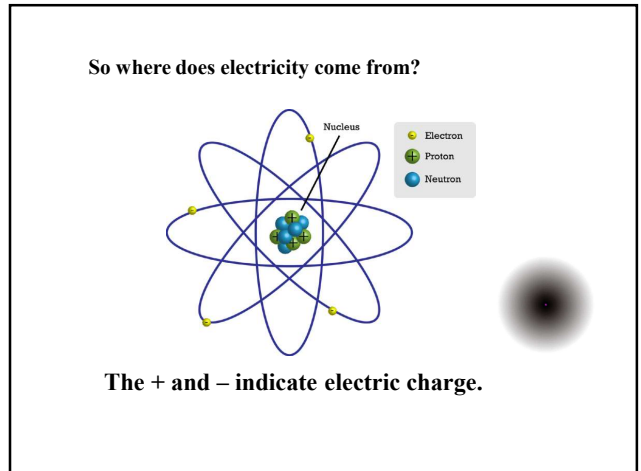


16

Charge is carried by a charge carrier which can be electrons, protons, ions or holes.


Electrons are the charge carriers in metals and are responsible for charge movement in electrical and electronic applications.

Ions are the charge carriers in a plasma and in biological systems.

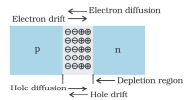Holes (and electrons) are the charge carriers in semiconductors.





17

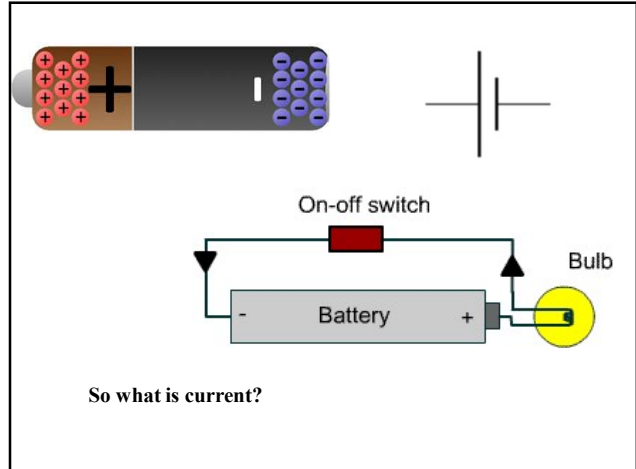

19

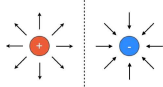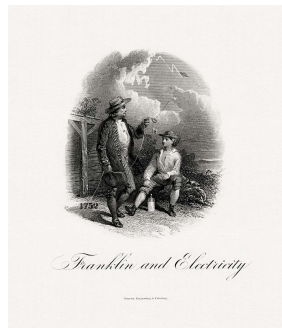
So we have two kinds of charge – positive and negative.




18

Current in a conductor must involve something moving because:

Closed circuit

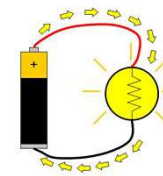


Open circuit

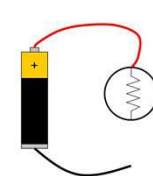


No connection, no current flow

20

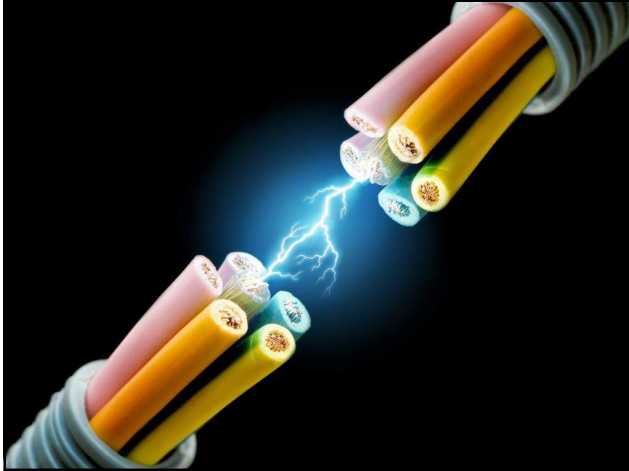


21

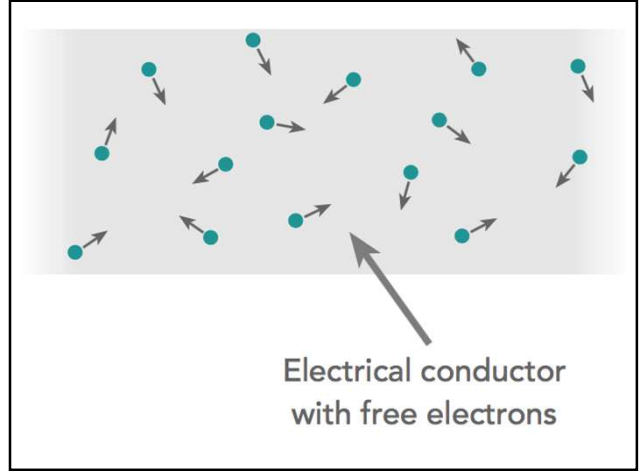


Electrical conductor  
with free electrons

23

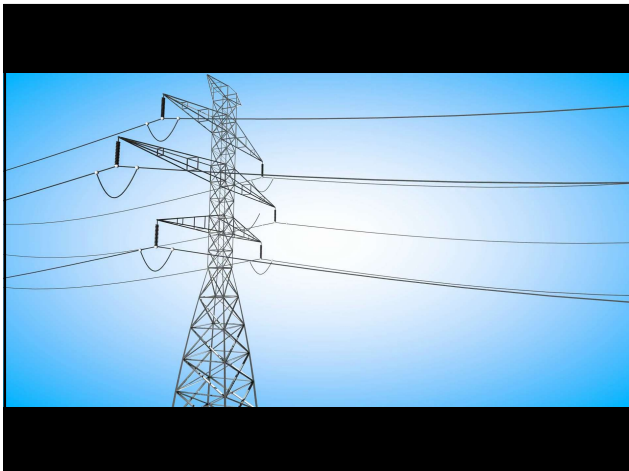


22

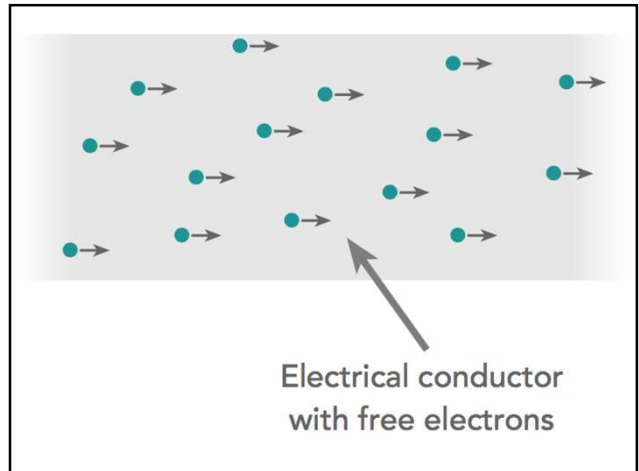


Electrical conductor  
with free electrons


24

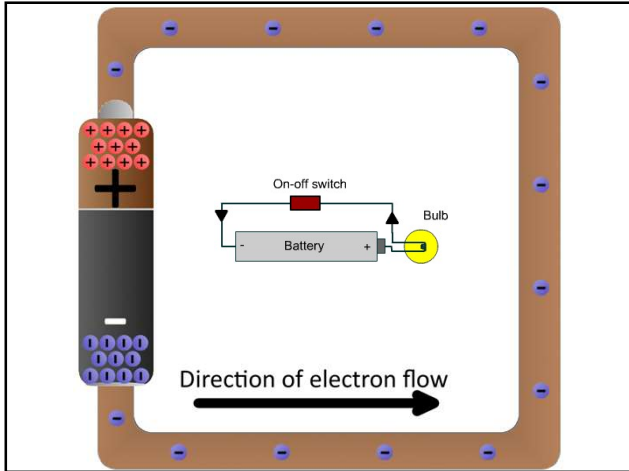


25

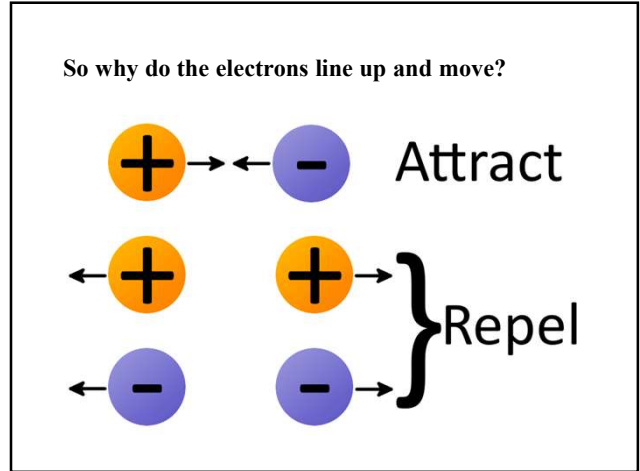


27

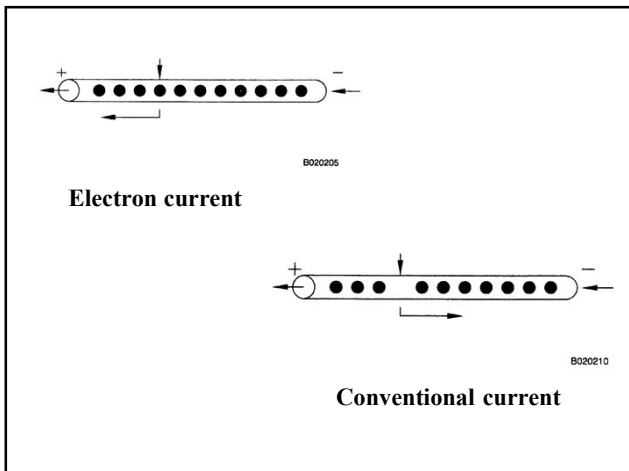


26

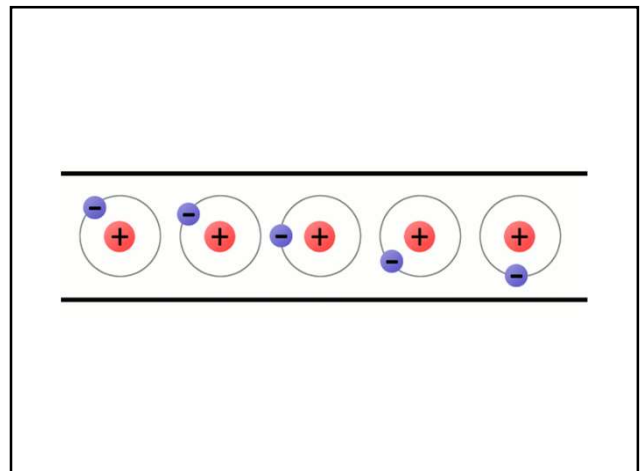


28

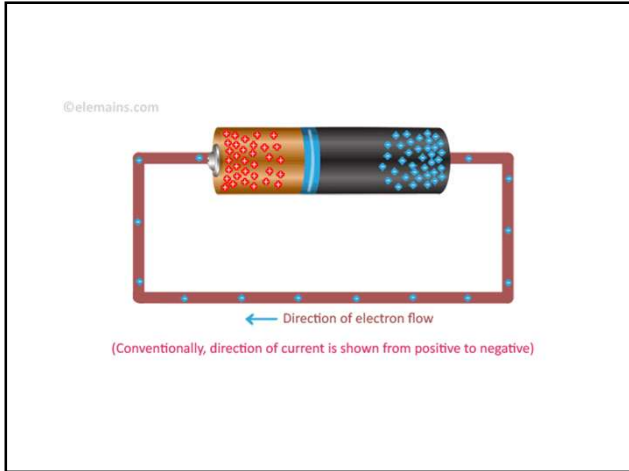

29

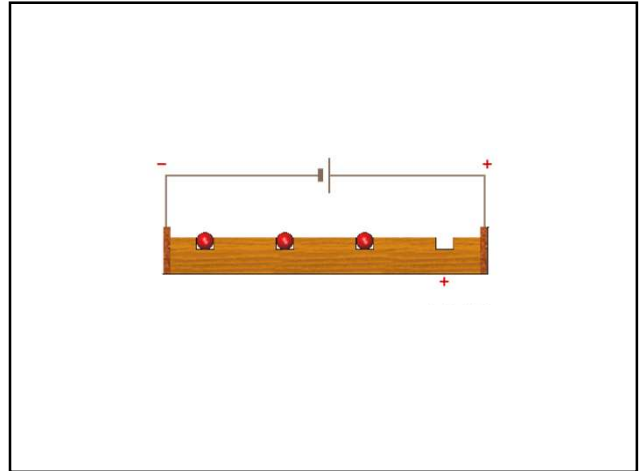


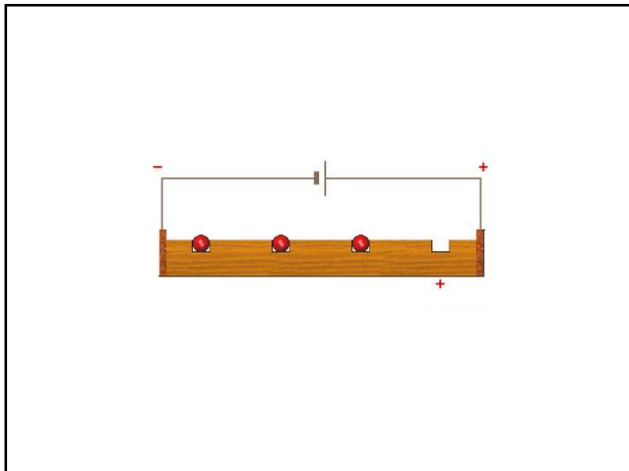

31



30
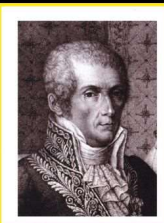
### Electrical Circuits

		
<b>ALESSANDRO VOLTA</b> (1745-1827)	<b>ANDRE MARIE AMPERE</b> (1775-1836)	<b>GEORG SIMON OHM</b> (1789-1854)

32




**So what exactly is current?**

**Current is the flow of electric charge**


**So current is really the movement (flow) of electrons along a conductor**

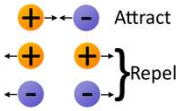**We measure current flow in Amperes (Amps) and use the symbol I (or i)**




33

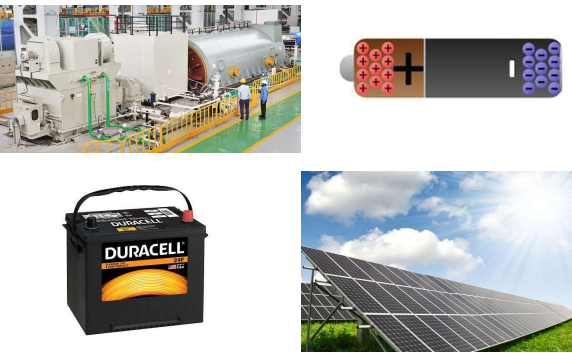**That work can be mechanical (friction or pressure), chemical, photovoltaic (light) or magnetic.**



35


**So what makes the electrons move?**

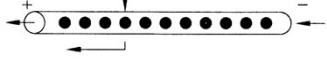

000205

**It takes work to push an extra electron in...**


**We call that work voltage and use the symbol V**



34

**Voltage is really a measure of the energy of electrons.**

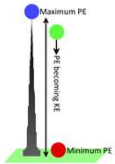**Electrons have potential energy and will flow from a point of high potential energy to a point of lower potential energy.**




**The difference in energy levels is referred to as the potential difference**

**Since it makes electrons move, it is also called the Electromotive Force (EMF).**

**E and V both mean essentially the same thing.**

36

**Why did the light bulb light?**

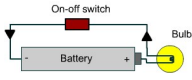


**The repulsion of that extra electron by one already there resists its movement, i.e. there is resistance**

**Resistance depends on the composition of a conductor, it's length, diameter and the temperature.**


**It is measured in Ohms ( $\Omega$ )**

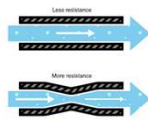**1  $\Omega$  permits 1 V to push 1 A along a conductor**




37

**Resistance to electron flow results in conversion of energy to heat and light**




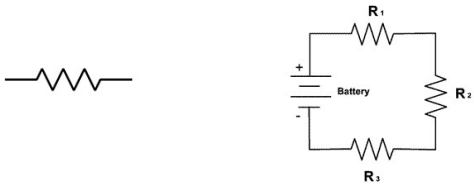**Resistance is present in every electrical circuit. We use known resistance in the design of circuits.**



39

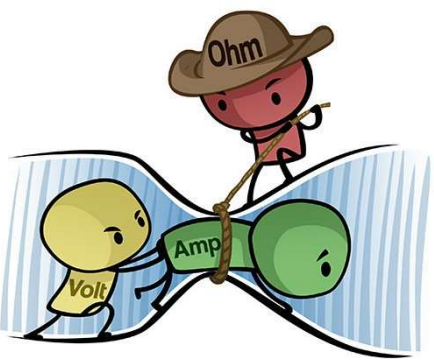
**1  $\Omega$  permits 1 V to push 1 A along a conductor**




38



40

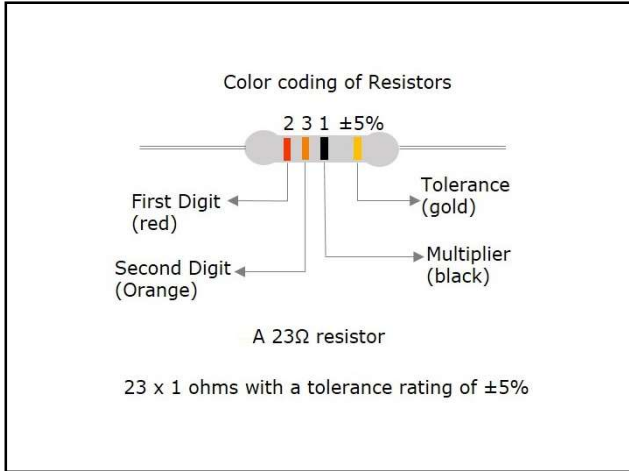

41

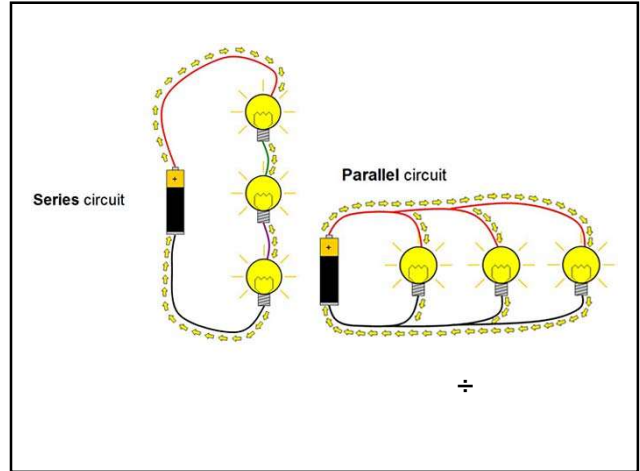


43

4 band color code resistor

Color	1 <sup>st</sup> digit	2 <sup>nd</sup> digit	Multiplier	Tolerance
Black	0	0	10 <sup>0</sup>	
Brown	1	1	10 <sup>1</sup>	1% (F)
Red	2	2	10 <sup>2</sup>	2% (G)
Orange	3	3	10 <sup>3</sup>	
Yellow	4	4	10 <sup>4</sup>	
Green	5	5	10 <sup>5</sup>	0.5% (D)
Blue	6	6	10 <sup>6</sup>	0.25% (C)
Violet	7	7	10 <sup>7</sup>	0.10% (B)
Gray	8	8	10 <sup>8</sup>	0.05%
White	9	9	10 <sup>9</sup>	
Gold			10 <sup>-1</sup>	5% (J)
Silver			10 <sup>-2</sup>	10% (K)

**Bad Booze Rots Our Young Guts But Vodka Goes Well.**


42

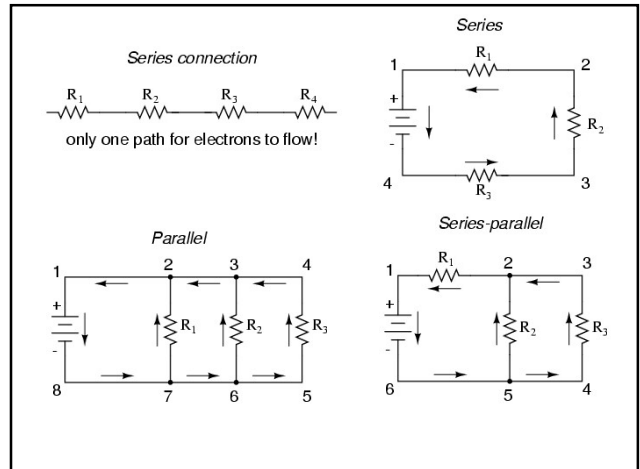


44

**Types of resistors**

**Fixed**

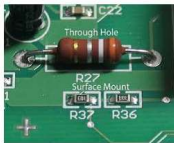

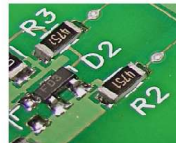Surface mount resistor when compared to the size of a normal resistor



Surface mount resistors mounted on a PCB

45



Single tube Rheostat




Double tube Rheostat

47

**Variable resistors**



Image of a Potentiometer

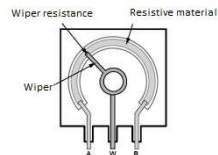


Internal structure of a Pot

46



Images showing different types of Trim Pots

48

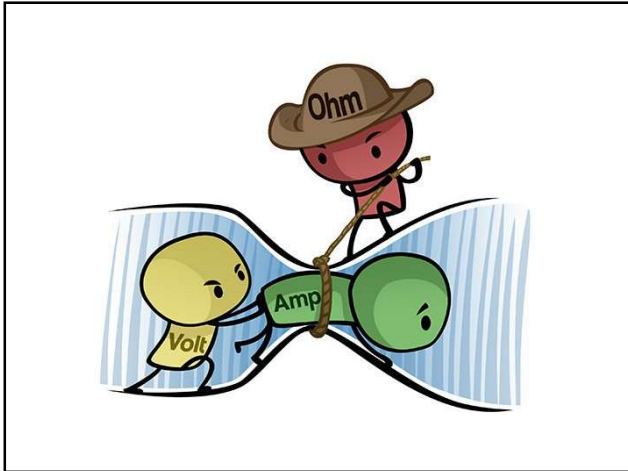

49

<b>Pressure</b> = increase	<b>Voltage</b> = increase
<b>Flow rate</b> = increase	<b>Current</b> = increase
<b>Resistance</b> = same	<b>Resistance</b> = same

$$\begin{matrix} \uparrow & \uparrow \\ E = I R \end{matrix}$$

*If the resistance to water flow stays the same and the pump pressure increases, the flow rate must also increase.*

51

**Ohm's Law** *"Ohm, Ohm on the range"*

$$E = I \times R$$

$$I = E \div R \qquad R = E \div I$$

50

<b>Pressure</b> = same	<b>Voltage</b> = same
<b>Flow rate</b> = decrease	<b>Current</b> = decrease
<b>Resistance</b> = increase	<b>Resistance</b> = increase

$$\begin{matrix} & \uparrow \\ E = I R \\ & \downarrow \end{matrix}$$

*If the pressure stays the same and the resistance increases (making it more difficult for the water to flow), then the flow rate must decrease:*

52

**Pressure** = decrease      **Voltage** = decrease  
**Flow rate** = same          **Current** = same  
**Resistance** = decrease      **Resistance** = decrease

$$E = I R$$

↓                      ↓  
*If the flow rate were to stay the same while the resistance to flow decreased, the required pressure from the pump would necessarily decrease:*

53

PREFIX	SYMBOL	MULTIPLIER	EXPONENT FORM
exa	E	1, 000, 000, 000, 000, 000, 000	10 <sup>18</sup>
peta	P	1, 000, 000, 000, 000, 000	10 <sup>15</sup>
tera	T	1, 000, 000, 000, 000	10 <sup>12</sup>
giga	G	1, 000, 000, 000	10 <sup>9</sup>
mega	M	1, 000, 000	10 <sup>6</sup>
kilo	k	1, 000	10 <sup>3</sup>
hecto	h	100	10 <sup>2</sup>
deca	da	10	10 <sup>1</sup>
Basic Unit	Basic Unit	1	10 <sup>0</sup>
deci	d	0.1	10 <sup>-1</sup>
centi	c	0.01	10 <sup>-2</sup>
milli	m	0.001	10 <sup>-3</sup>
micro	μ	0.000, 001	10 <sup>-6</sup>
nano	n	0.000, 000, 001	10 <sup>-9</sup>
pico	p	0.000, 000, 000, 001	10 <sup>-12</sup>
femto	f	0.000, 000, 000, 000, 001	10 <sup>-15</sup>
atto	a	0.000, 000, 000, 000, 000, 001	10 <sup>-18</sup>

55

**Calculations**

$i = 0.48A$   
 $= 480 \text{ mA}$

54

**Practice the calculations in the book both in Chapter 3 and in the Appendix and at IC \*NB**

B-005-1-6    A kilohm is:


1. 0.1 ohm
2. 0.001 ohm
3. 10 ohms
4. 1000 ohms

56

B-005-1-9 How many millivolts are equivalent to two volts?  
 1. 0.000002  
 2. 2 000  
 3. 2 000 000  
 4. 0.002

57

**Series and Parallel calculations**

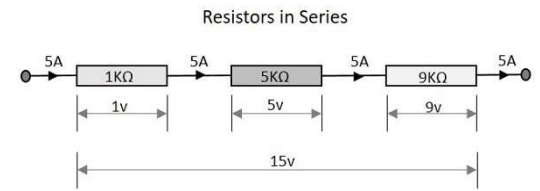


$$R_T = R_1 + R_2 + R_3 + \dots \quad \text{Eqn 3-4}$$

$$E_T = E_1 + E_2 + E_3 + \dots \quad I_T = I_1 = I_2 = I_3 \dots$$

59

B-005-1-2 If an ammeter marked in amperes is used to measure a 3000 milliampere current, what reading would it show?  
 1. 3 amperes  
 2. 0.003 ampere  
 3. 0.3 ampere  
 4. 3 000 000 amperes


58

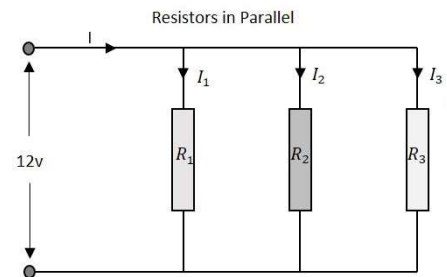

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \quad \text{Eqn 3-7}$$

$$E = E_1 = E_2 = \dots \quad I_T = I_1 + I_2 + I_3 + \dots$$

60

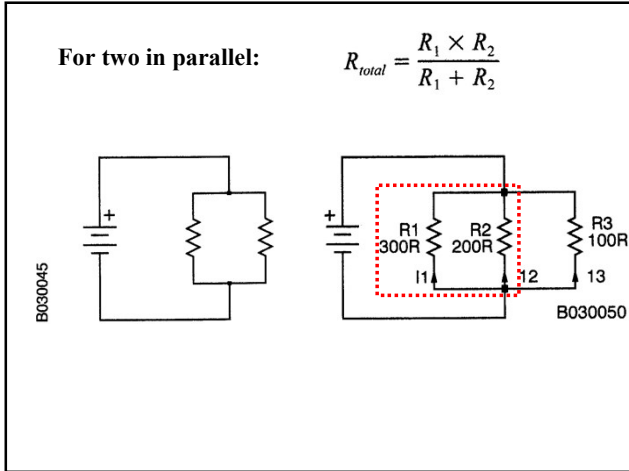

61

**Power**

**Power is the rate of doing work**

$$P = E \times I \quad \text{Eqn 3-11}$$


$$P = \frac{E^2}{R} \quad \text{Eqn 3-12}$$

$$P = I^2 \times R \quad \text{Eqn 3-13}$$

If,  $I = \frac{E}{R}$  and  $P = I E$       If,  $E = I R$  and  $P = I E$

Then,  $P = \frac{E}{R} E$  or  $P = \frac{E^2}{R}$       Then,  $P = I(I R)$  or  $P = I^2 R$

63

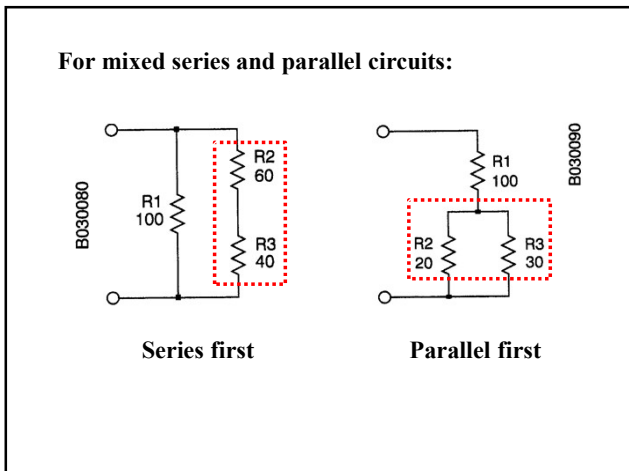

62

*Power equations*

$$P = I E \quad P = \frac{E^2}{R} \quad P = I^2 R$$

64



B-005-6-2 How many watts of electrical power are used by a 12-VDC light bulb that draws 0.2 ampere?

1. 2.4 watts
2. 60 watts
3. 24 watts
4. 6 watts

65

B-004-6-10 A resistor with a colour code of brown, black and red would have a value of:

1. 1000 ohms
2. 100 ohms
3. 10 ohms
4. 10 000 ohms

4 band color code resistor


Color	Digit	Multiplier	Tolerance
Brown	1	$10^1$	$\pm 1\%$
Black	0	$10^0$	$\pm 0.1\%$
Red	2	$10^2$	$\pm 2\%$
Orange	3	$10^3$	$\pm 3\%$
Yellow	4	$10^4$	$\pm 4\%$
Green	5	$10^5$	$\pm 0.5\%$
Blue	6	$10^6$	$\pm 0.2\%$
Violet	7	$10^7$	$\pm 0.1\%$
Purple	8	$10^8$	$\pm 0.05\%$
Gold	-	$10^{-1}$	$\pm 5\%$
Silver	-	$10^{-2}$	$\pm 10\%$

67


B-005-6-3 The DC input power of a transmitter operating at 12 volts and drawing 500 milliamps would be:

1. 20 watts
2. 6 watts
3. 500 watts
4. 12 watts


66

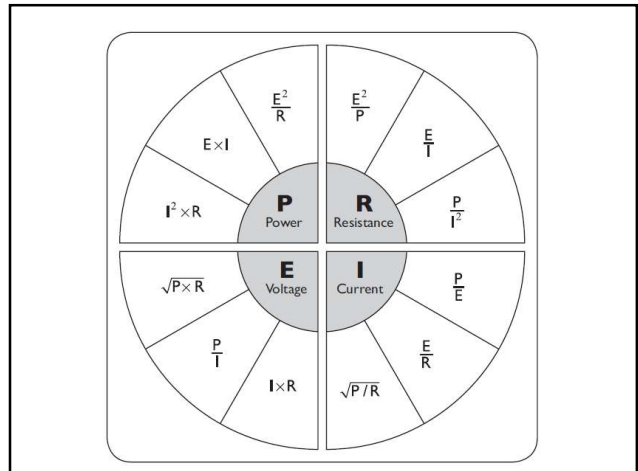


68

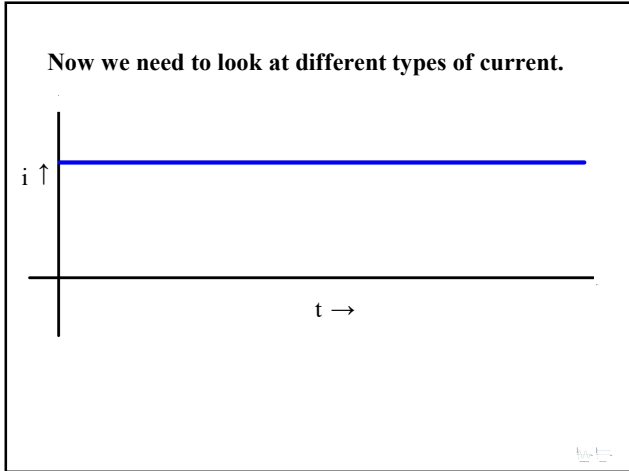


69

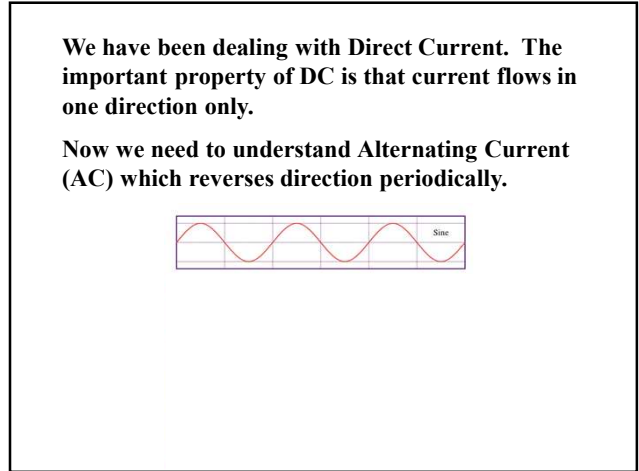


71

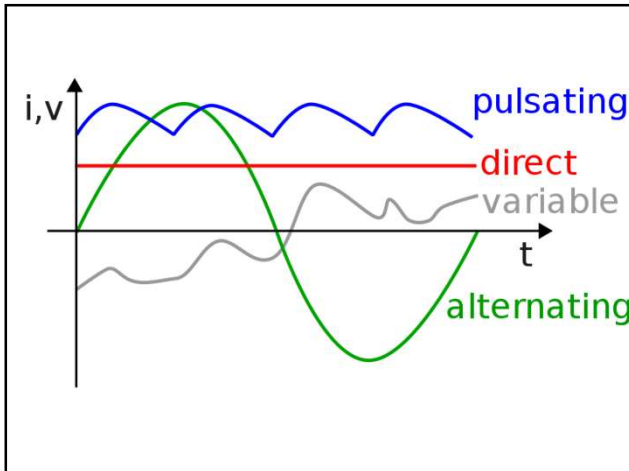


70

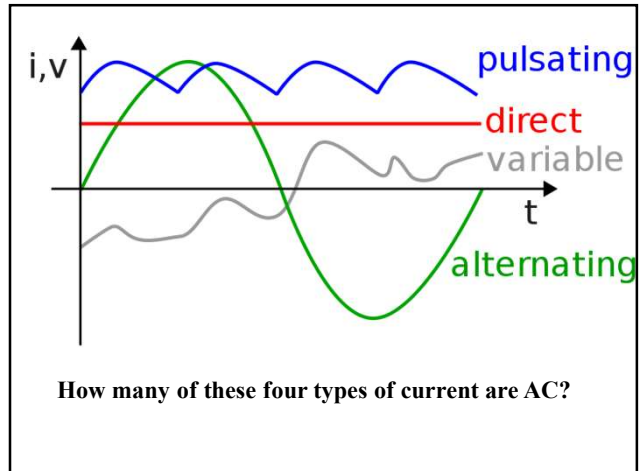


72

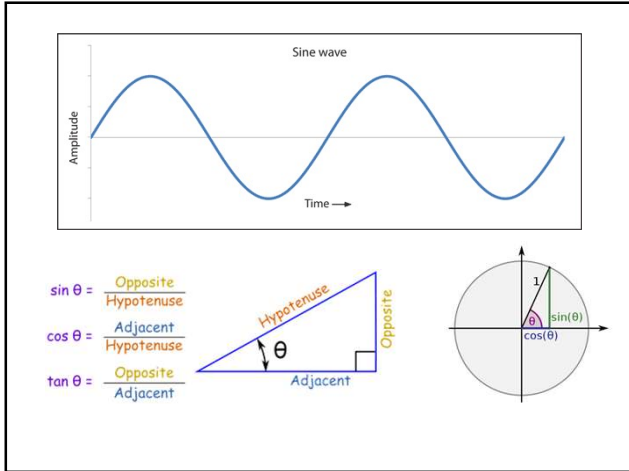


73

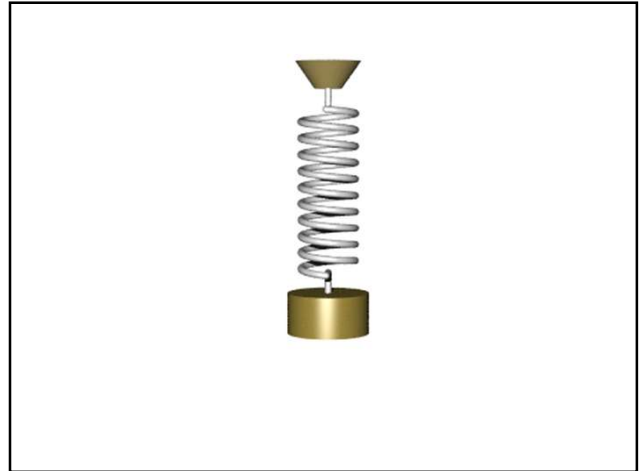


75

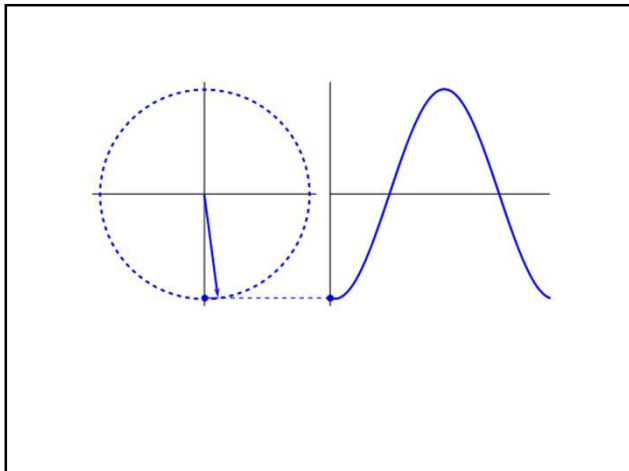


74

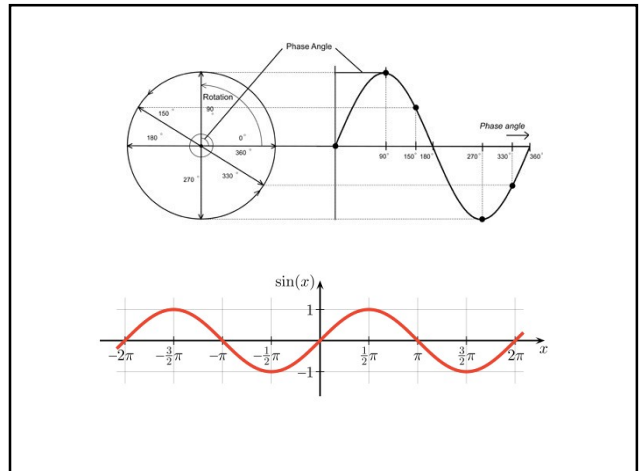


76

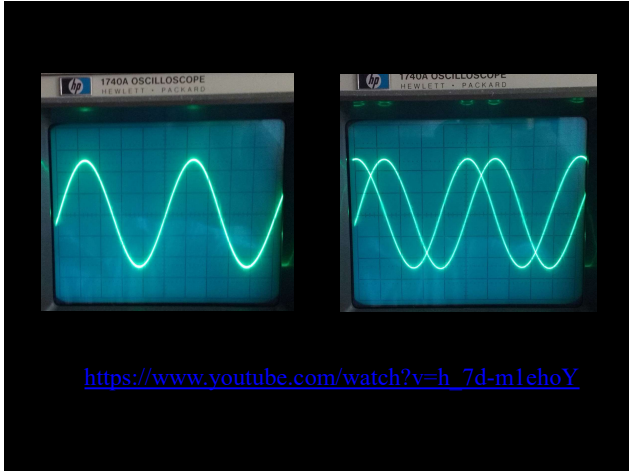


77

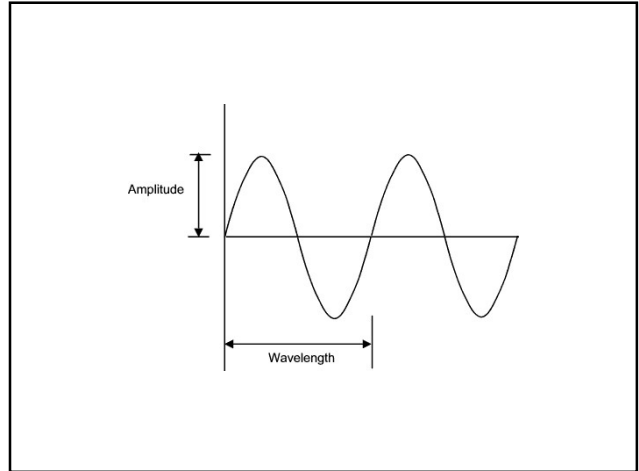


79

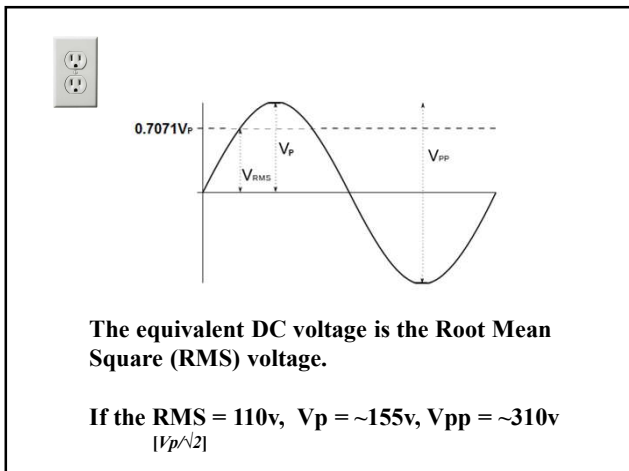


78

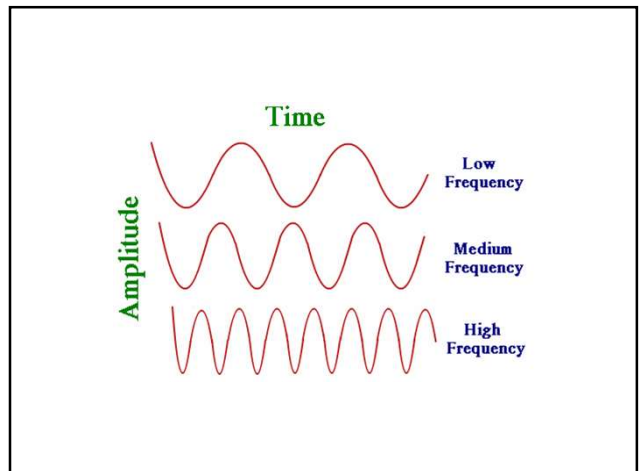


80

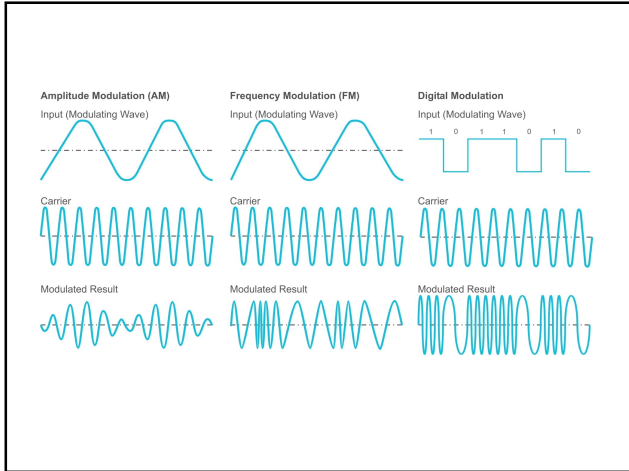


81

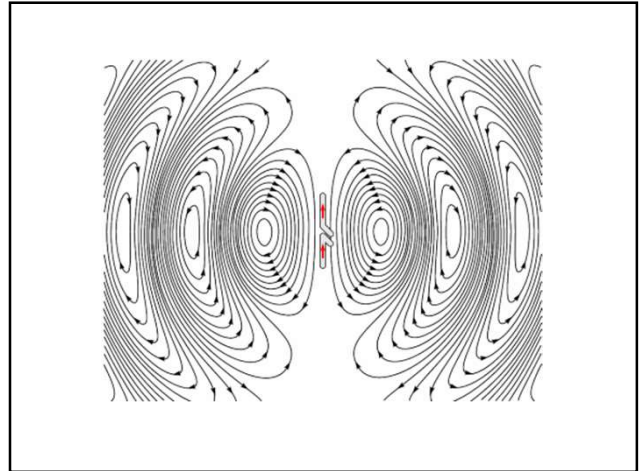


83

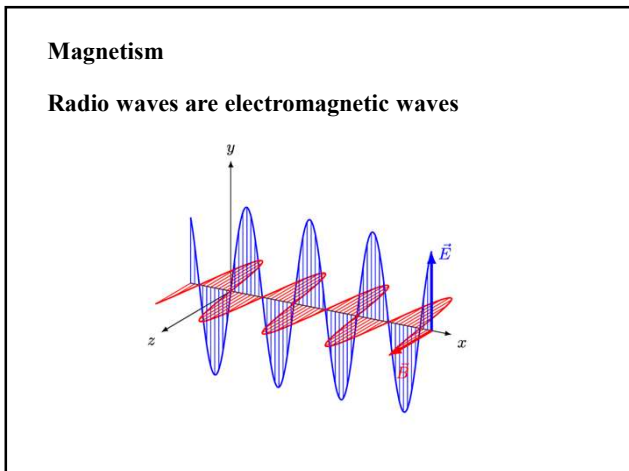


82

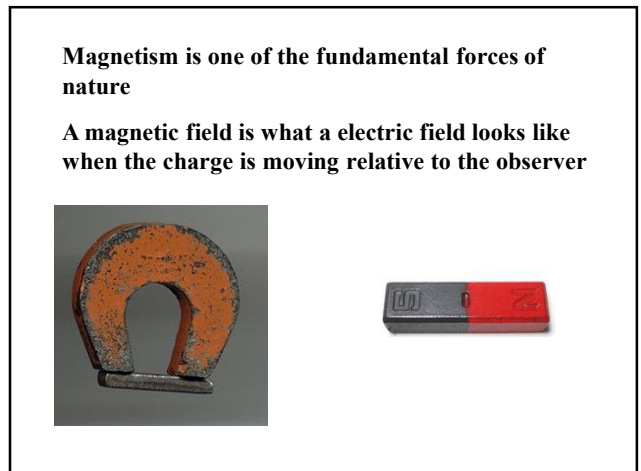


84

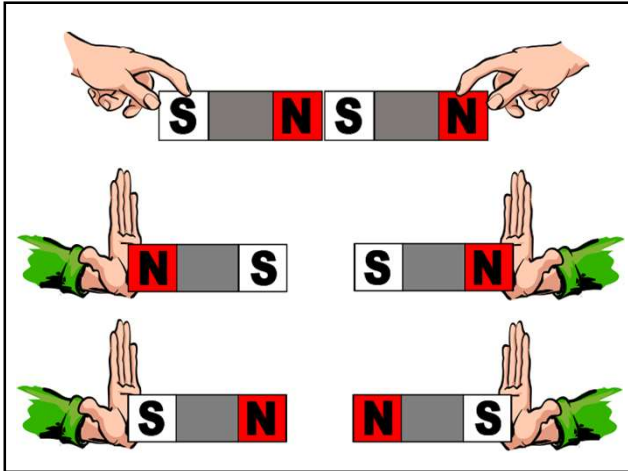


85

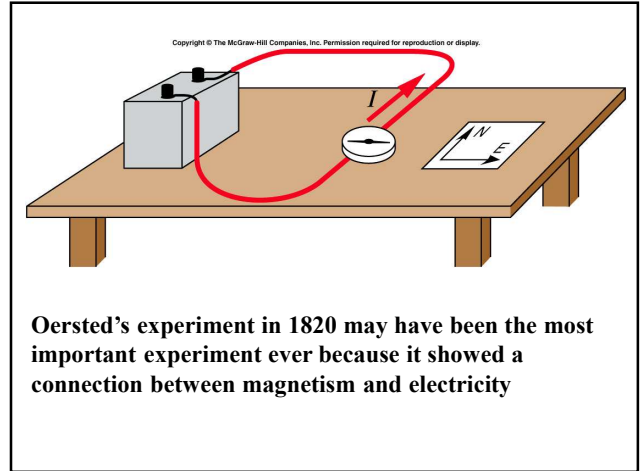


87

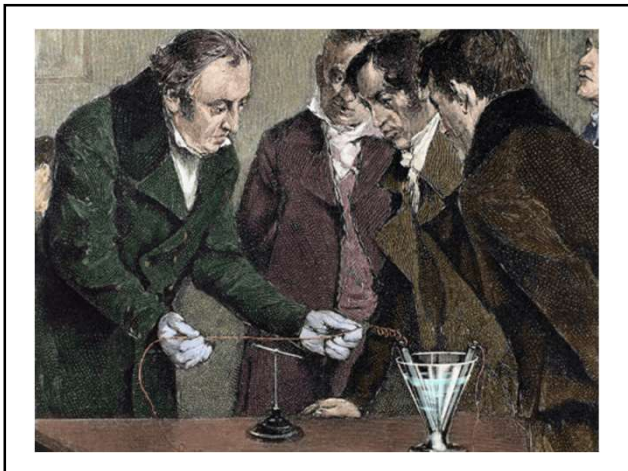


86

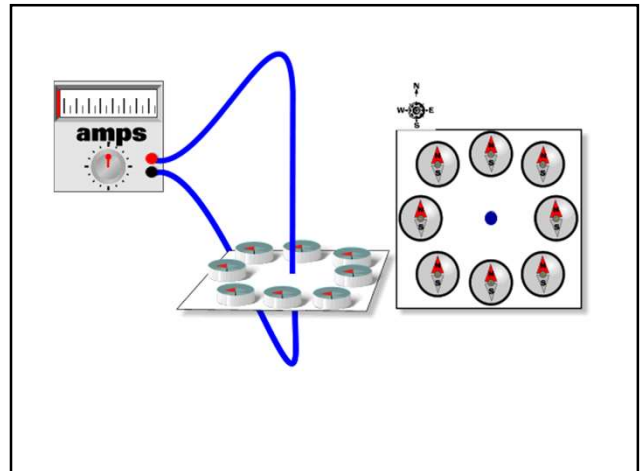


88

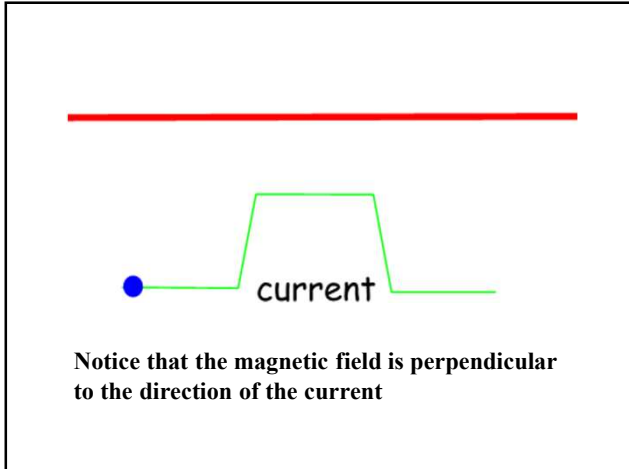

89

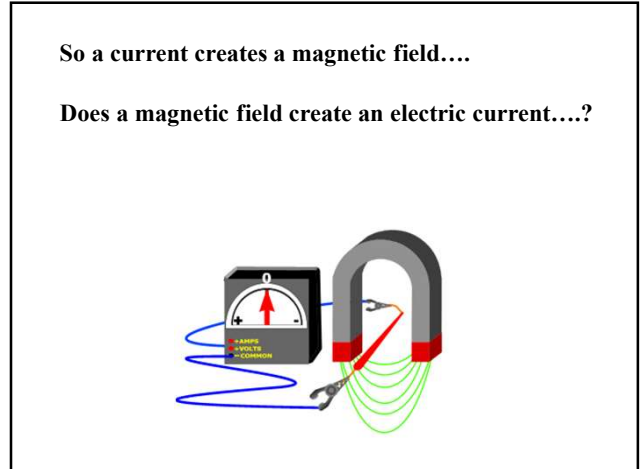

91

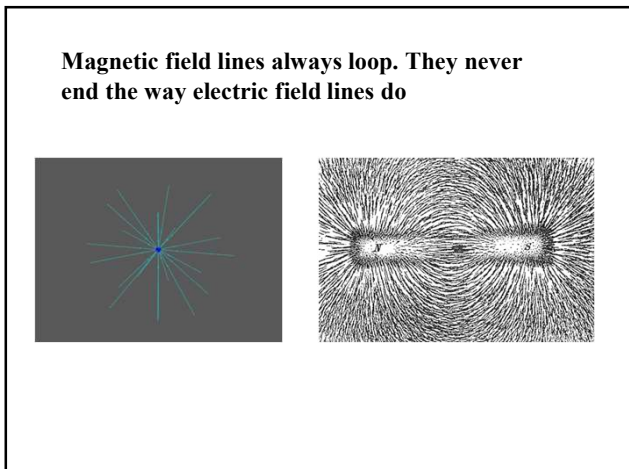

90



92

**We will need to think about magnetic fields when we look at inductance...**

**Next time...**