

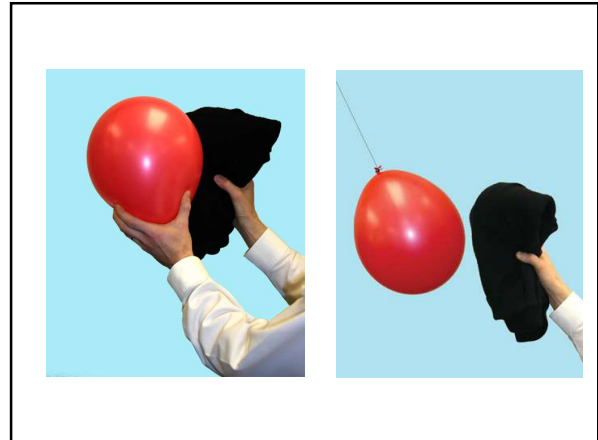

LARC BASIC AMATEUR RADIO COURSE - 2019
CAPACITANCE and INDUCTANCE (Chapter 4)
Mike Cook[®] VE3ZMC


1



3

Capacitance and Inductance are very important properties affecting AC currents.

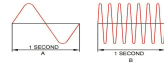They are both frequency-dependent properties.



We will also look at the phenomenon of resonance which is very important for radio and involves both capacitance and inductance.


There are two kinds of induction, electrostatic and electromagnetic.

Electrostatic induction is involved in the way capacitors work so we will start with capacitance.


2




4

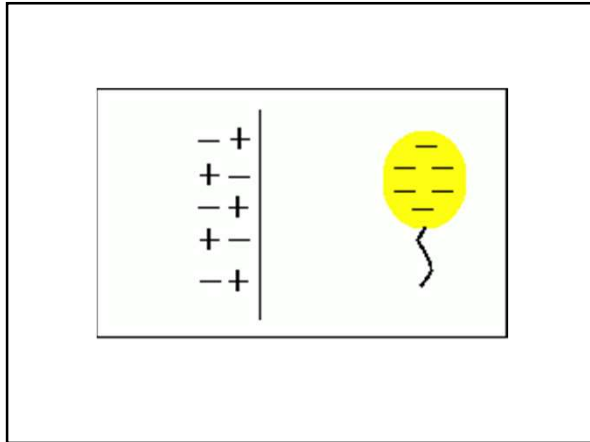


5

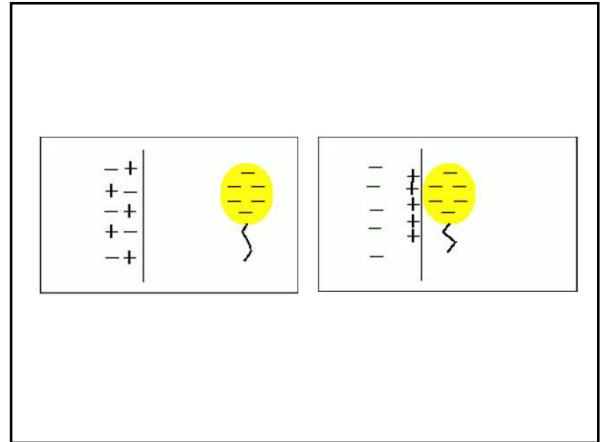


7

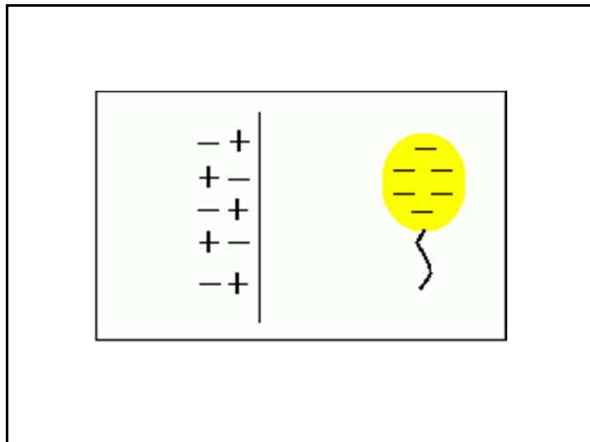


6

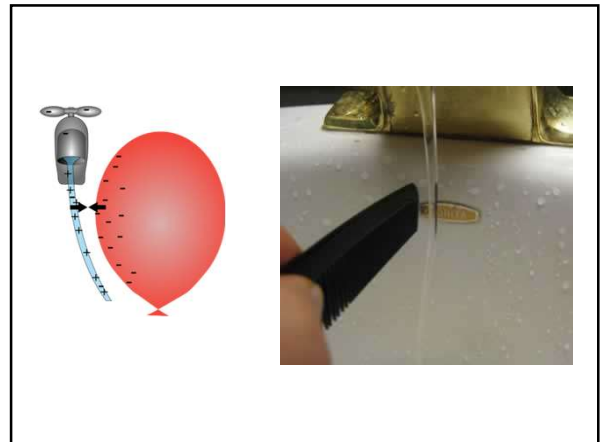


8

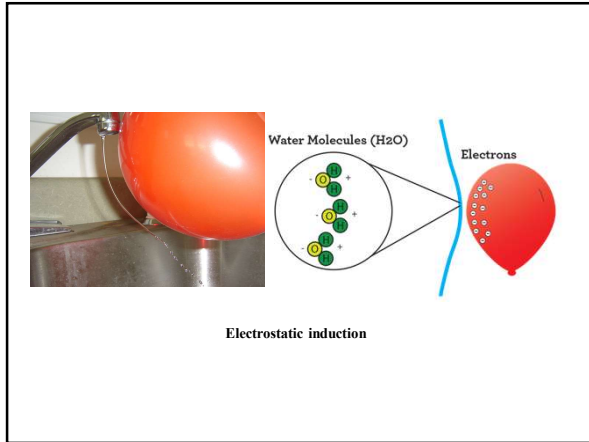


9

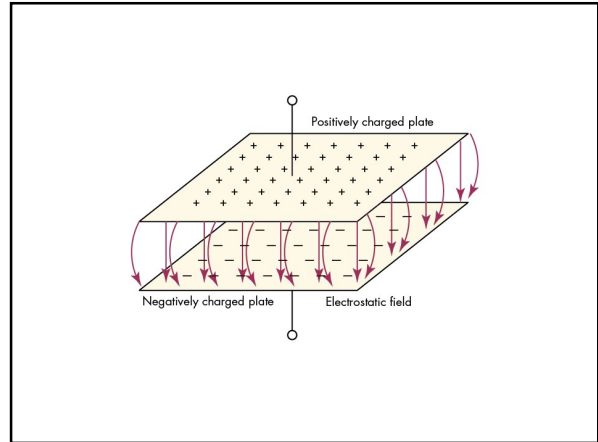


11

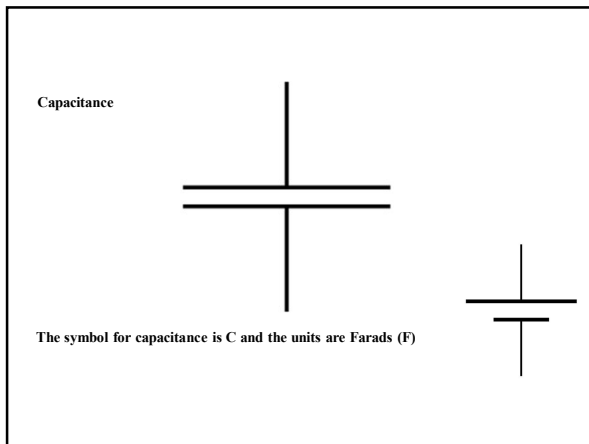


10

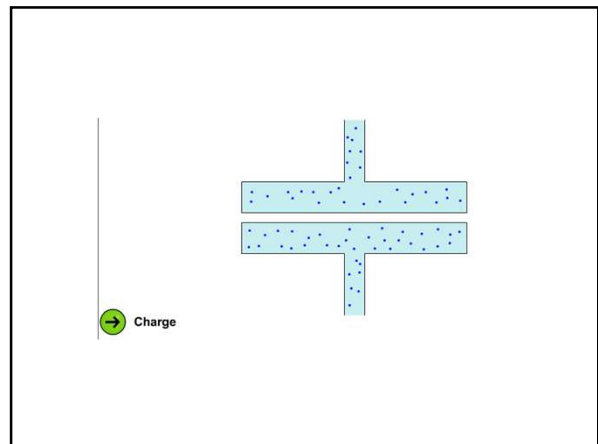

12

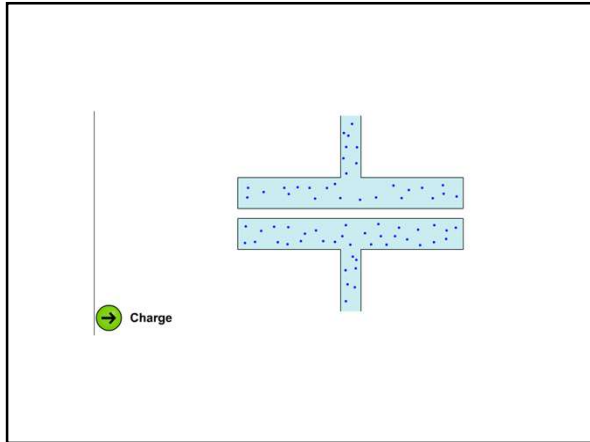

13

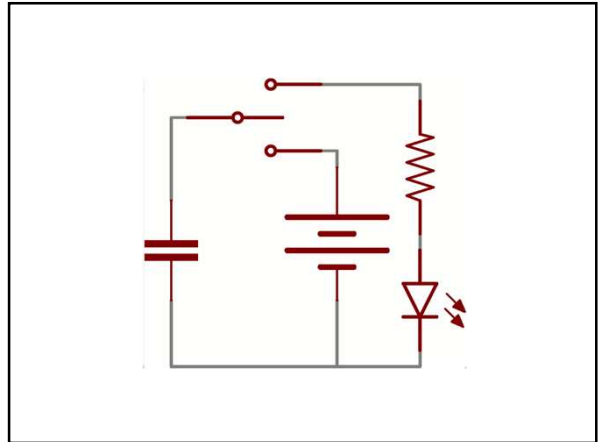

15

Capacitor charging

Electric field
Dielectric
Positively charged
Negatively charged
Capacitor
Conductive plates
Voltage
Electrons
Holes


Capacitor Charging

ΔV applied
charge: $0 \rightarrow \pm Q$


Using DC, the current only flows until the charge on the plate saturates

Removing the battery and connecting a load allows current to flow and discharge the capacitor

14

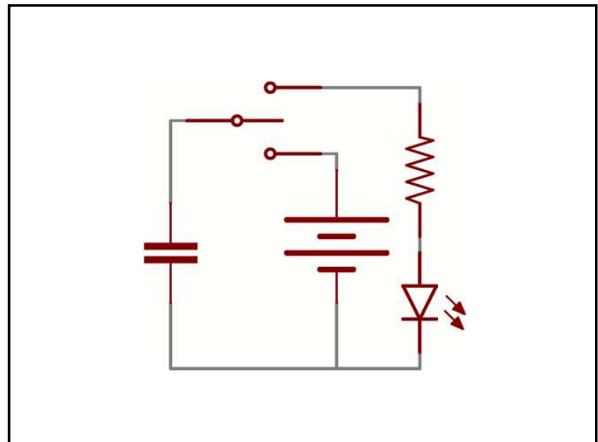

16

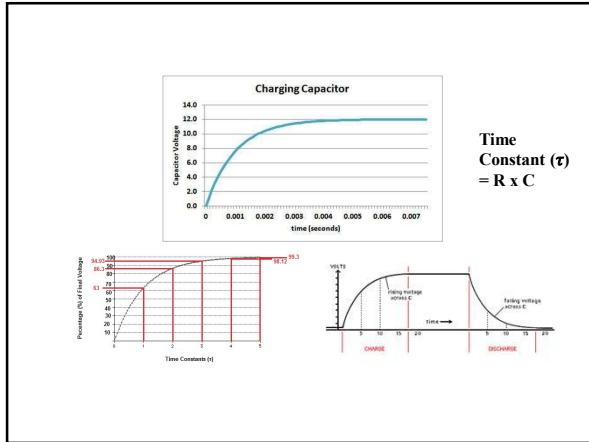

17

A very brief flow of current occurs and then it stops.
The charge is stored. *So capacitors block DC current*


But what happens if AC current is used?

AC

DC

AC can pass depending on frequency (f) (or wavelength (λ))

19

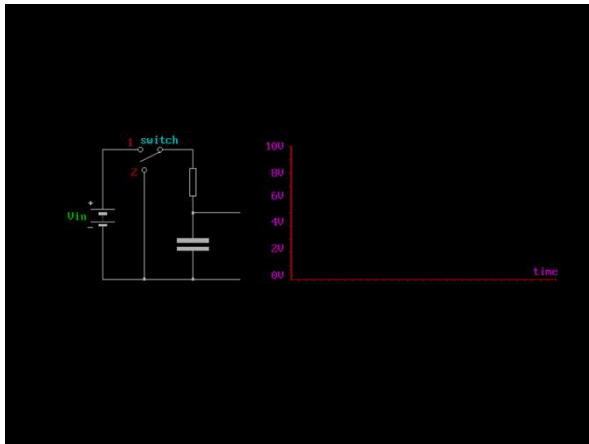


18

Ohms


frequency

For “resistance” to AC current we use the term “reactance” symbol X and units Ω


20

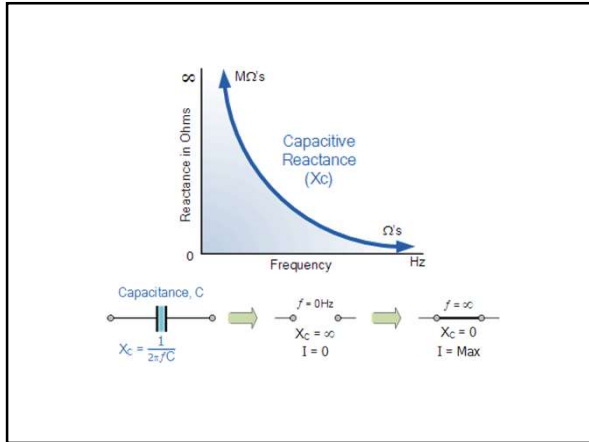


21

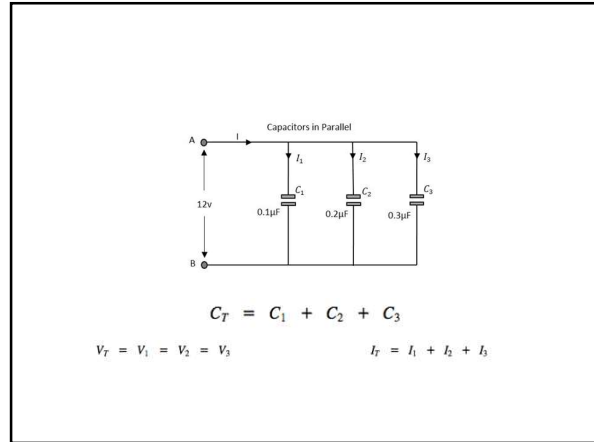


23

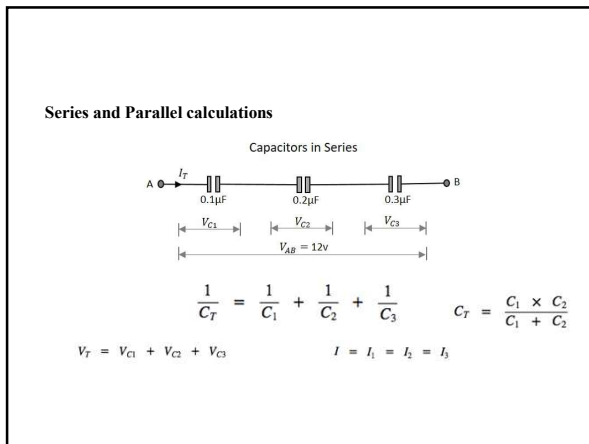

22

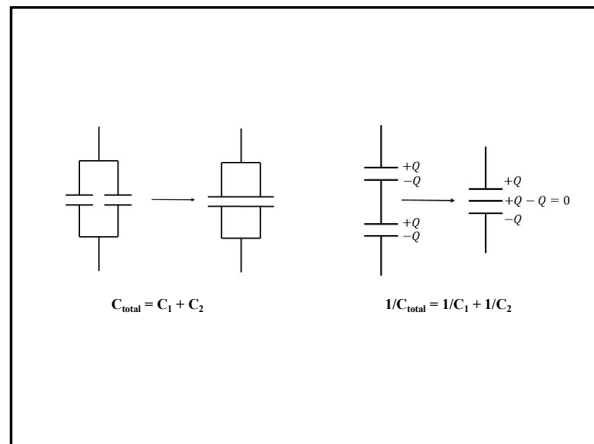

24

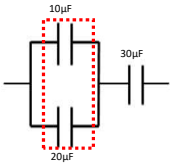


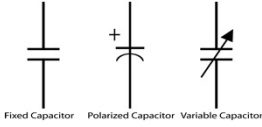
Parallel first:
 $C_1 = 10\mu\text{F} + 20\mu\text{F} = 30\mu\text{F}$
Then series:
 $1/C_{\text{total}} = 1/C_1 + 1/C_2 = 1/30\mu\text{F} + 1/30\mu\text{F} = 2/30\mu\text{F}$
 $C_{\text{total}} = 30\mu\text{F}/2 = 15\mu\text{F}$
Or $30 \times 30 / 30 + 30 = 900 / 60 = 15$

25



27

There are many types of capacitors

Fixed Capacitor Polarized Capacitor Variable Capacitor
 Images of Glass Capacitors

26

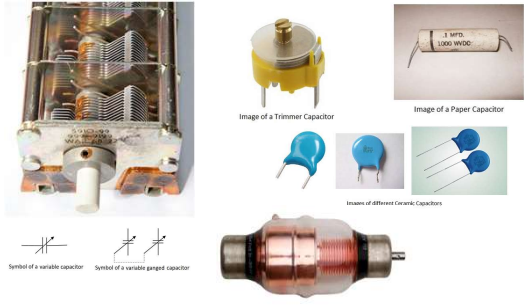



Image of a variable capacitor Symbol of a variable capacitor Symbol of a variable ganged capacitor
 Image of a Trimmer Capacitor Image of a Paper Capacitor
 Images of different Ceramic Capacitors


28

Capacitance depends on the area of the plates, the distance between the plates, and the dielectric in between them. The dielectric can include air, glass, polyethylene, mica, Teflon® etc.


Vacuum capacitors (fixed or variable) are designed to overcome high voltage breakdown. You will see them used in loop antennas.




29

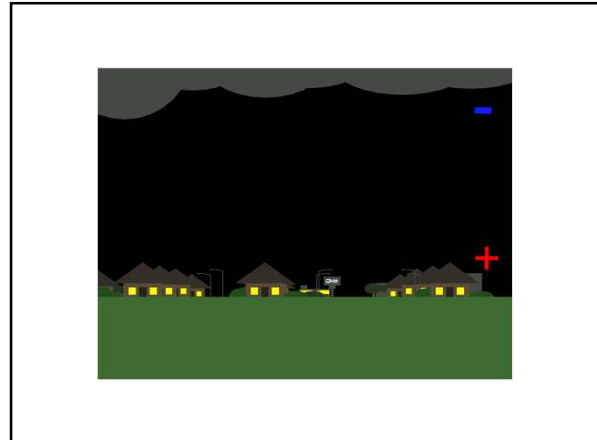

31

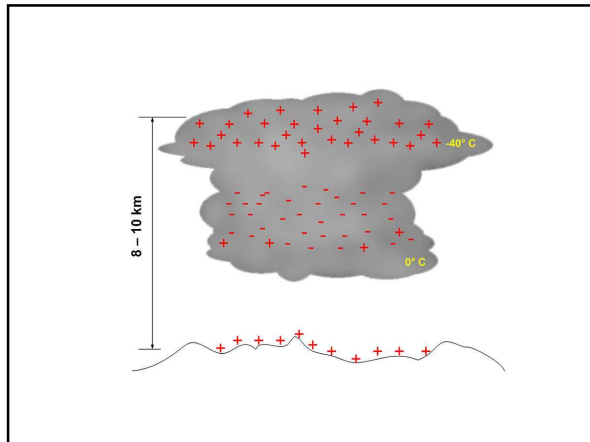


30




Can you see the positive upstroke?
 Luminosity is very low because the current is very low
 Photographs like this are very rare


32

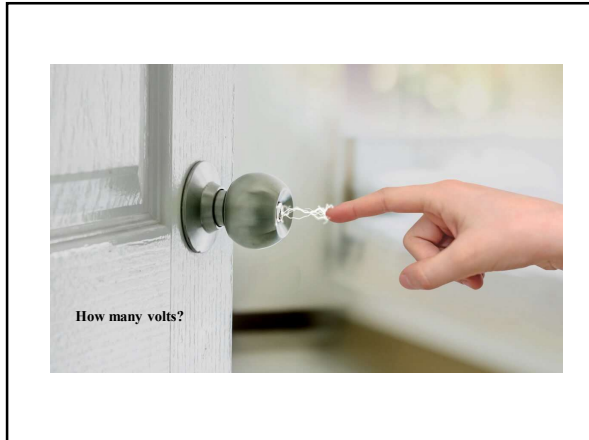


33

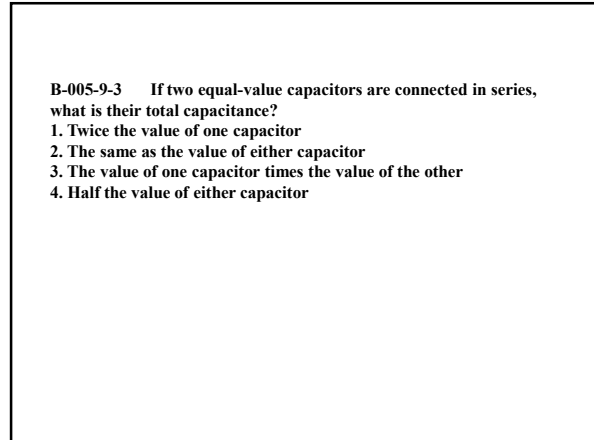

35

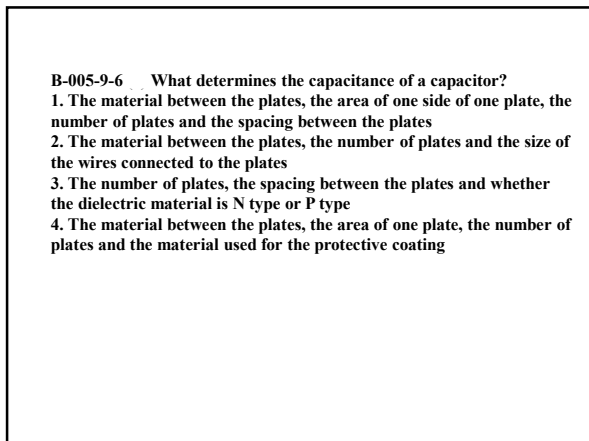

34

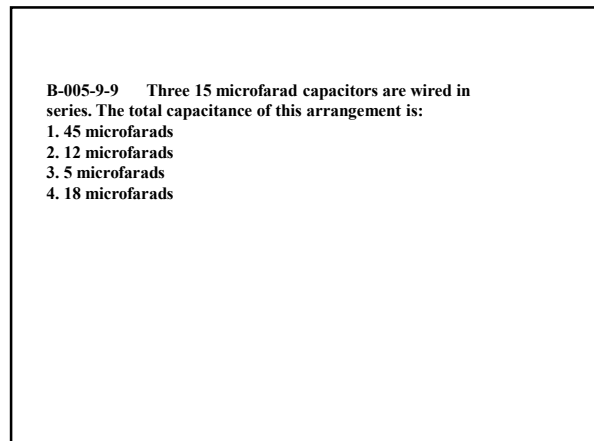


36

B-005-9-7 If two equal-value capacitors are connected in parallel, what is their capacitance?

1. The same value of either capacitor
2. The value of one capacitor times the value of the other
3. Half the value of either capacitor
4. Twice the value of either capacitor

37

Inductance

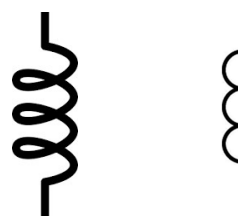


The symbol for inductance is L and the units are Henrys (H)

39


B-005-10-2 How does a capacitor react to AC?

1. As the frequency of the applied AC increases, the reactance decreases
2. As the frequency of the applied AC increases, the reactance increases
3. As the amplitude of the applied AC increases, the reactance increases
4. As the amplitude of the applied AC increases, the reactance decreases


38

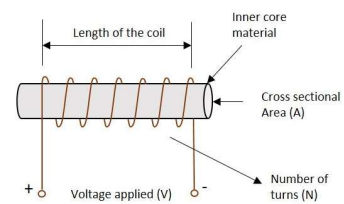

40

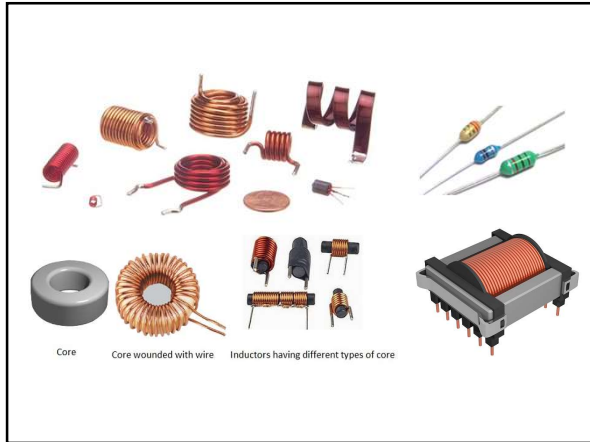


41

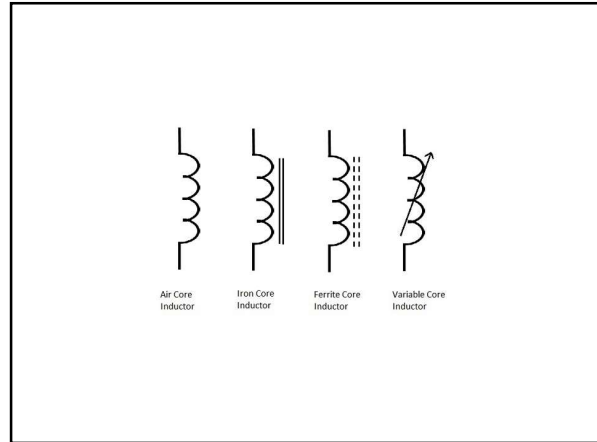


43




42

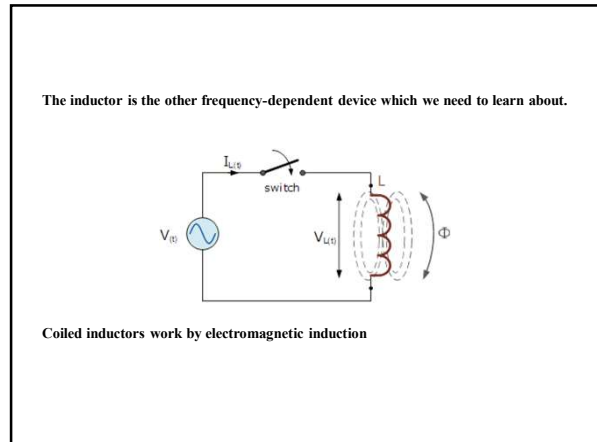


44

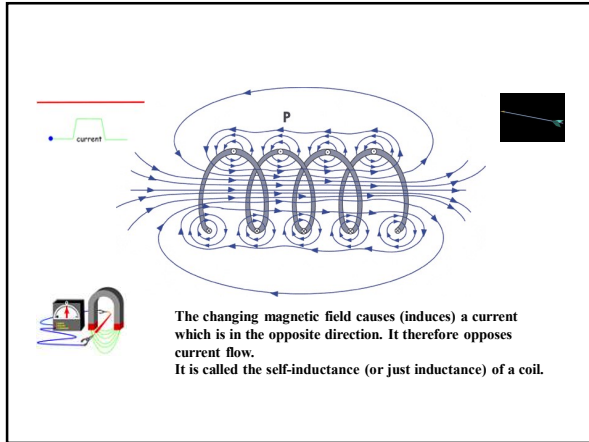


45

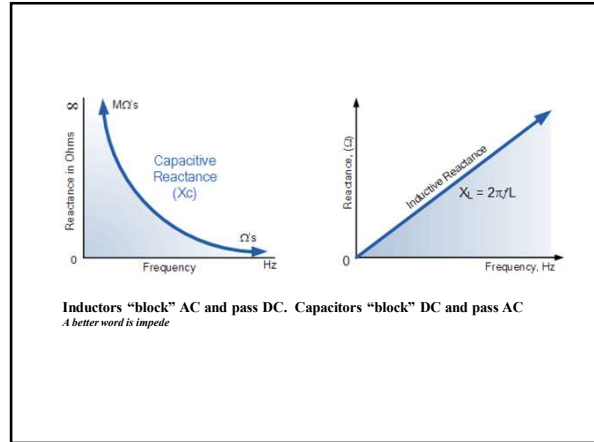

47

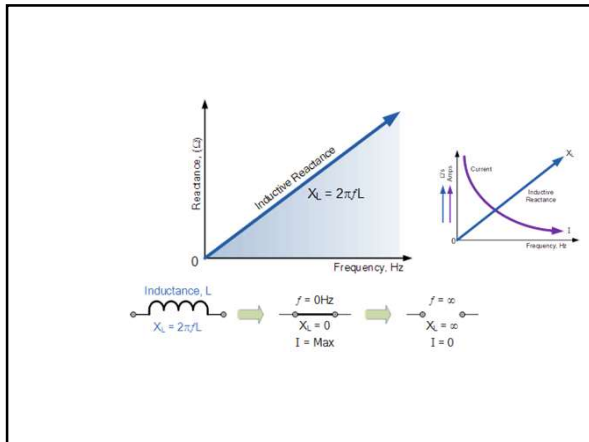

46

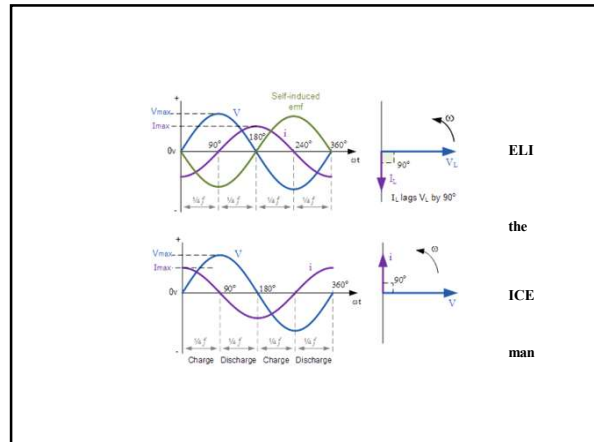

48

Series and Parallel calculations *similar to resistance*

Inductors in Series

$L_T = L_1 + L_2 + L_3$

$V = V_1 + V_2 + V_3$ $I = I_1 = I_2 = I_3$

49

B-005-9-1 If two equal-value inductors are connected in series, what is their total inductance?

1. Half the value of one inductor
2. The same as the value of either inductor
3. The value of one inductor times the value of the other
4. Twice the value of one inductor

51

Inductors in Parallel

$L_T = \frac{L_1 \times L_2}{L_1 + L_2}$

$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$

$V = V_1 = V_2 = V_3$ $I = I_1 + I_2 + I_3$

50


B-005-9-5 What determines the inductance of a coil?

1. The core material, the number of turns used to wind the core and the frequency of the current through the coil
2. The core diameter, the number of turns of wire used to wind the coil and the type of metal used for the wire
3. The core material, the core diameter, the length of the coil and the number of turns of wire used to wind the coil
4. The core material, the core diameter, the length of the coil and whether the coil is mounted horizontally or vertically


52

B-005-10-10 What is the approximate inductive reactance of a 1.0 Henry choke coil used in a 60 hertz circuit?
 1. 376 ohms
 2. 3760 ohms
 3. 188 ohms
 4. 1888 ohms


53

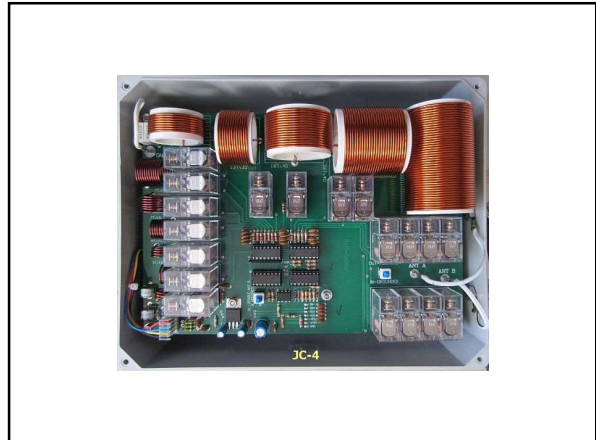


55

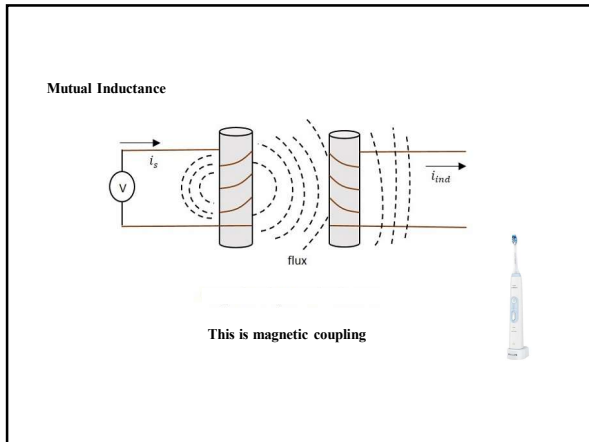


54

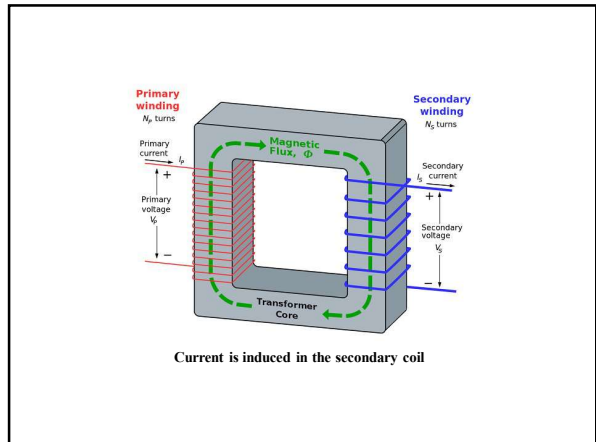

56

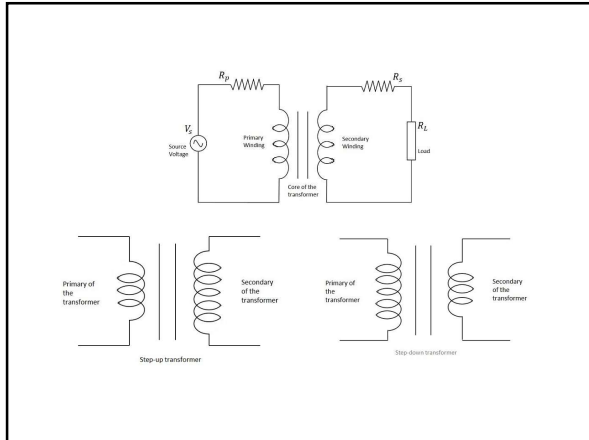

57

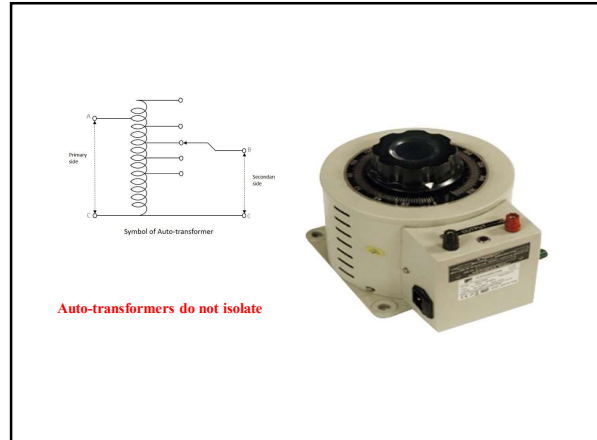

Auto-transformers do not isolate

59

$$\frac{E_S}{E_P} = \frac{N_S}{N_P} \quad \text{Eqn 4-3}$$

$$E_P = 150 \text{ VAC}$$

$$N_P = 120 \text{ turns}$$

$$\frac{N_S}{N_P} = 5:2$$

$$N_S = \frac{5 \times 120}{2} = 300 \text{ turns}$$

$$E_S = \frac{300 \times 150}{120} = 375 \text{ V}$$

58



60

B-005-11-4 In a mains power transformer, the primary winding has 250 turns, and the secondary has 500. If the input voltage is 110 volts, the likely secondary voltage is:

1. 440 V
2. 220 V
3. 560 V
4. 24 V

61

B-005-10-1 How does a coil react to AC?

1. As the amplitude of the applied AC increases, the reactance decreases
2. As the amplitude of the applied AC increases, the reactance increases
3. As the frequency of the applied AC increases, the reactance increases
4. As the frequency of the applied AC increases, the reactance decreases

63


B-005-11-2 A transformer operates a 6.3 volt 2 ampere light bulb from its secondary winding. The power consumed by the primary winding is approximately:

1. 13 watts
2. 6 watts
3. 8 watts
4. 3 watts


62

Impedance

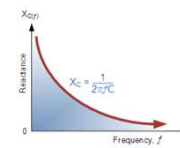We know about reactance now. Circuits can have reactance and resistance



$X_C = \frac{1}{2\pi fC}$

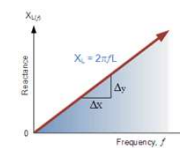

$X_L = 2\pi fL$


$$X_C = \frac{1}{2\pi fC} \quad \text{Eqn 4-7}$$

$$X_L = 2\pi fL \quad \text{Eqn 4-6}$$

64

Impedance Z (measured in Ω) is the sum of reactance and resistance

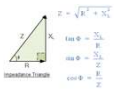
$$Z = \sqrt{R^2 + X^2} \quad \text{Eqn 4-8}$$



Matching impedances is an important concept in radio. The output of a transmitter should have the same impedance as the feed line and antenna it is connected to.


Hams spend a lot of time adjusting the impedance of their antennas so that the maximum power transfer from the transmitter can happen.

65

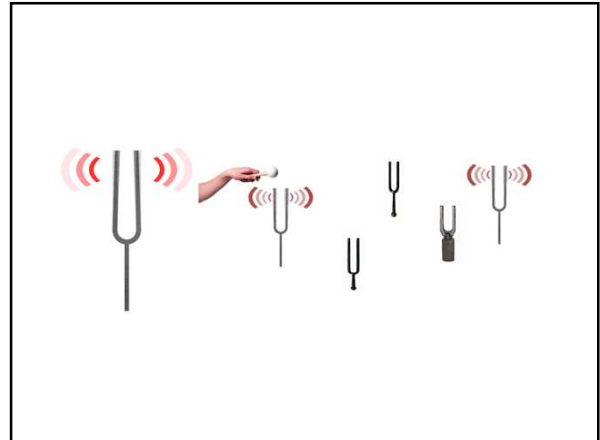

67


Resonance




66




68

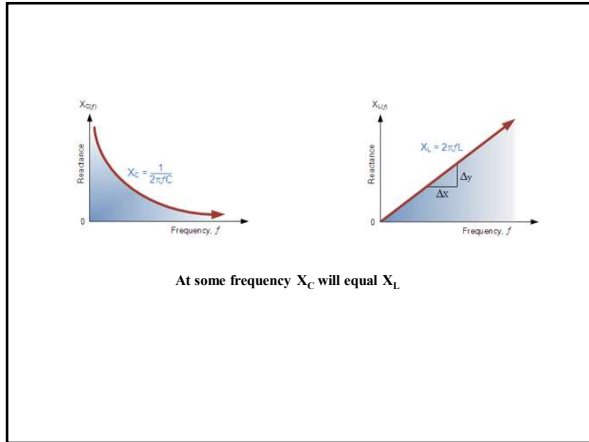


69

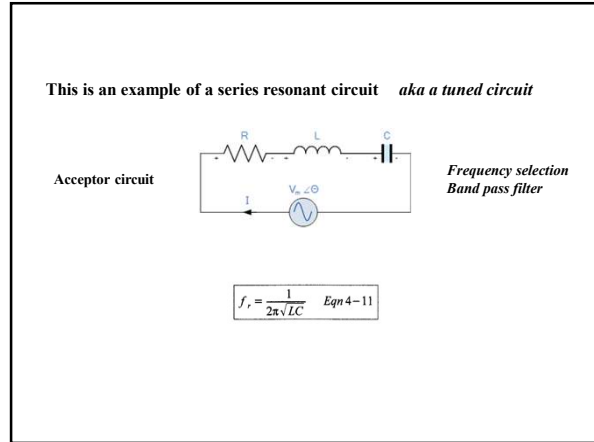


71

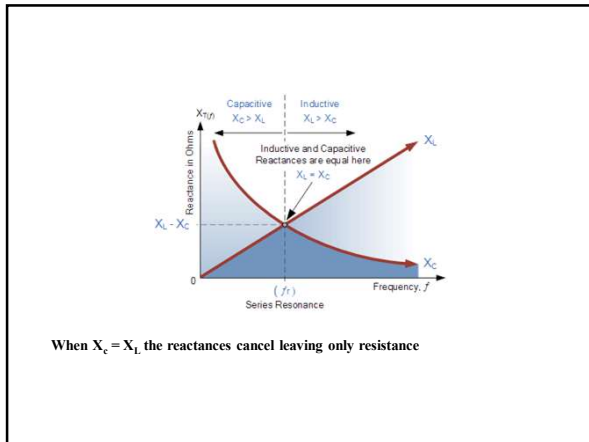


70

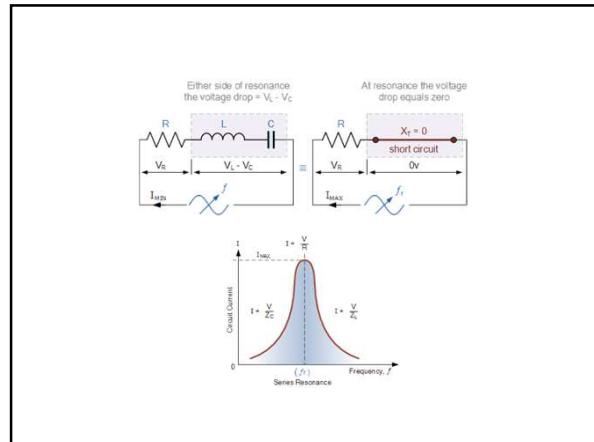


72

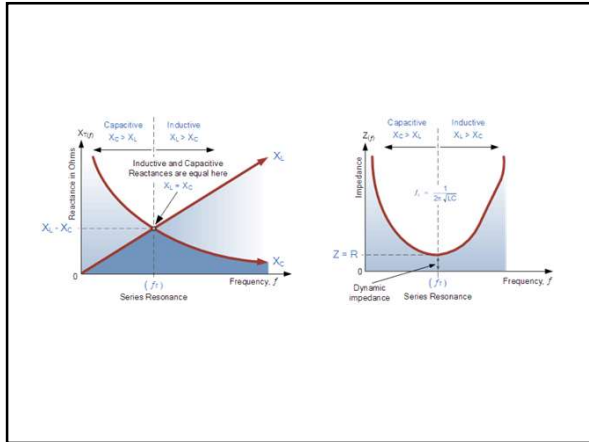


73

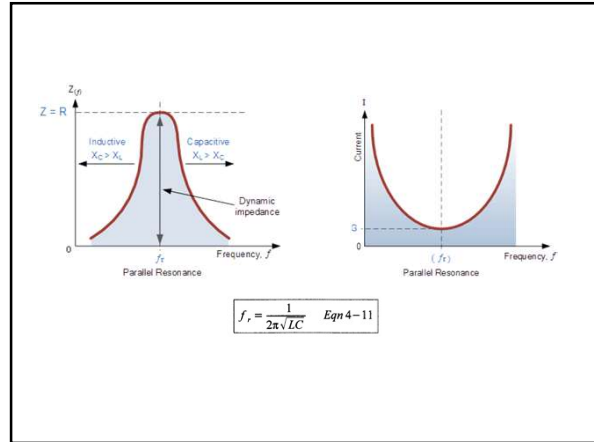


75

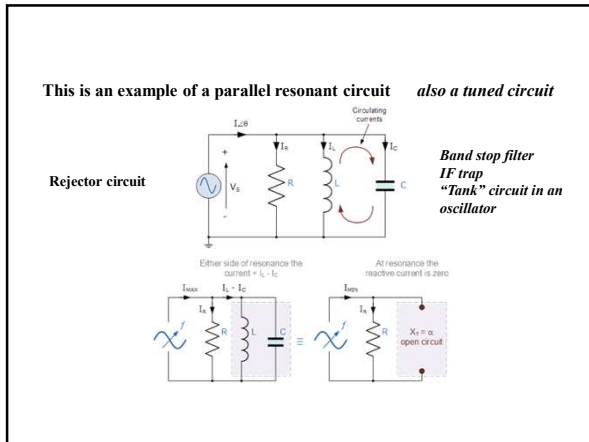


74

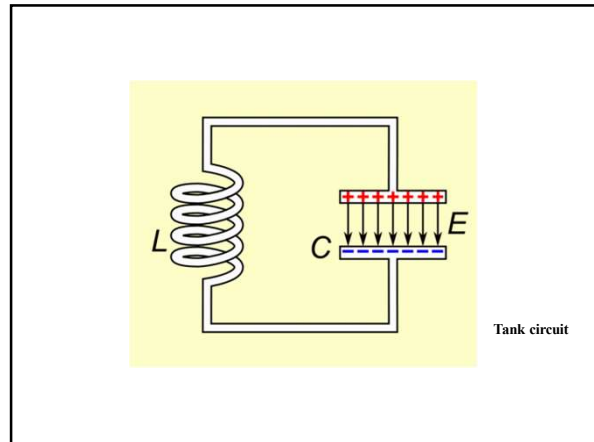


76

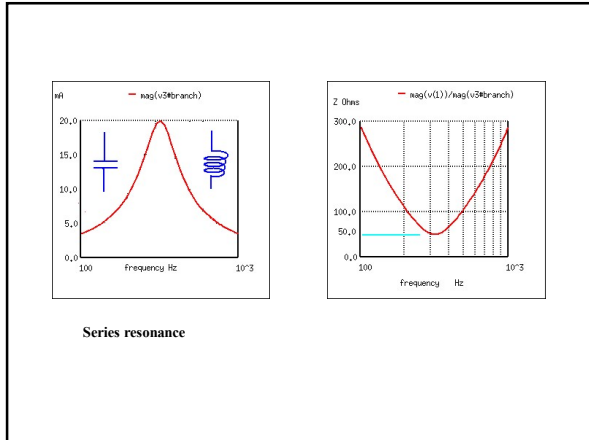


77

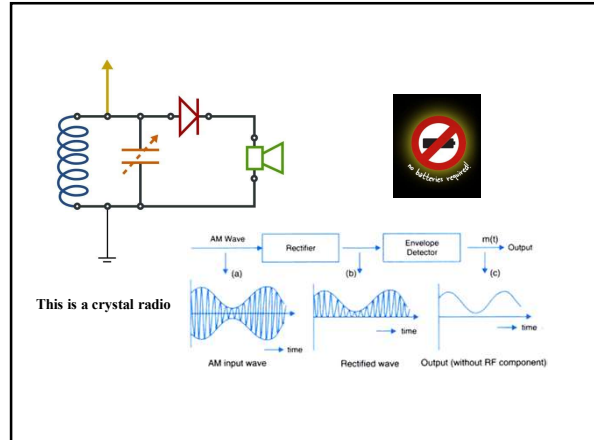


79

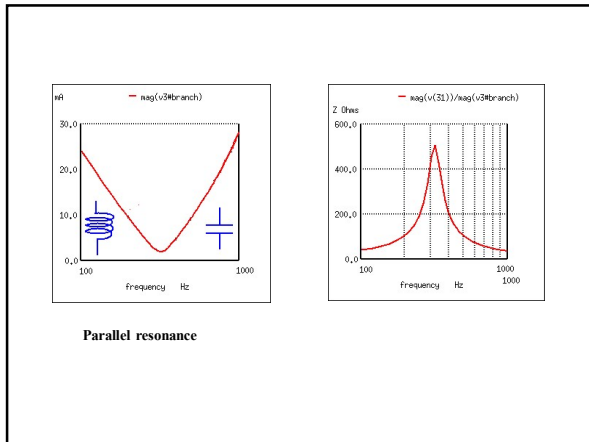


78

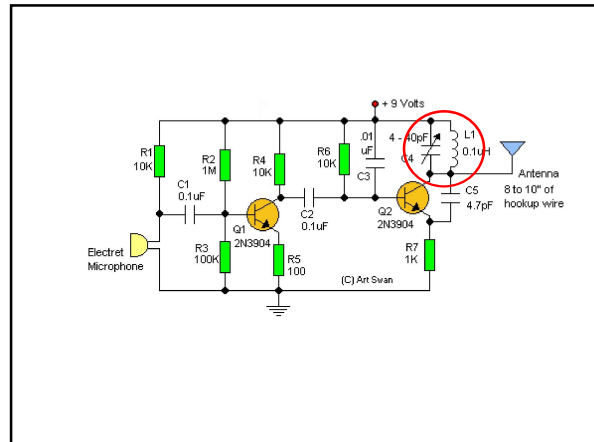


80

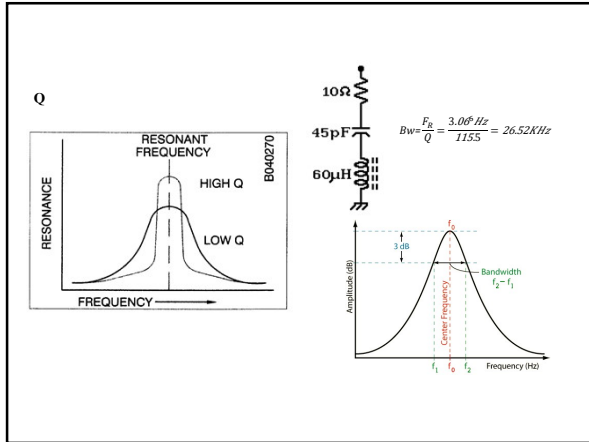

81

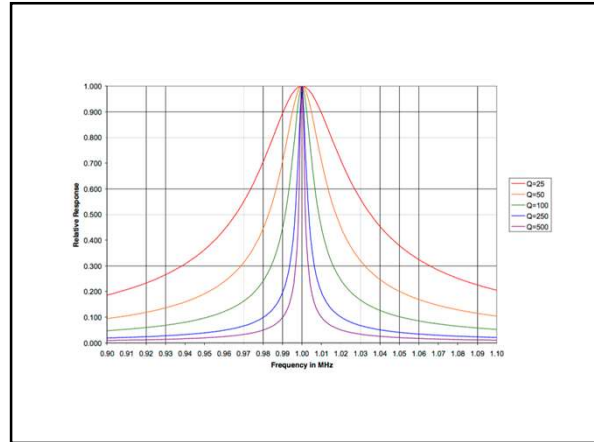

83

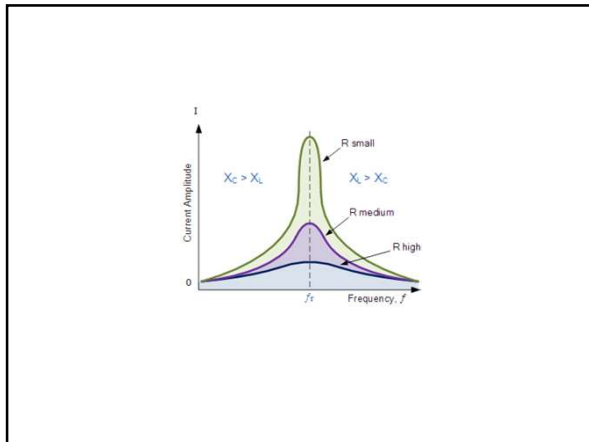

82

B-005-12-1 Resonance is the condition that exists when:

1. inductive reactance and capacitive reactance are equal
2. inductive reactance is the only opposition in the circuit
3. the circuit contains no resistance
4. resistance is equal to the reactance


84

B-005-12-7 In a series resonant circuit at resonance, the circuit has:

1. low impedance
2. high impedance
3. low mutual inductance
4. high mutual inductance

85

Next time: Waves and Propagation

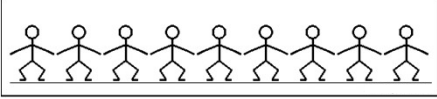

87

B-006-6-5 What happens when the impedance of an electrical load is equal to the internal impedance of the power source?

1. The electrical load is shorted
2. The source delivers maximum power to the load
3. No current can flow through the circuit
4. The source delivers minimum power to the load

86