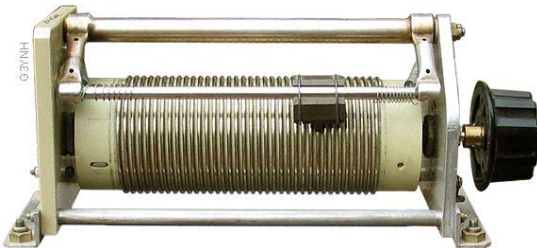




LARC BASIC AMATEUR RADIO COURSE - 2019


CAPACITANCE and INDUCTANCE (Chapter 4)

Mike Cook[©] VE3ZMC



Capacitance and Inductance are very important properties affecting AC currents.

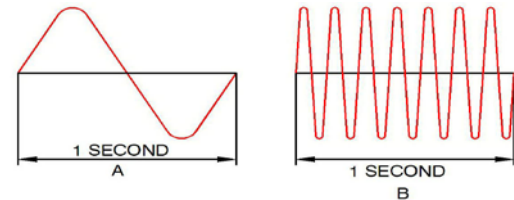They are both frequency-dependent properties.



We will also look at the phenomenon of resonance which is very important for radio and involves both capacitance and inductance.


There are two kinds of induction, electrostatic and electromagnetic.

Electrostatic induction is involved in the way capacitors work so we will start with capacitance.









—	+
+	—
—	+
+	—
—	+

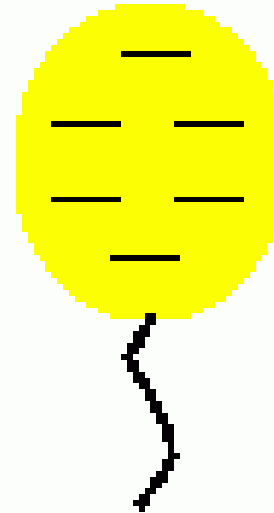

—	+
+	—
—	+
+	—
—	+

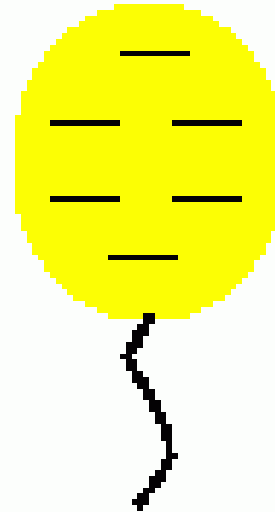


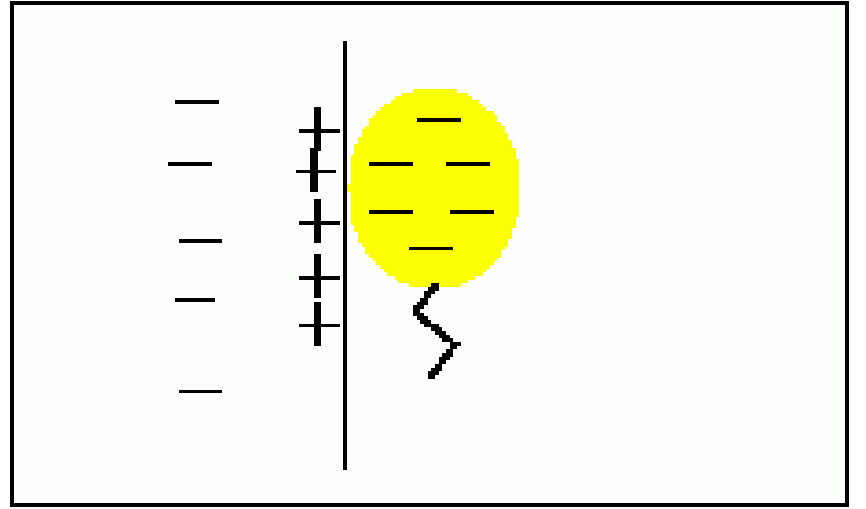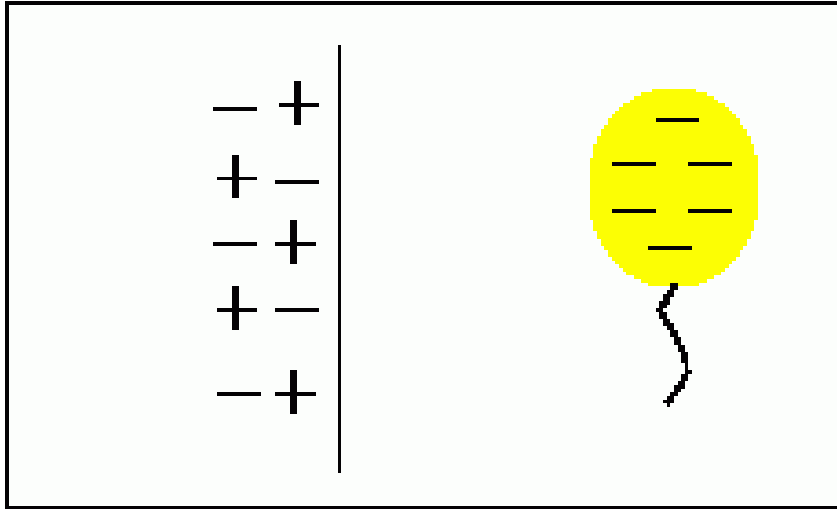

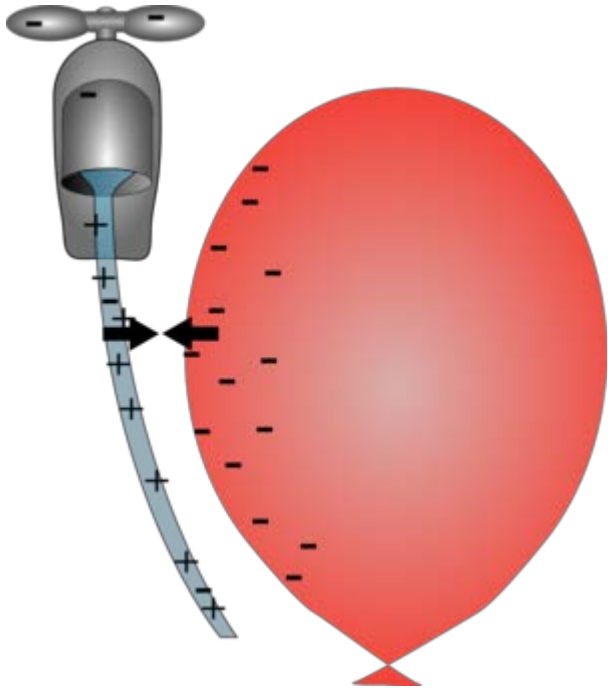




Water Molecules (H₂O)

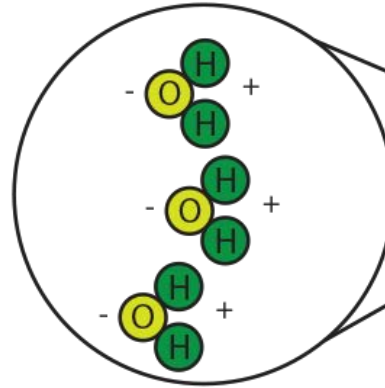


Electrons

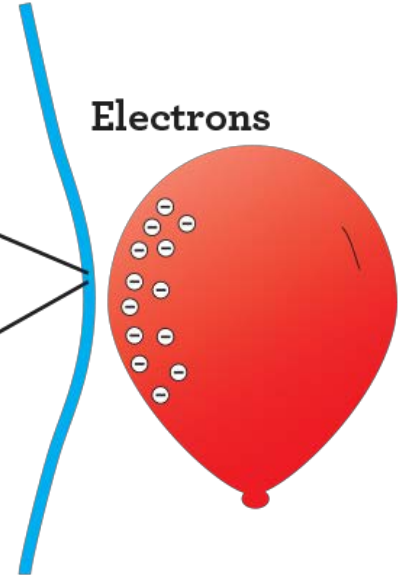



Electrostatic induction

Capacitance

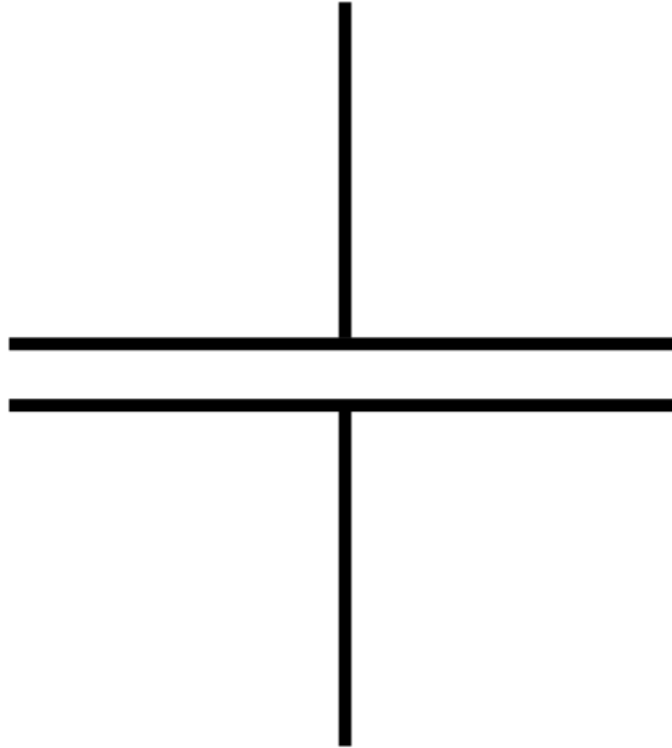


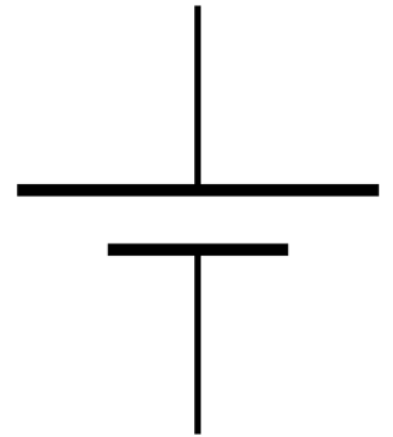The symbol for capacitance is **C** and the units are Farads (**F**)




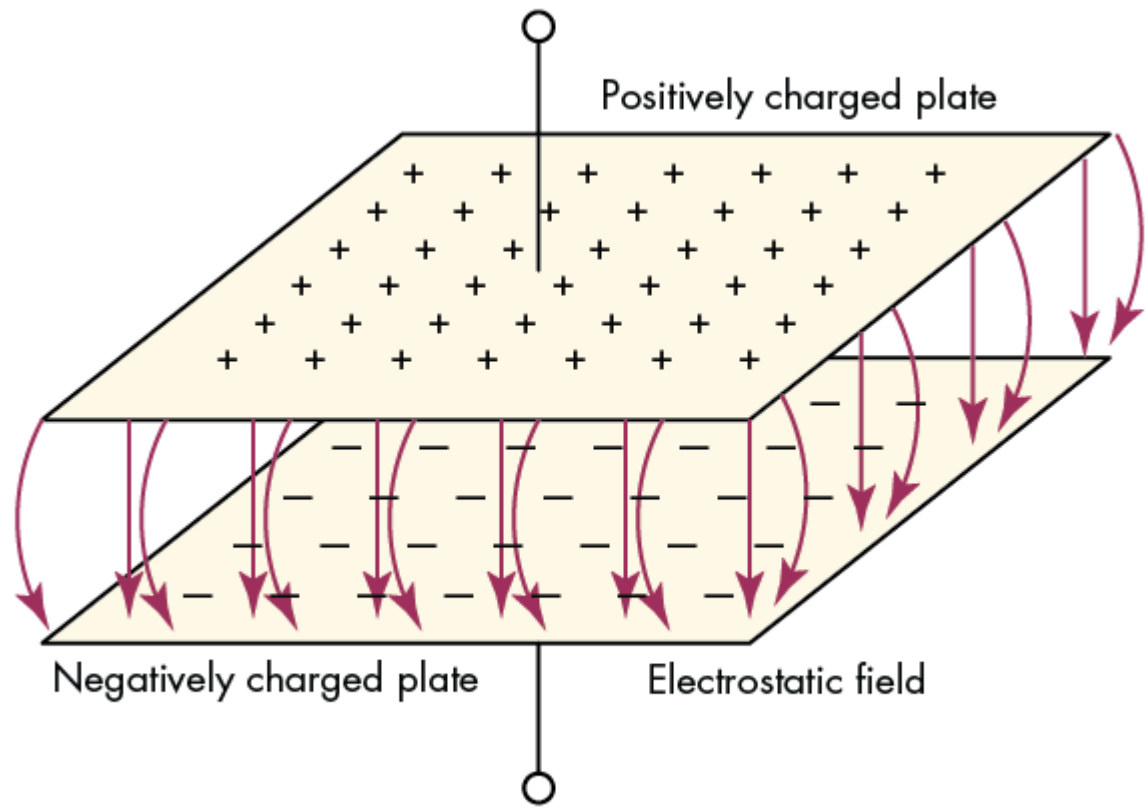


→ Charge

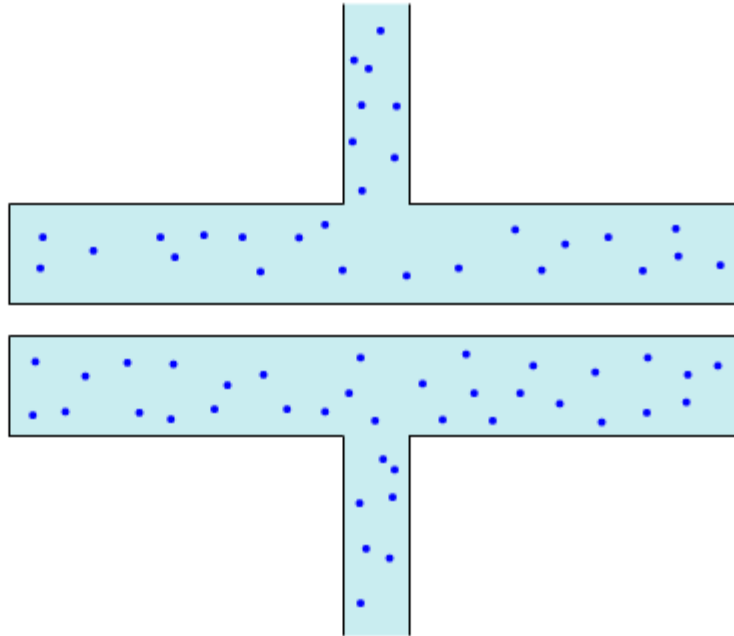


→ Charge

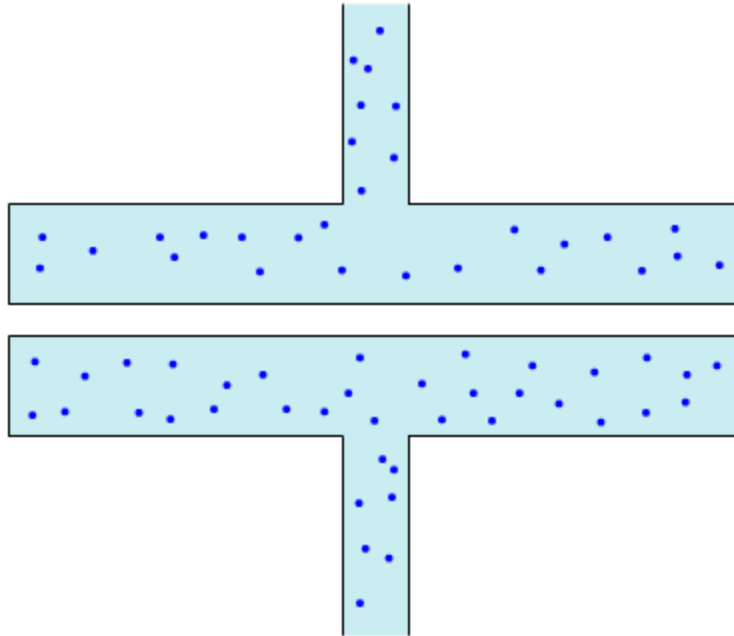

Capacitor charging

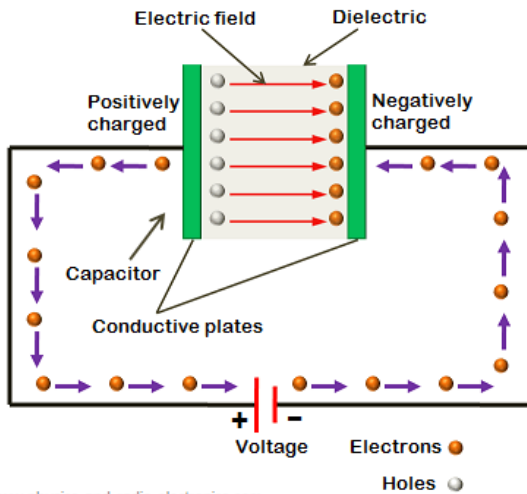



Capacitor Charging

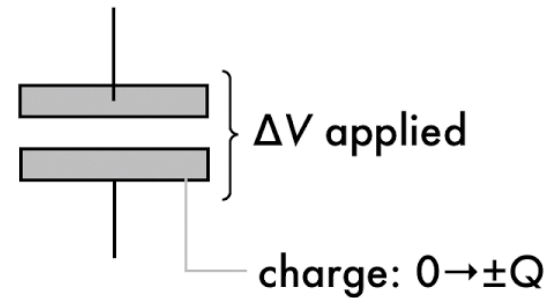


Using DC, the current only flows until the charge on the plate saturates


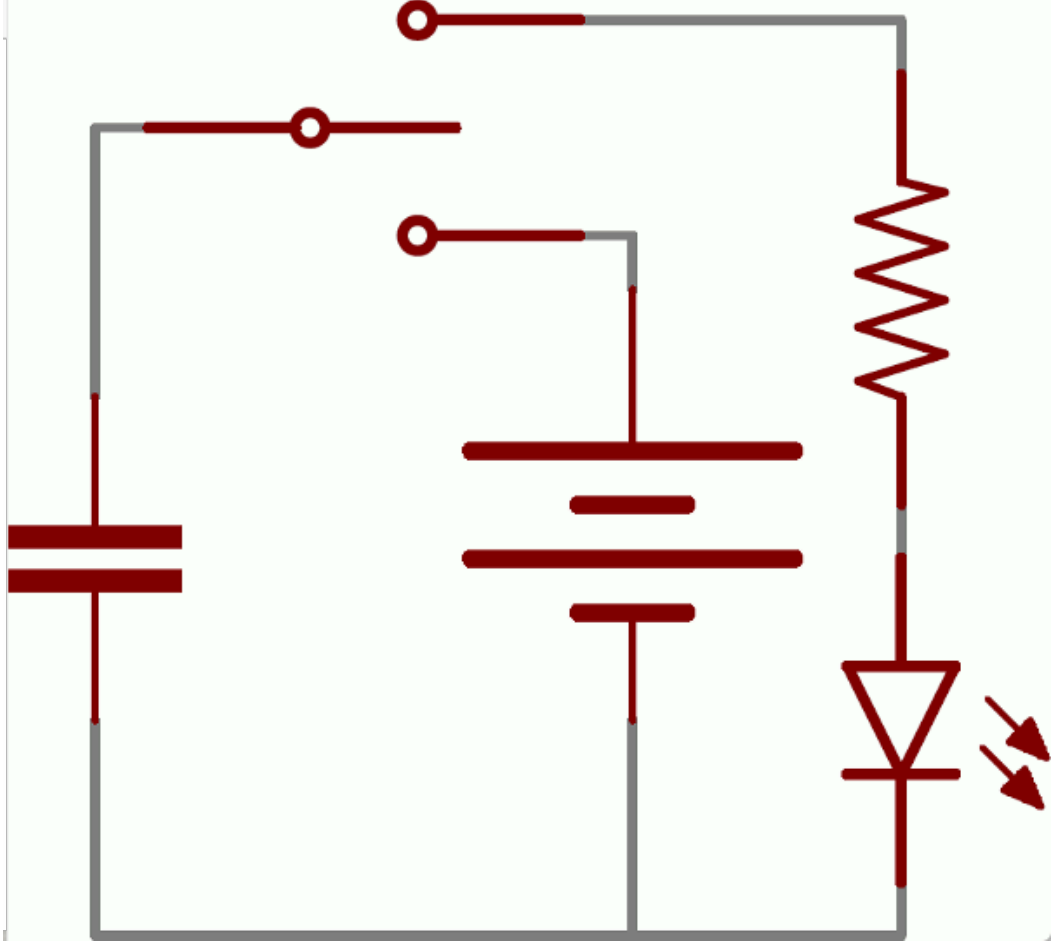
Removing the battery and connecting a load allows current to flow and discharge the capacitor





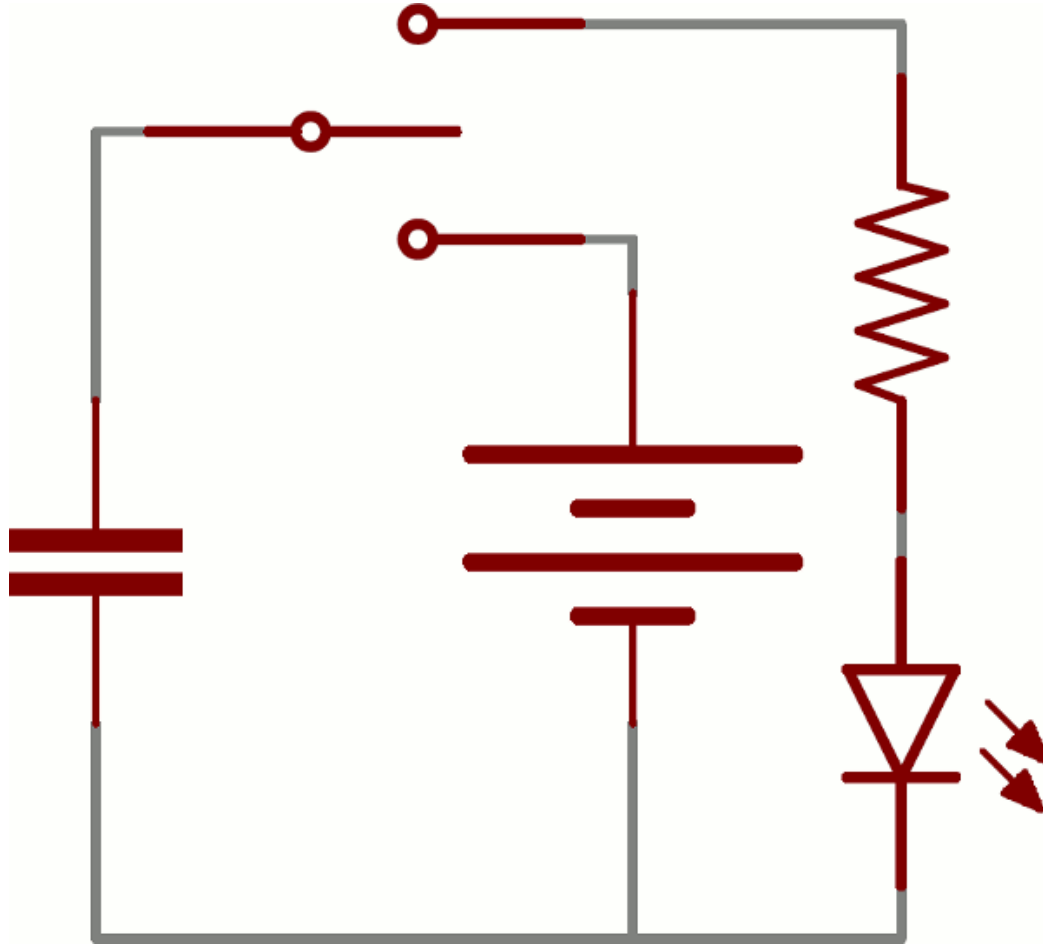

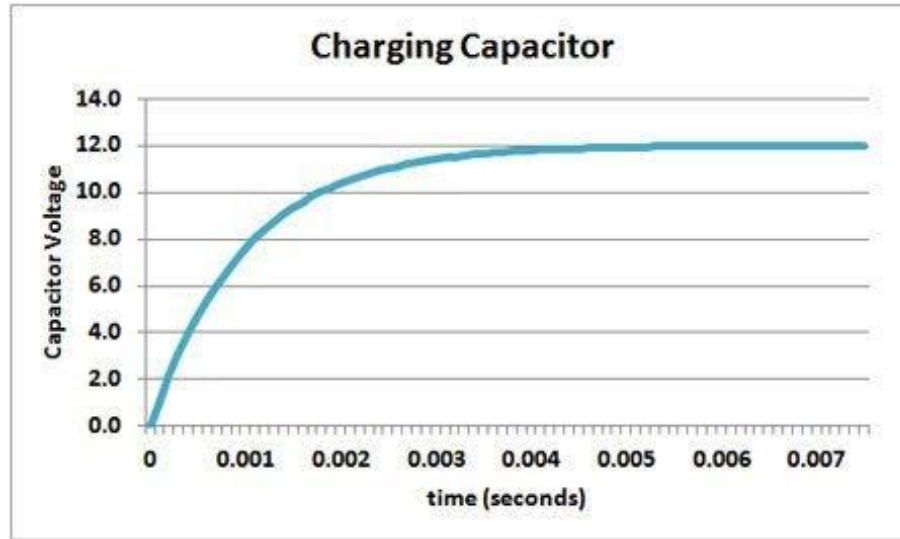



**Time
Constant (τ)
= R x C**

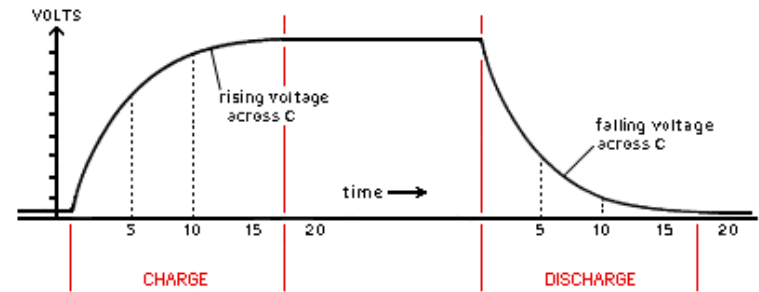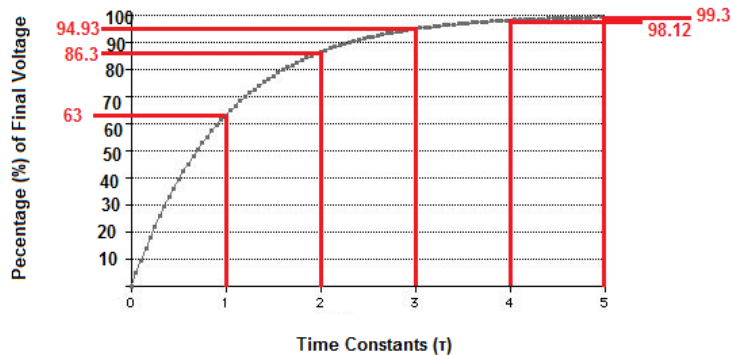

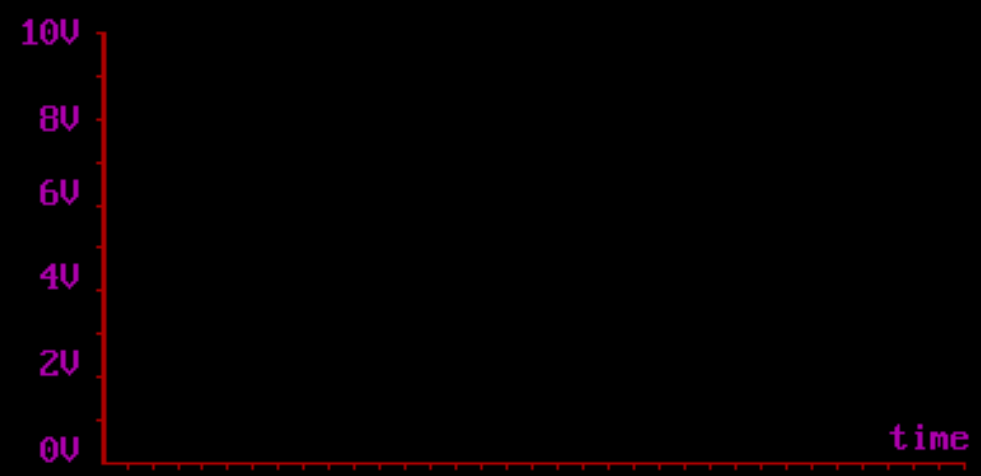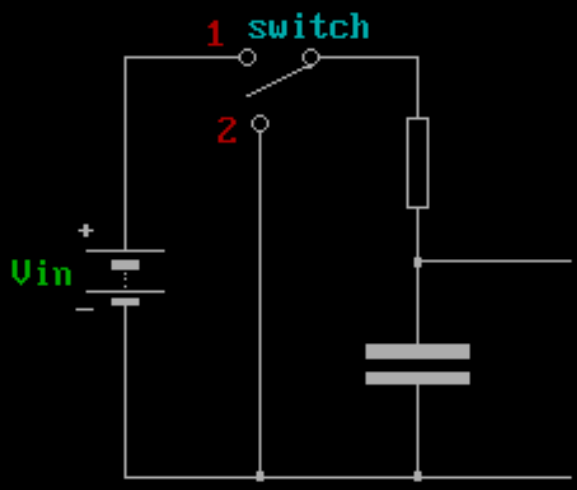


**A very brief flow of current occurs and then it stops.
The charge is stored. *So capacitors block DC current***


But what happens if AC current is used?

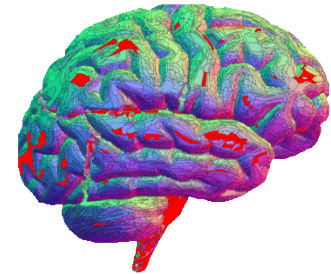
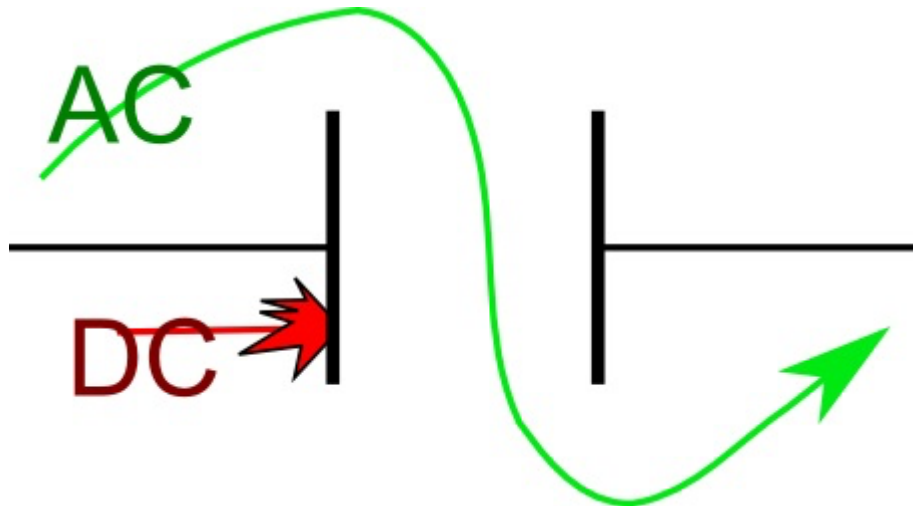


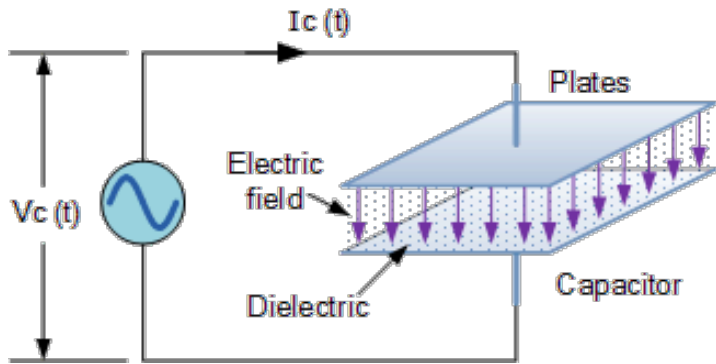**AC can pass depending on
frequency (f) (or
wavelength (λ))**



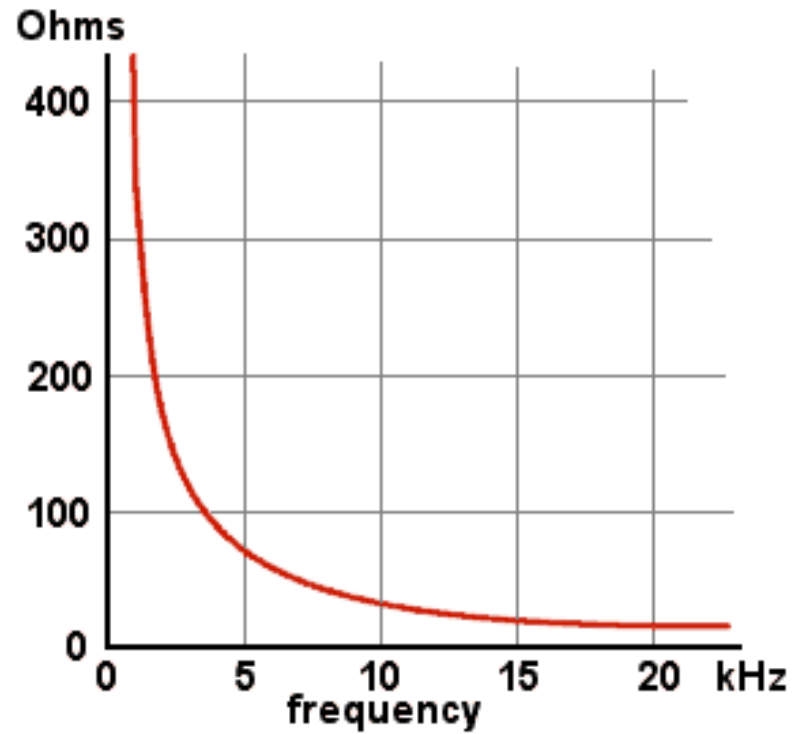
For “resistance” to AC current we use the term “reactance” symbol X and units Ω



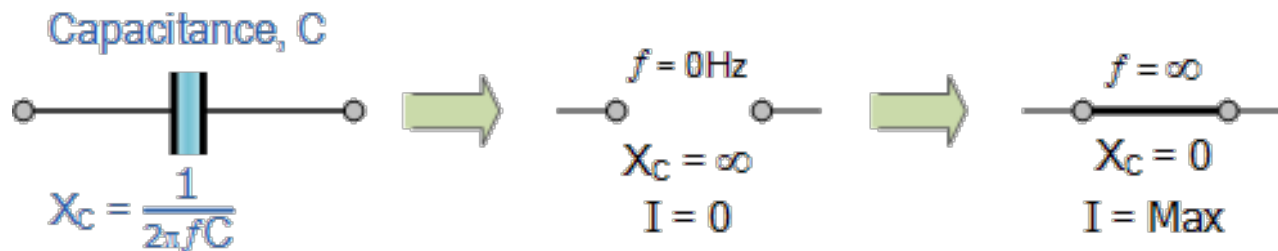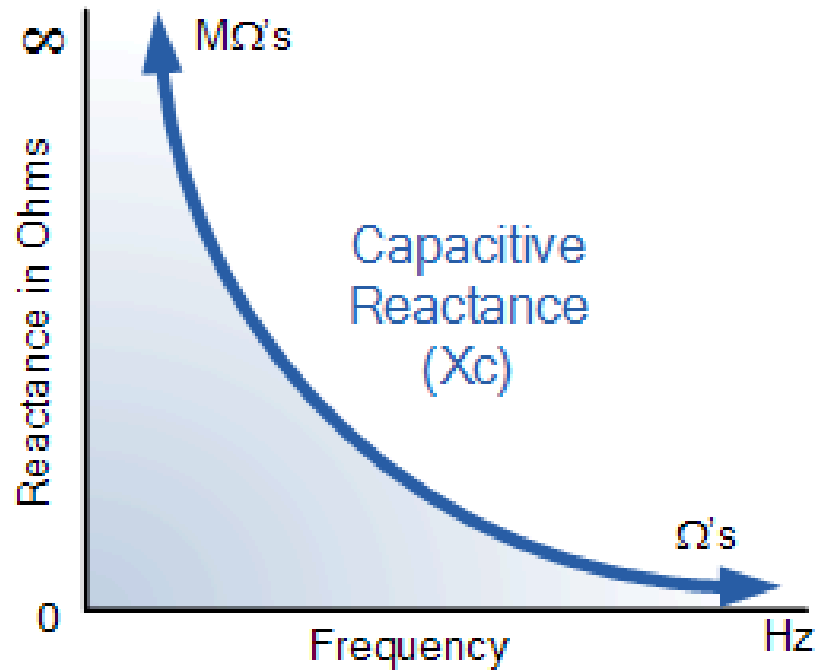

Series and Parallel calculations


Capacitors in Series

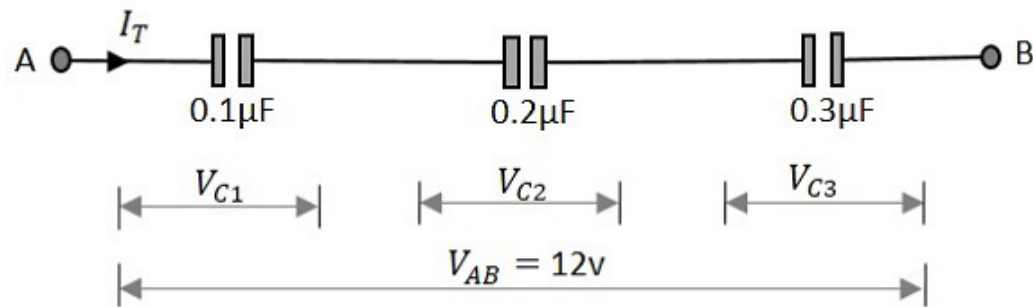

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad C_T = \frac{C_1 \times C_2}{C_1 + C_2}$$

$$V_T = V_{C1} + V_{C2} + V_{C3}$$


$$I = I_1 = I_2 = I_3$$

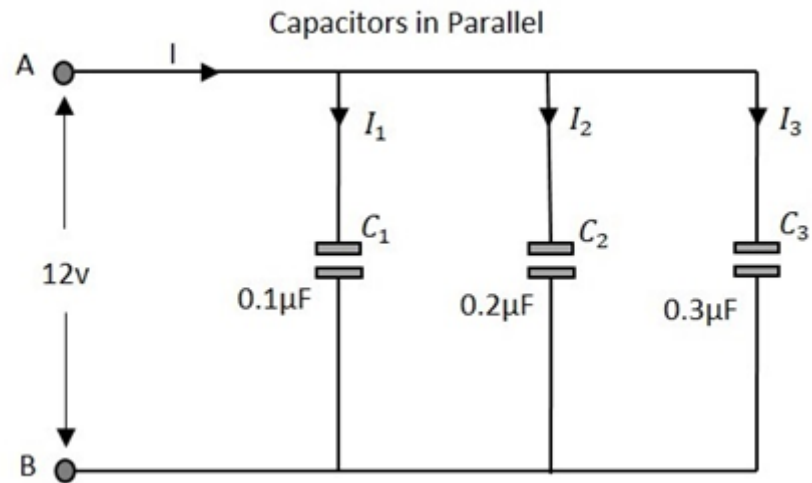


$$C_T = C_1 + C_2 + C_3$$

$$V_T = V_1 = V_2 = V_3$$


$$I_T = I_1 + I_2 + I_3$$

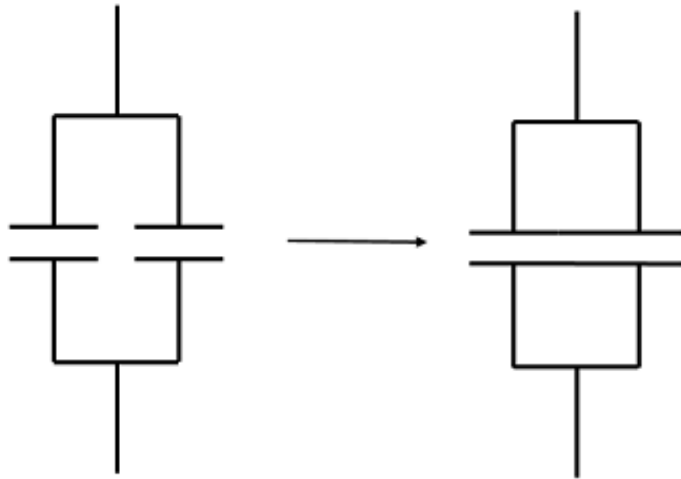

$$C_{\text{total}} = C_1 + C_2$$

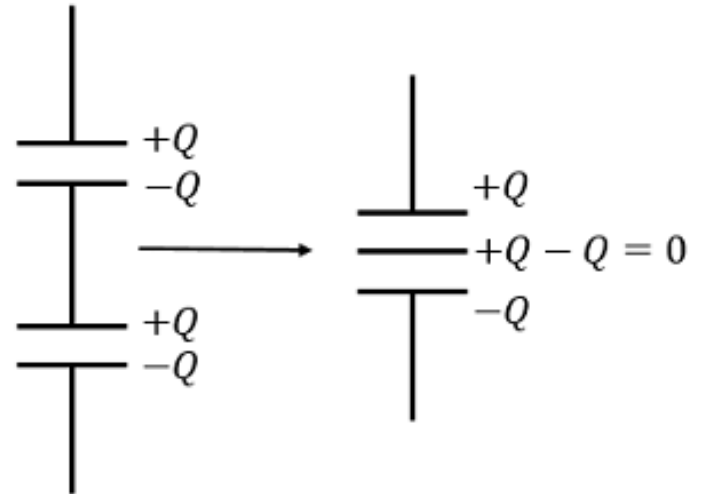

$$1/C_{\text{total}} = 1/C_1 + 1/C_2$$

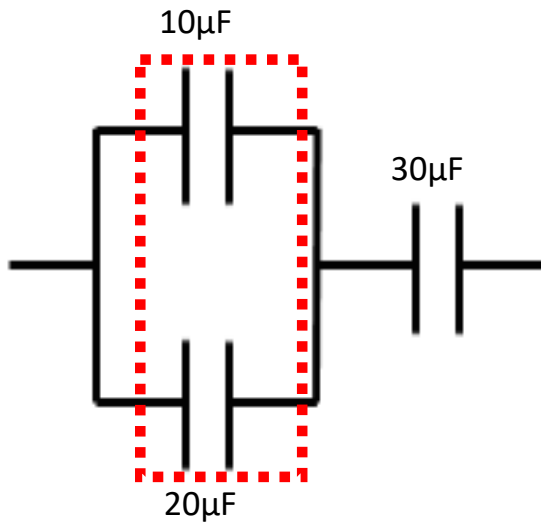

Parallel first:

$$C_1 = 10\mu\text{F} + 20\mu\text{F} = 30\mu\text{F}$$


Then series:

$$1/C_{\text{total}} = 1/C_1 + 1/C_2 = 1/30\mu\text{F} + 1/30\mu\text{F} = 2/30\mu\text{F}$$

$$C_{\text{total}} = 30\mu\text{F}/2 = 15\mu\text{F}$$

$$\text{Or } 30 \times 30 / 30 + 30 = 900 / 60 = 15$$

There are many types of capacitors

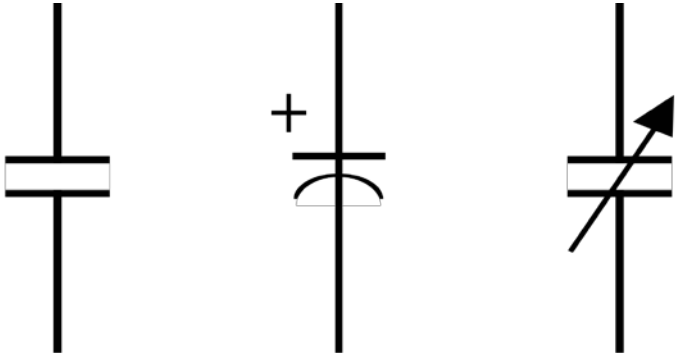

Fixed Capacitor Polarized Capacitor Variable Capacitor



Images of Glass Capacitors



Qili Electronic Material CO., LTD

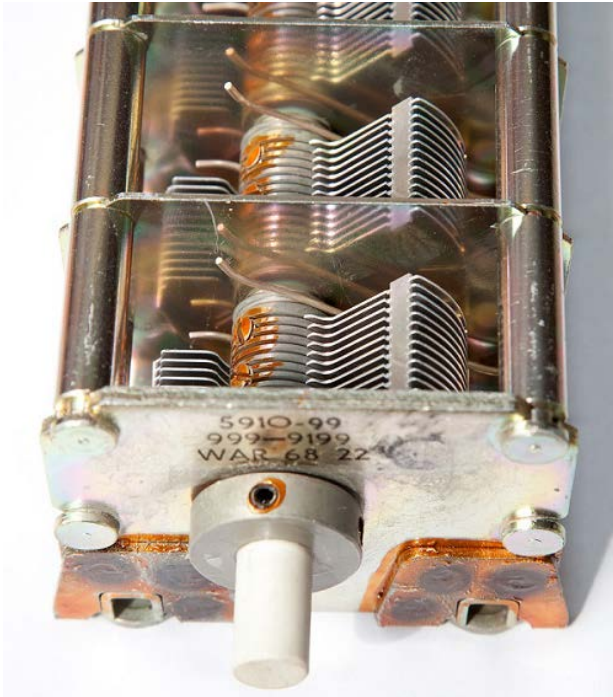


Image of a Trimmer Capacitor


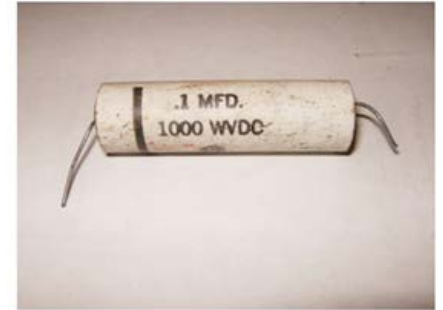



Image of a Paper Capacitor

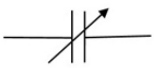

Images of different Ceramic Capacitors



Symbol of a variable capacitor

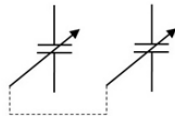



Symbol of a variable ganged capacitor



Capacitance depends on the area of the plates, the distance between the plates, and the dielectric in between them. The dielectric can include air, glass, polyethylene, mica, Teflon® etc.

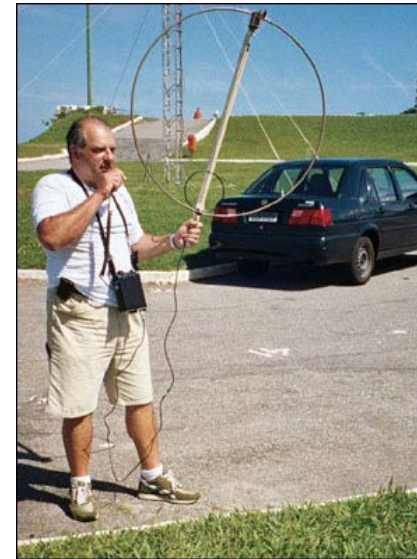Vacuum capacitors (fixed or variable) are designed to overcome high voltage breakdown. You will see them used in loop antennas.



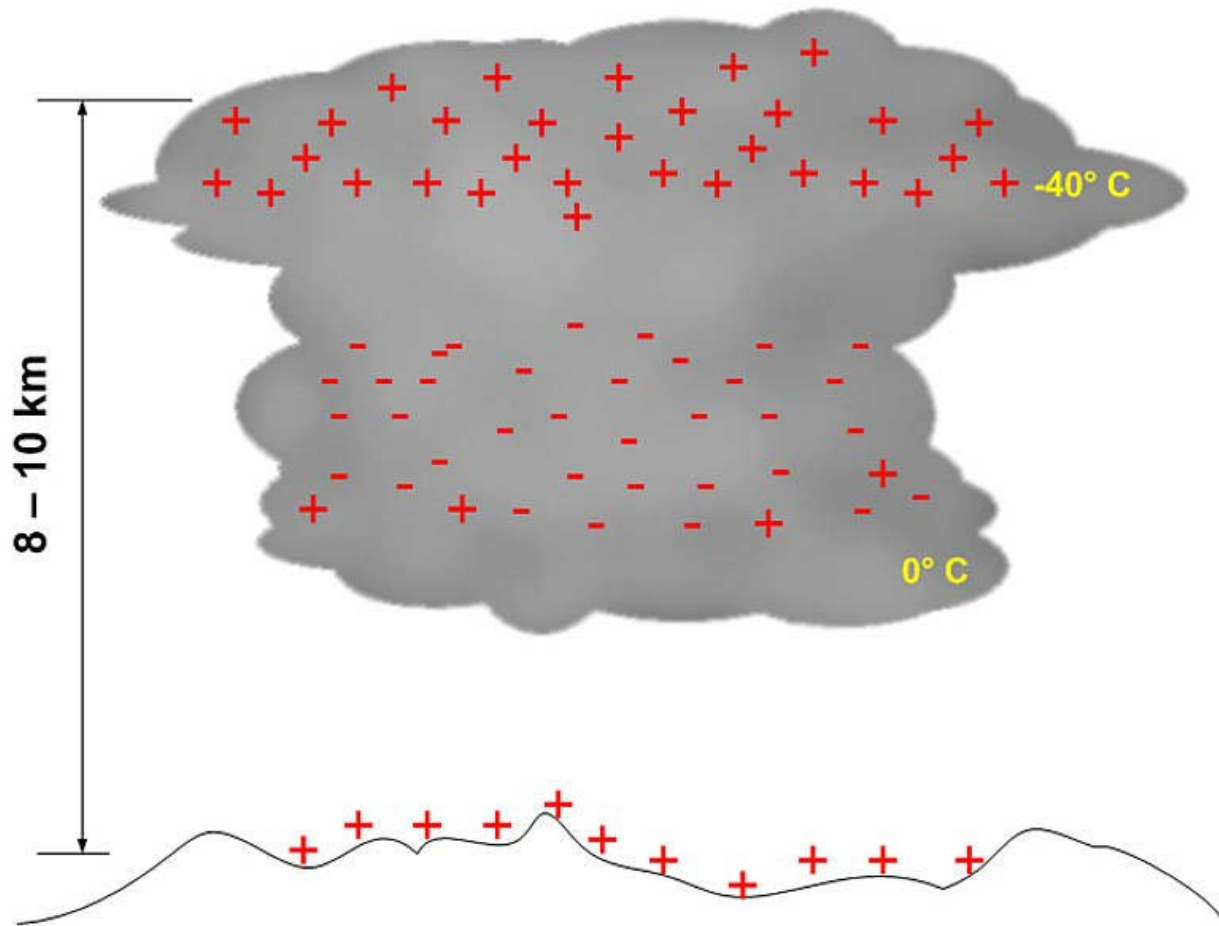





Can you see the positive upstroke?

Luminosity is very low because the current is very low

Photographs like this are very rare



How many volts?

B-005-9-6 What determines the capacitance of a capacitor?

- 1. The material between the plates, the area of one side of one plate, the number of plates and the spacing between the plates**
- 2. The material between the plates, the number of plates and the size of the wires connected to the plates**
- 3. The number of plates, the spacing between the plates and whether the dielectric material is N type or P type**
- 4. The material between the plates, the area of one plate, the number of plates and the material used for the protective coating**

B-005-9-3 If two equal-value capacitors are connected in series, what is their total capacitance?

- 1. Twice the value of one capacitor**
- 2. The same as the value of either capacitor**
- 3. The value of one capacitor times the value of the other**
- 4. Half the value of either capacitor**

B-005-9-9 Three 15 microfarad capacitors are wired in series. The total capacitance of this arrangement is:

- 1. 45 microfarads**
- 2. 12 microfarads**
- 3. 5 microfarads**
- 4. 18 microfarads**

B-005-9-7 If two equal-value capacitors are connected in parallel, what is their capacitance?

- 1. The same value of either capacitor**
- 2. The value of one capacitor times the value of the other**
- 3. Half the value of either capacitor**
- 4. Twice the value of either capacitor**


B-005-10-2 How does a capacitor react to AC?

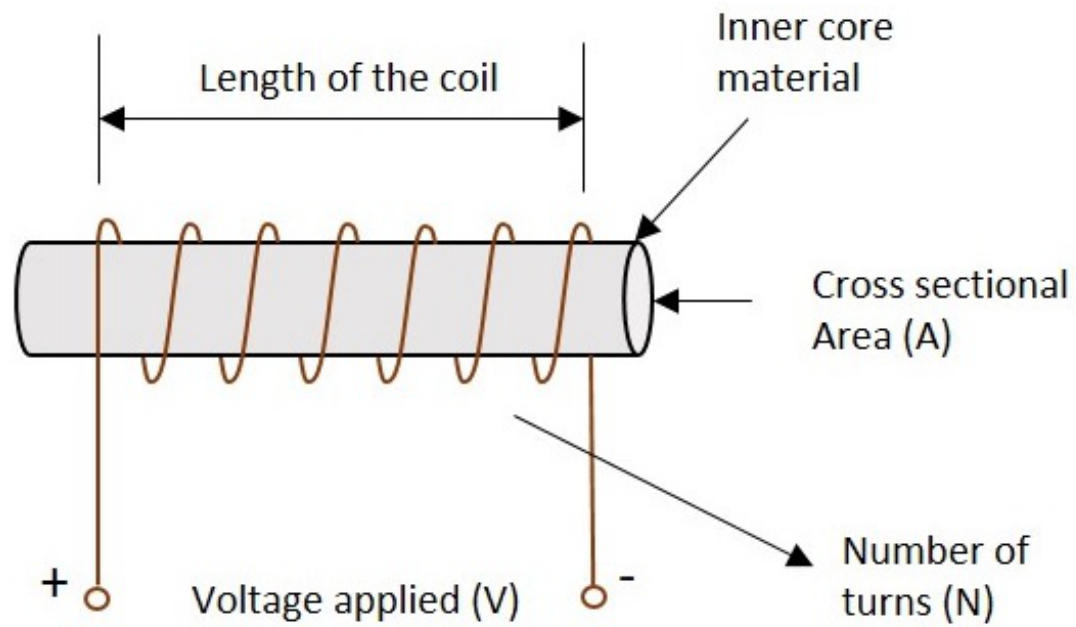
- 1. As the frequency of the applied AC increases, the reactance decreases**
- 2. As the frequency of the applied AC increases, the reactance increases**
- 3. As the amplitude of the applied AC increases, the reactance increases**
- 4. As the amplitude of the applied AC increases, the reactance decreases**

Inductance



The symbol for inductance is L and the units are Henrys (H)



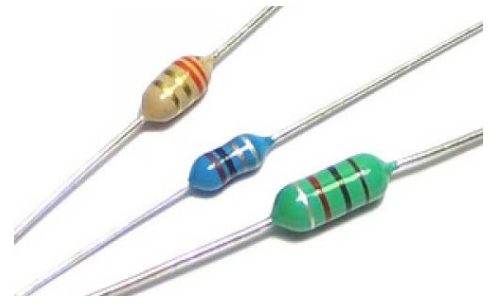


Core




Core wounded with wire



Inductors having different types of core

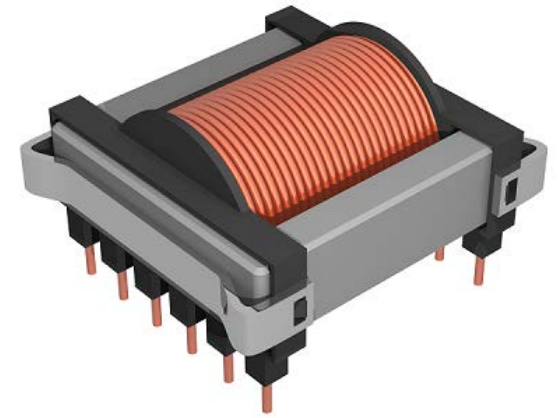

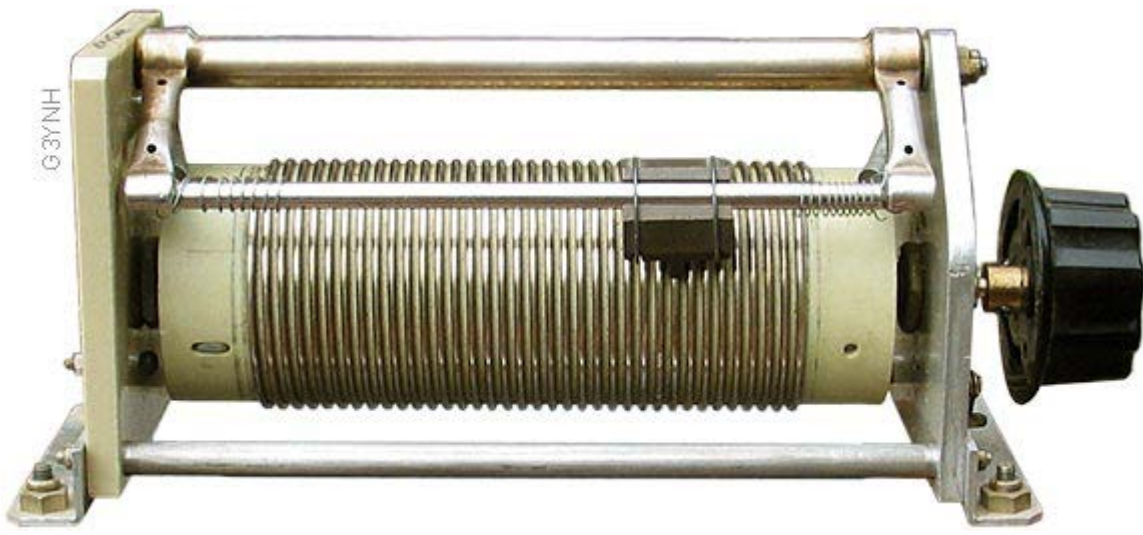



Air Core Inductor



Iron Core Inductor




Ferrite Core Inductor






Variable Core Inductor

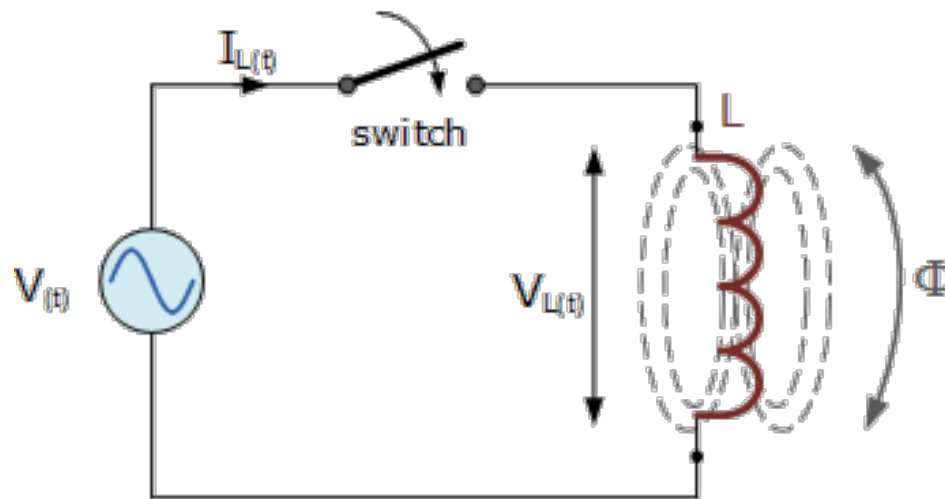The inductor is the other frequency-dependent device which we need to learn about.






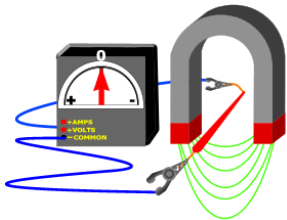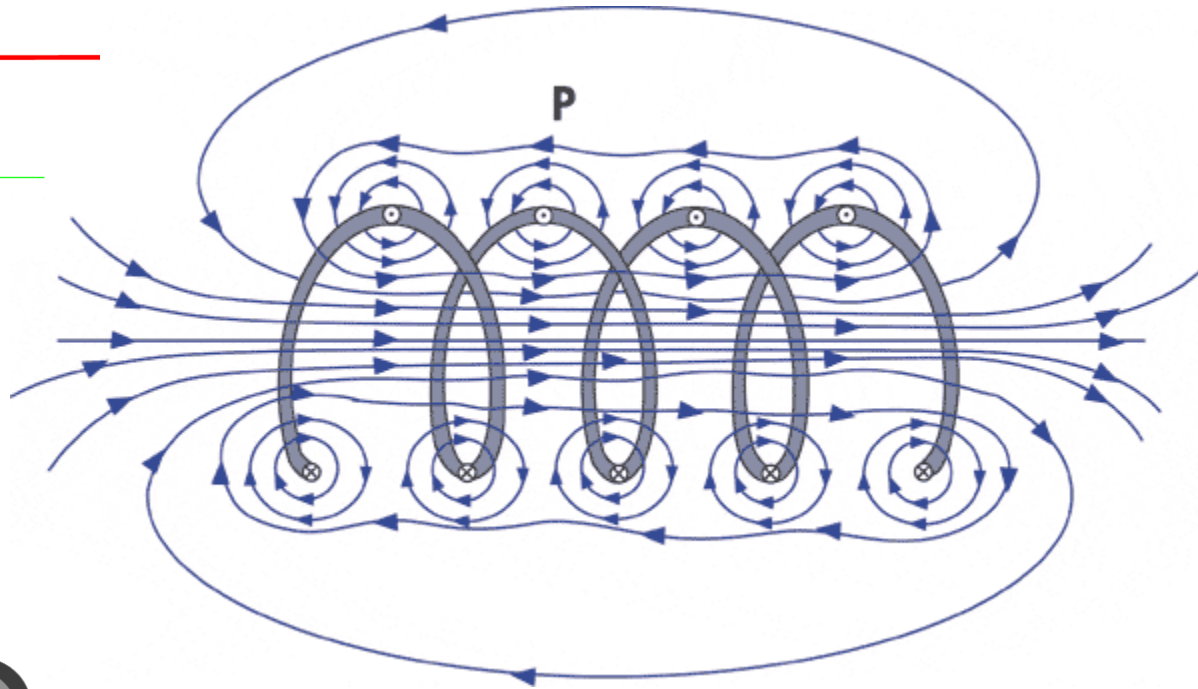
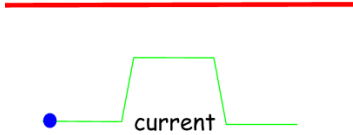
Coiled inductors work by electromagnetic induction





The changing magnetic field causes (induces) a current which is in the opposite direction. It therefore opposes current flow.

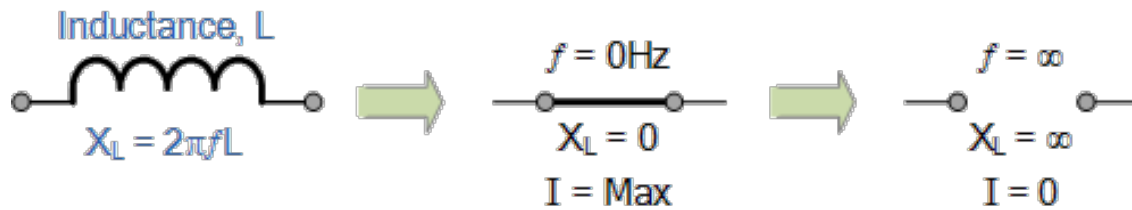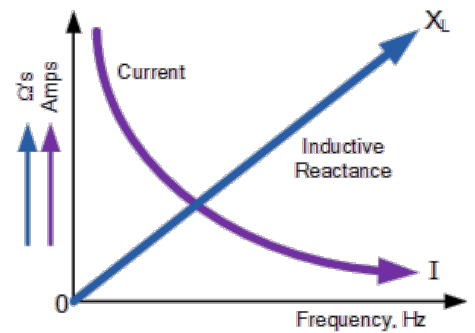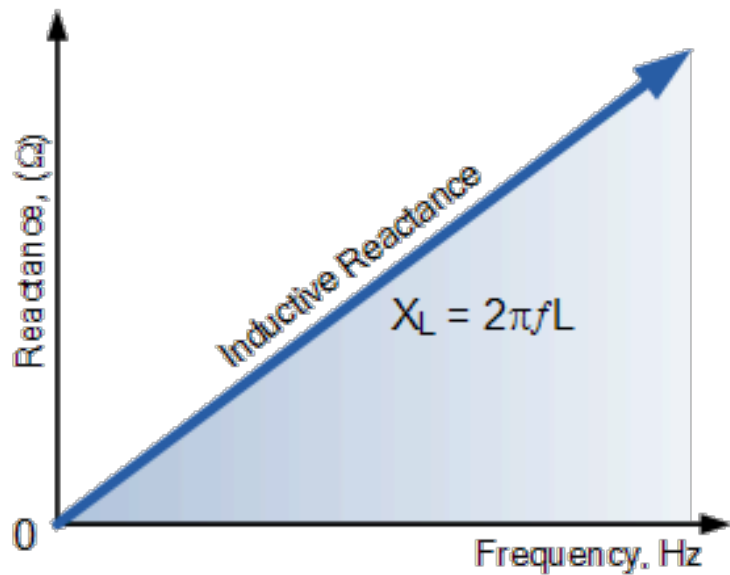It is called the self-inductance (or just inductance) of a coil.





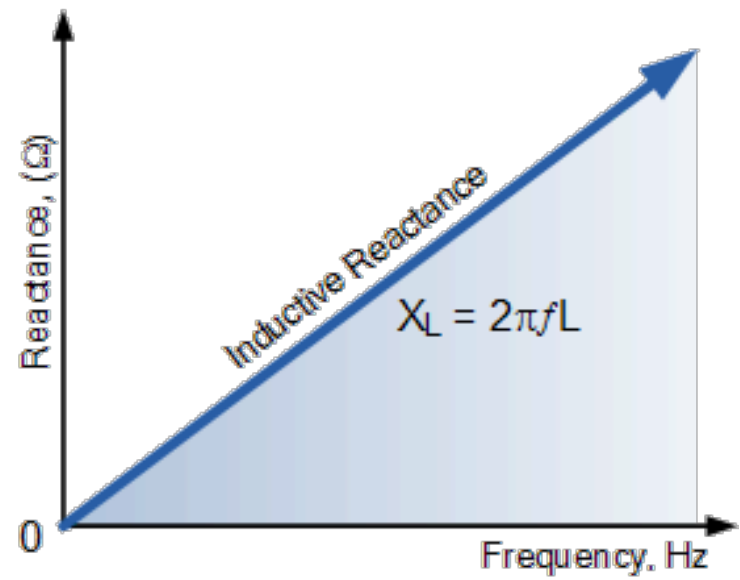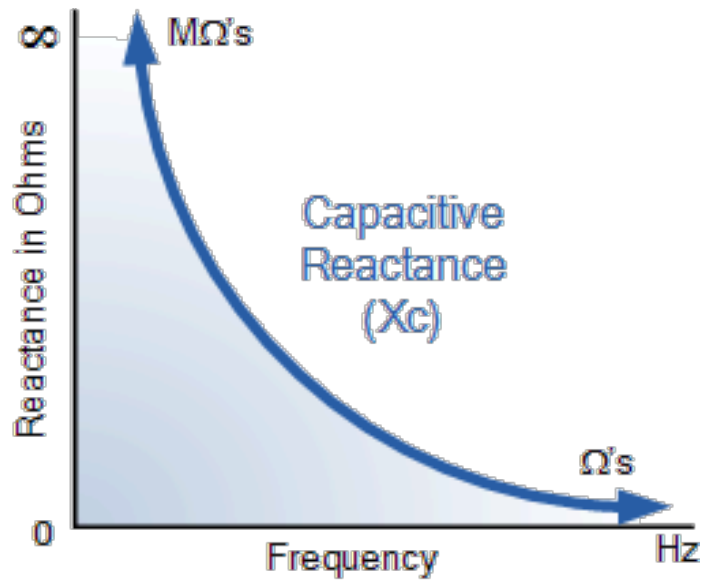

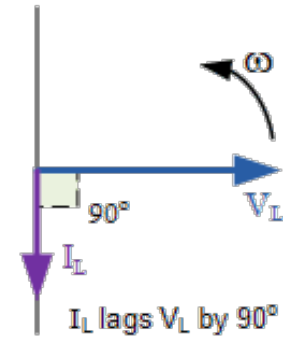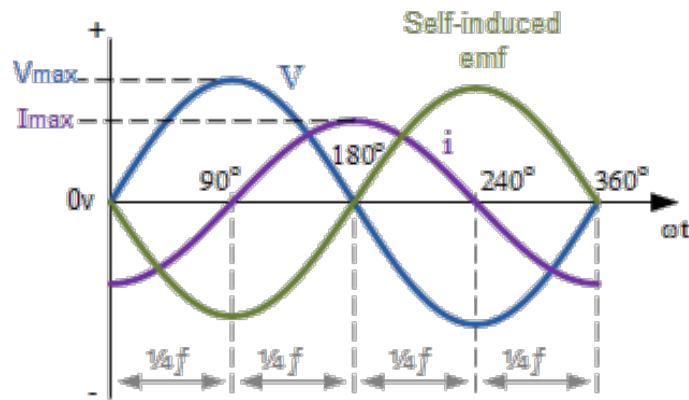Inductors “block” AC and pass DC. Capacitors “block” DC and pass AC
A better word is impede



ELI

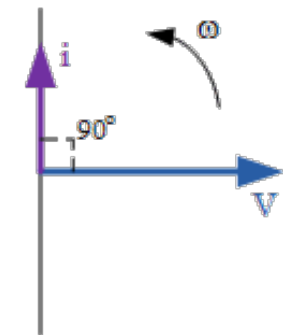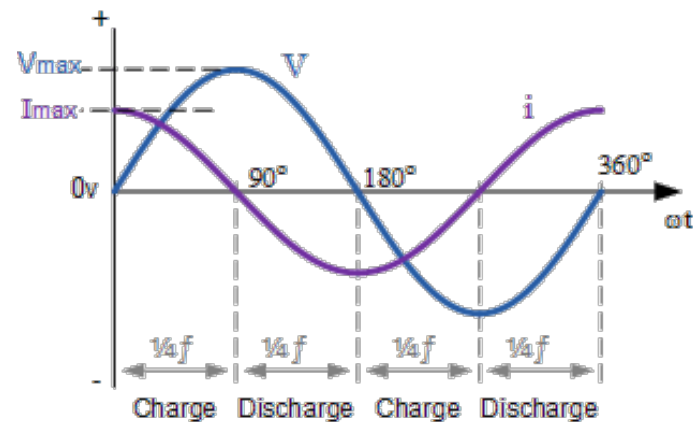

the


ICE

man

Series and Parallel calculations

similar to resistance


Inductors in Series

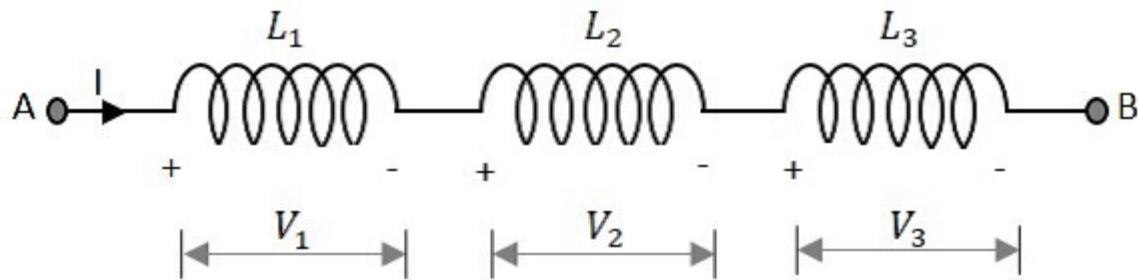

$$L_T = L_1 + L_2 + L_3$$

$$V = V_1 + V_2 + V_3$$

$$I = I_1 = I_2 = I_3$$

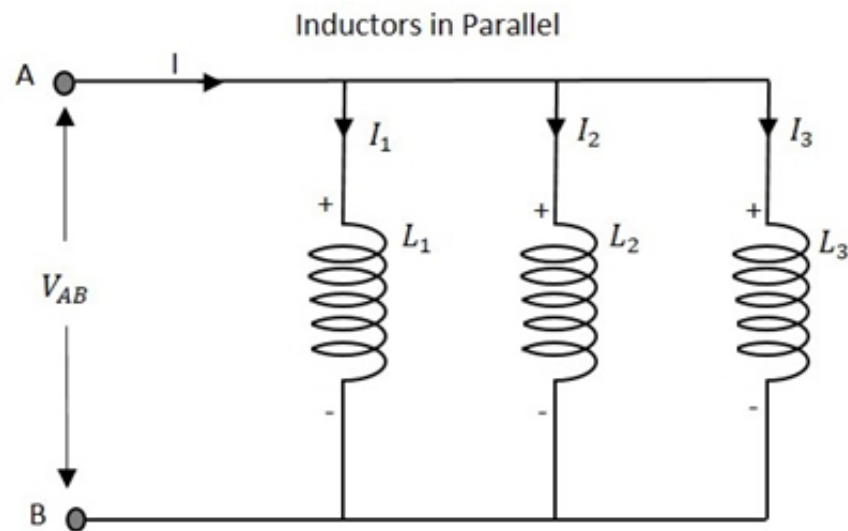

$$L_T = \frac{L_1 \times L_2}{L_1 + L_2}$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$V = V_1 = V_2 = V_3$$

$$I = I_1 + I_2 + I_3$$

B-005-9-1 If two equal-value inductors are connected in series, what is their total inductance?

- 1. Half the value of one inductor**
- 2. The same as the value of either inductor**
- 3. The value of one inductor times the value of the other**
- 4. Twice the value of one inductor**

B-005-9-5 What determines the inductance of a coil?

- 1. The core material, the number of turns used to wind the core and the frequency of the current through the coil**
- 2. The core diameter, the number of turns of wire used to wind the coil and the type of metal used for the wire**
- 3. The core material, the core diameter, the length of the coil and the number of turns of wire used to wind the coil**
- 4. The core material, the core diameter, the length of the coil and whether the coil is mounted horizontally or vertically**

B-005-10-10 What is the approximate inductive reactance of a 1.0 Henry choke coil used in a 60 hertz circuit?


1. 376 ohms

2. 3760 ohms

3. 188 ohms


4. 1888 ohms

Mutual Inductance

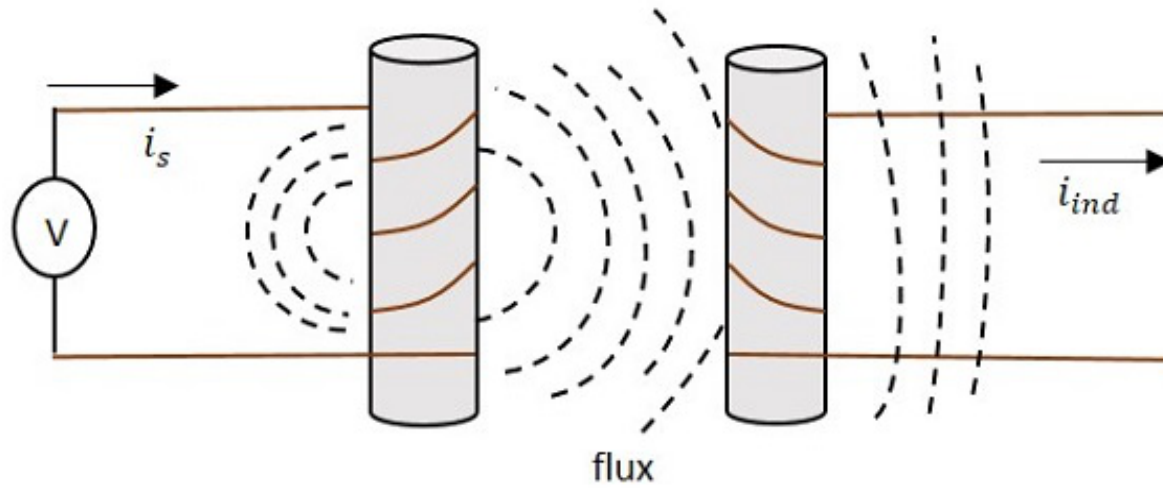


This is magnetic coupling





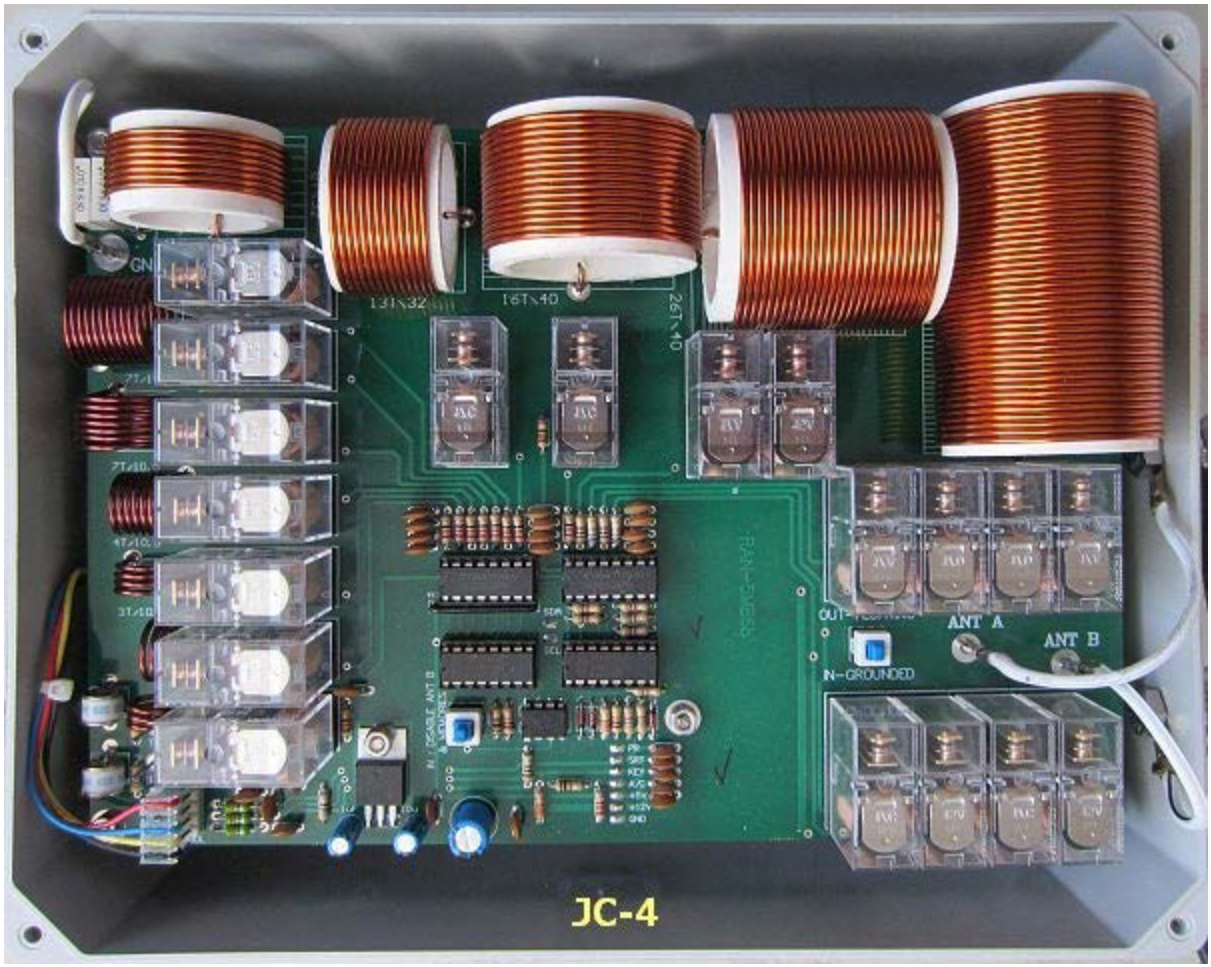


JC-4

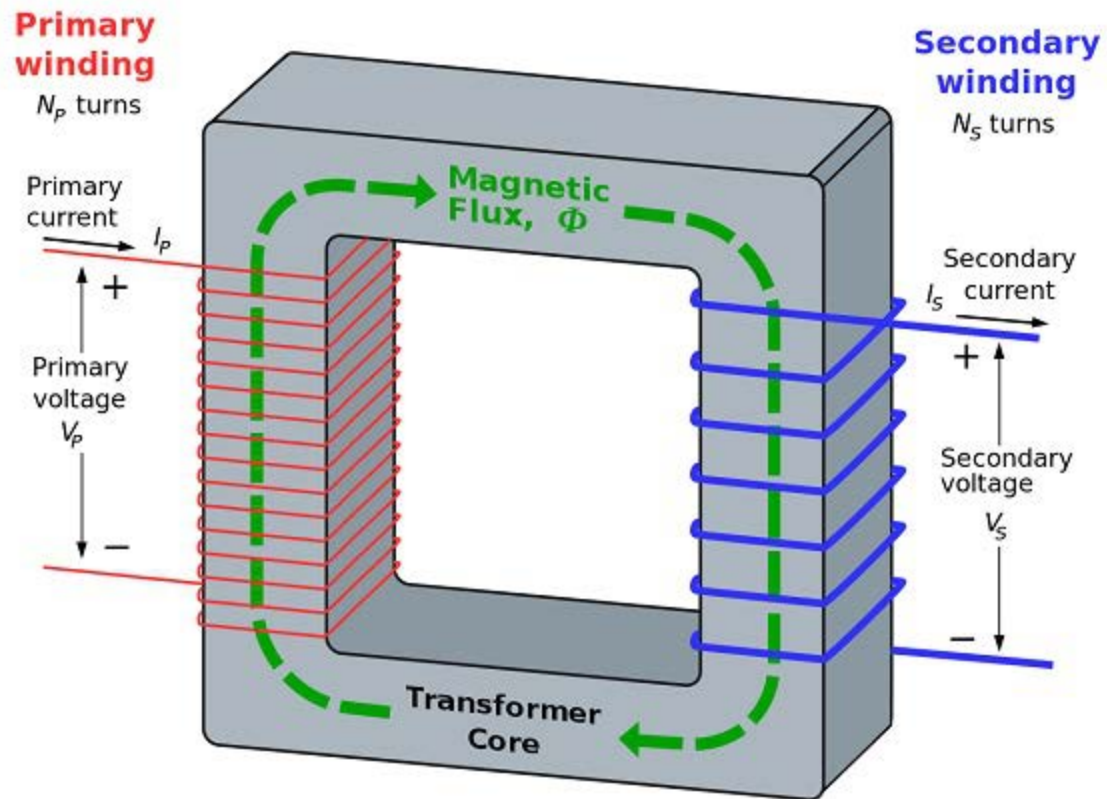

Current is induced in the secondary coil

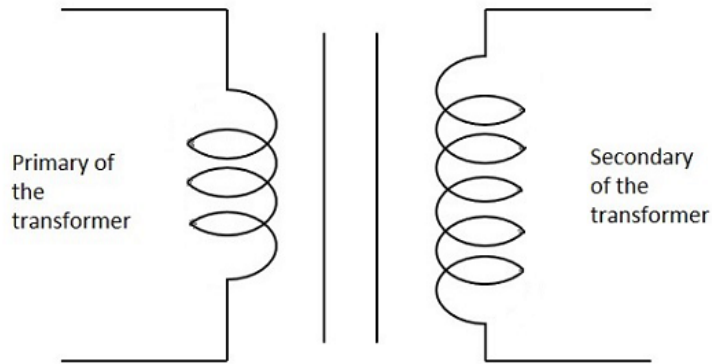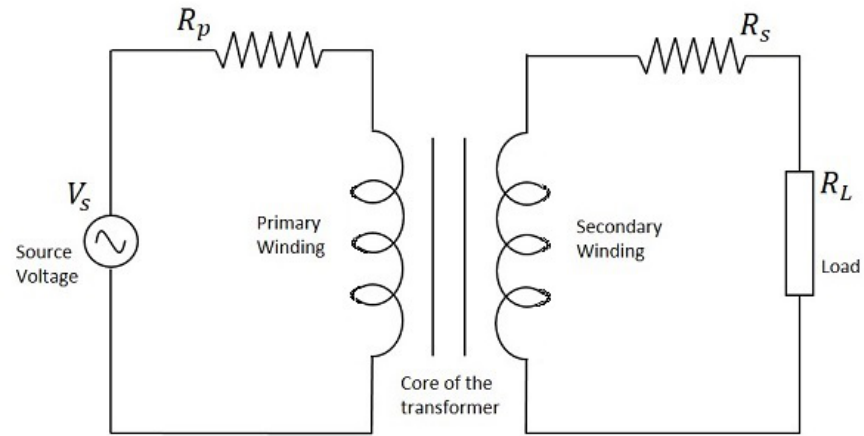

Step-up transformer

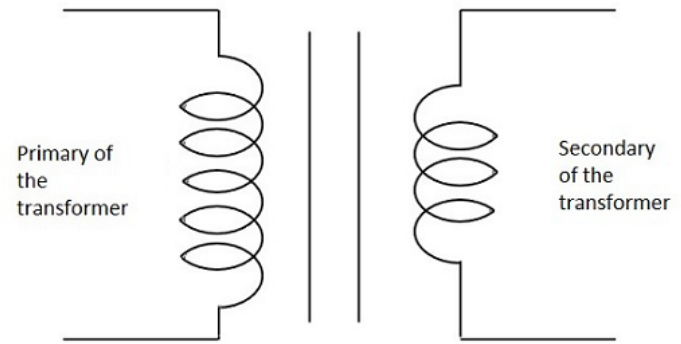

Step-down transformer

$$\frac{E_S}{E_P} = \frac{N_S}{N_P} \quad \text{Eqn 4-3}$$


$$E_P = 150 \text{ VAC}$$

$$N_P = 120 \text{ turns}$$

$$\frac{N_S}{N_P} = 5:2$$

$$N_S = \frac{5 \times 120}{2} = 300 \text{ turns}$$
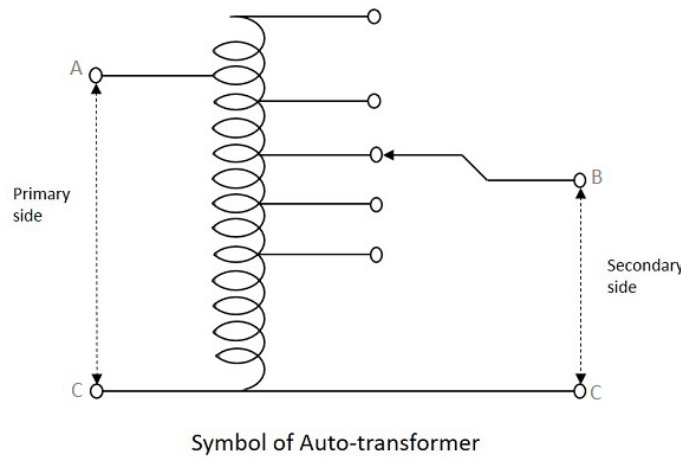
$$E_S = \frac{300 \times 150}{120} = 375 \text{ V}$$



Auto-transformers do not isolate



B-005-11-4 In a mains power transformer, the primary winding has 250 turns, and the secondary has 500. If the input voltage is 110 volts, the likely secondary voltage is:

- 1. 440 V**
- 2. 220 V**
- 3. 560 V**
- 4. 24 V**

B-005-11-2 A transformer operates a 6.3 volt 2 ampere light bulb from its secondary winding. The power consumed by the primary winding is approximately:


- 1. 13 watts**
- 2. 6 watts**
- 3. 8 watts**
- 4. 3 watts**

B-005-10-1 How does a coil react to AC?

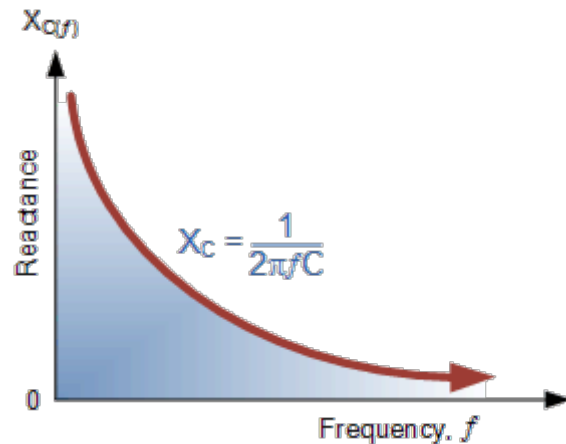
- 1. As the amplitude of the applied AC increases, the reactance decreases**
- 2. As the amplitude of the applied AC increases, the reactance increases**
- 3. As the frequency of the applied AC increases, the reactance increases**
- 4. As the frequency of the applied AC increases, the reactance decreases**

Impedance

We know about reactance now. Circuits can have reactance and resistance



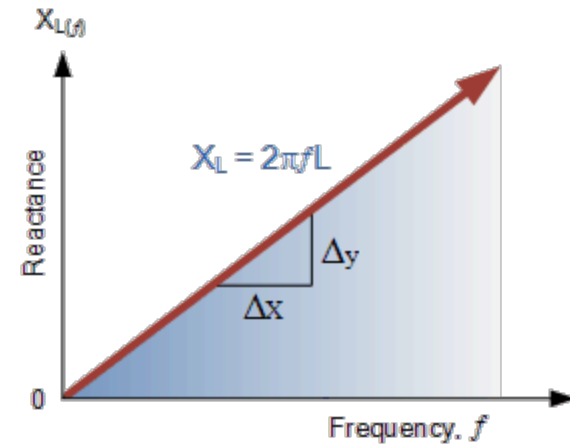
$$X_C = \frac{1}{2\pi fC} \quad \text{Eqn 4-7}$$



$$X_L = 2\pi fL \quad \text{Eqn 4-6}$$

Impedance Z (measured in Ω) is the sum of reactance and resistance
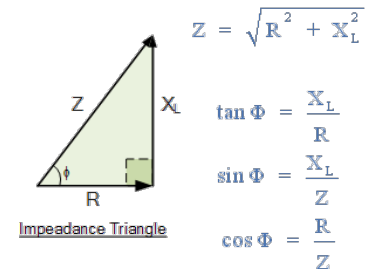
$$Z = \sqrt{R^2 + X^2} \quad \text{Eqn 4-8}$$




Matching impedances is an important concept in radio. The output of a transmitter should have the same impedance as the feed line and antenna it is connected to.



Hams spend a lot of time adjusting the impedance of their antennas so that the maximum power transfer from the transmitter can happen.

Resonance




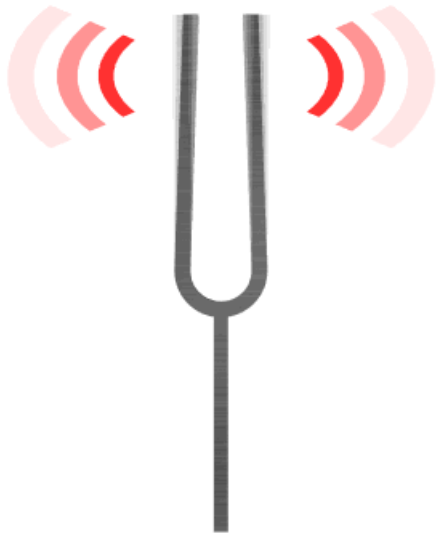



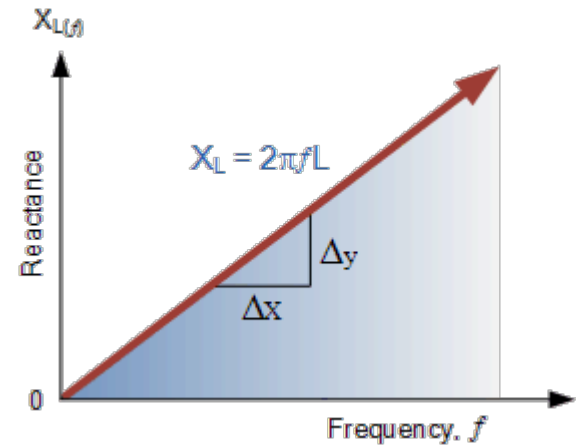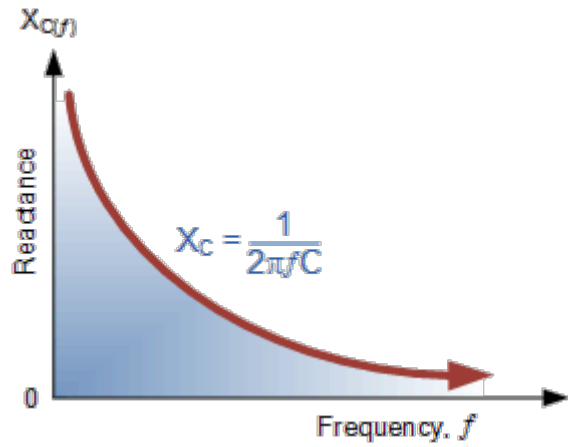


At some frequency X_C will equal X_L

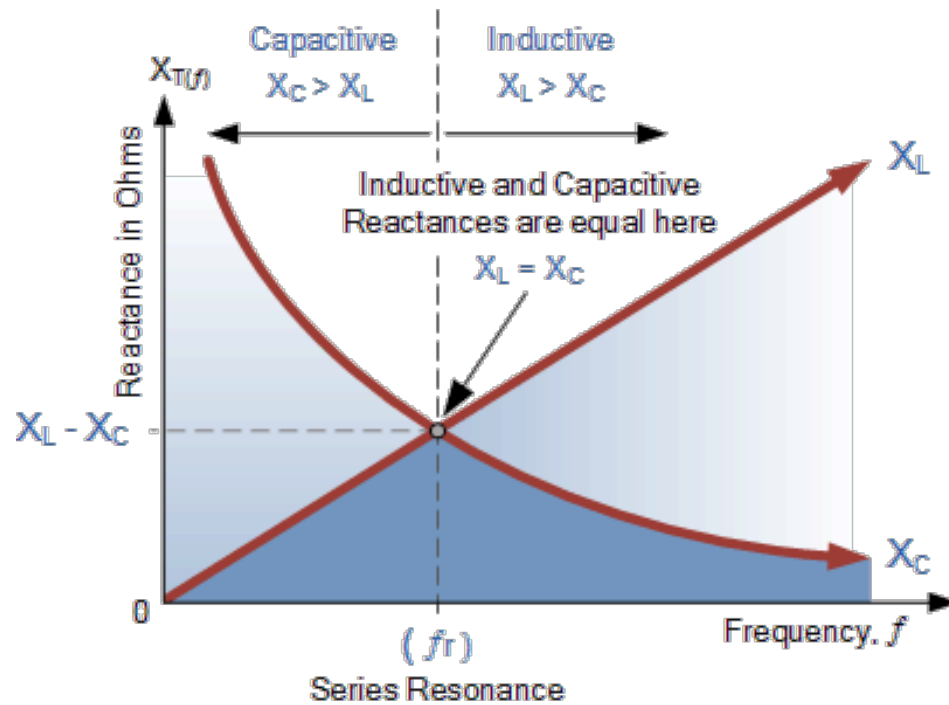

When $X_c = X_L$ the reactances cancel leaving only resistance

This is an example of a series resonant circuit *aka a tuned circuit*


Acceptor circuit

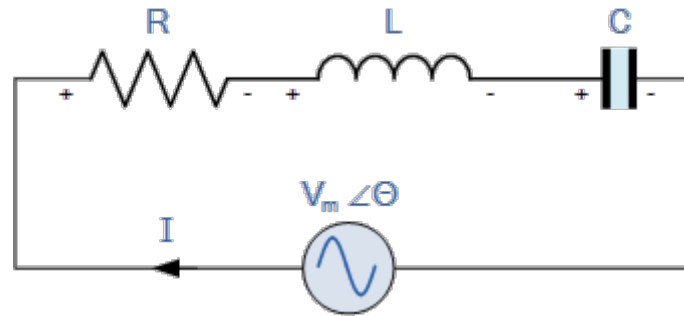



Frequency selection
Band pass filter



$$f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{Eqn 4-11}$$

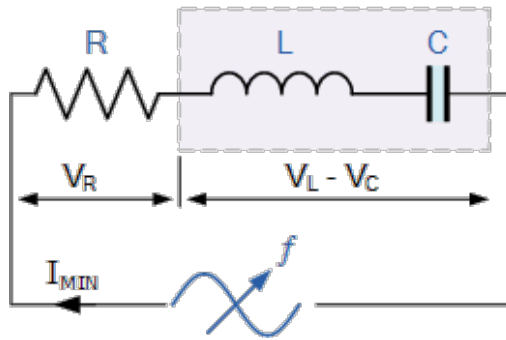Either side of resonance
the voltage drop = $V_L - V_C$



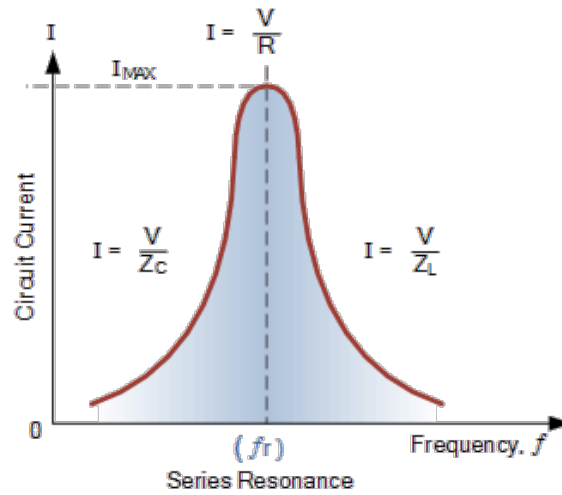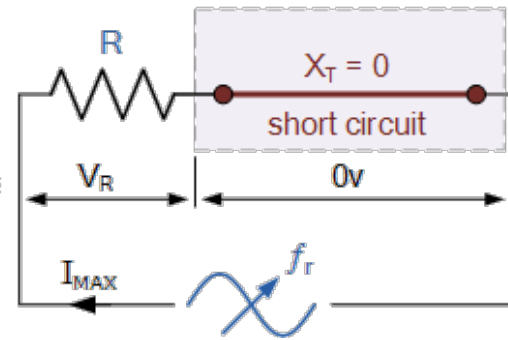At resonance the voltage
drop equals zero




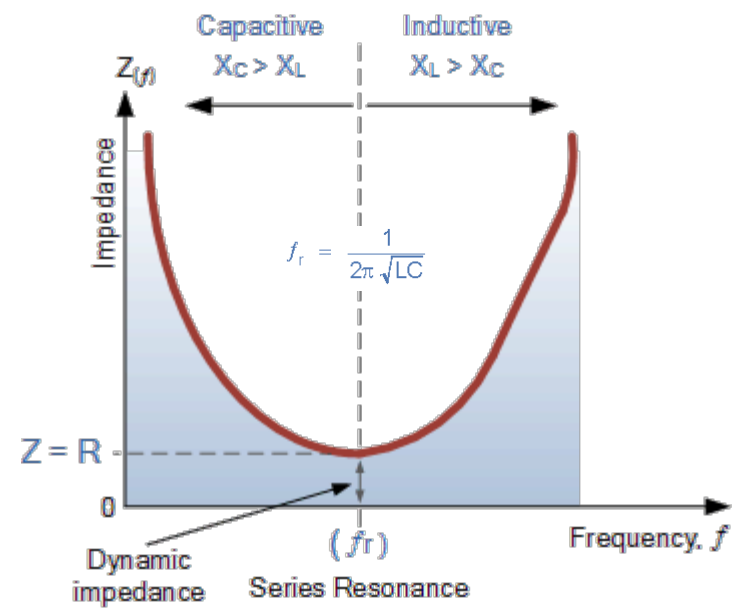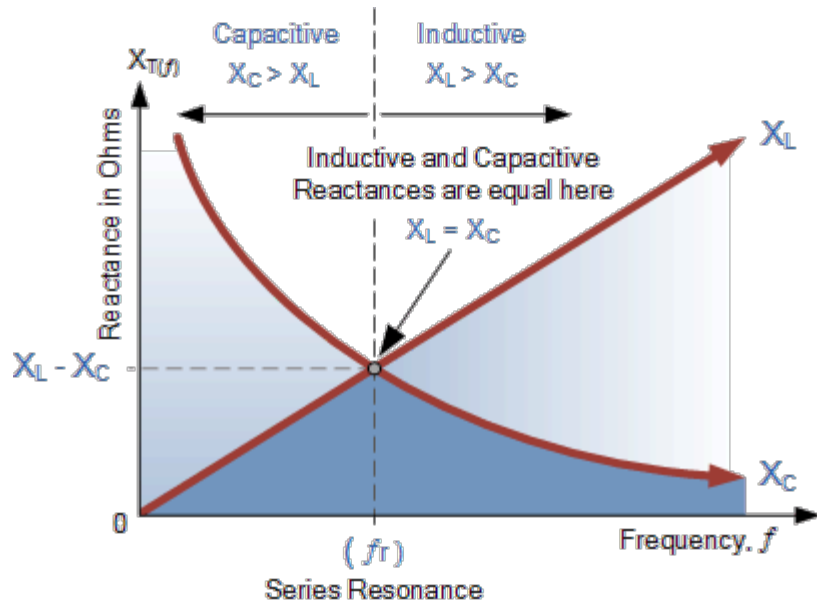

This is an example of a parallel resonant circuit

also a tuned circuit


Rejector circuit


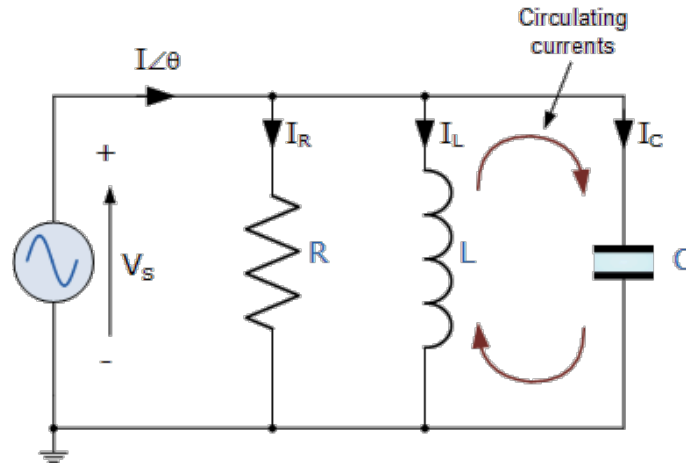


Band stop filter
IF trap
“Tank” circuit in an oscillator


Either side of resonance the current = $I_L - I_C$

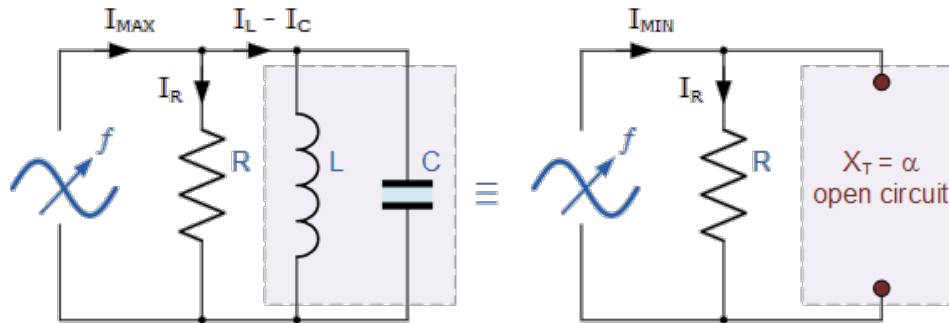At resonance the reactive current is zero





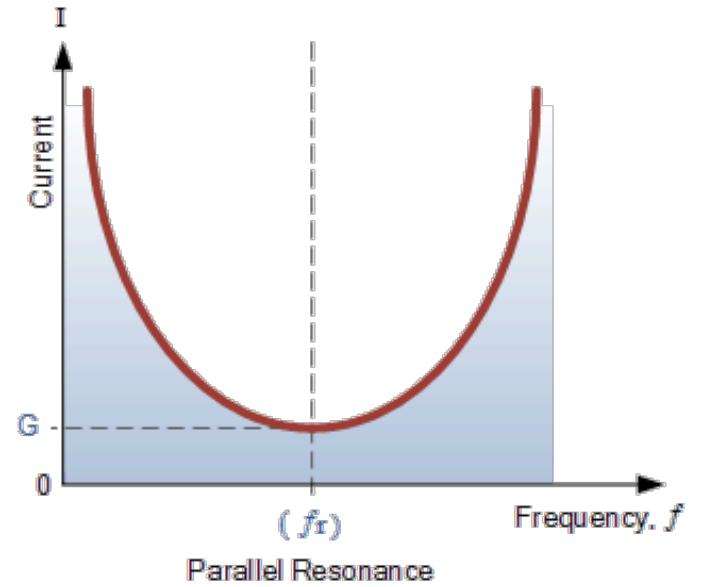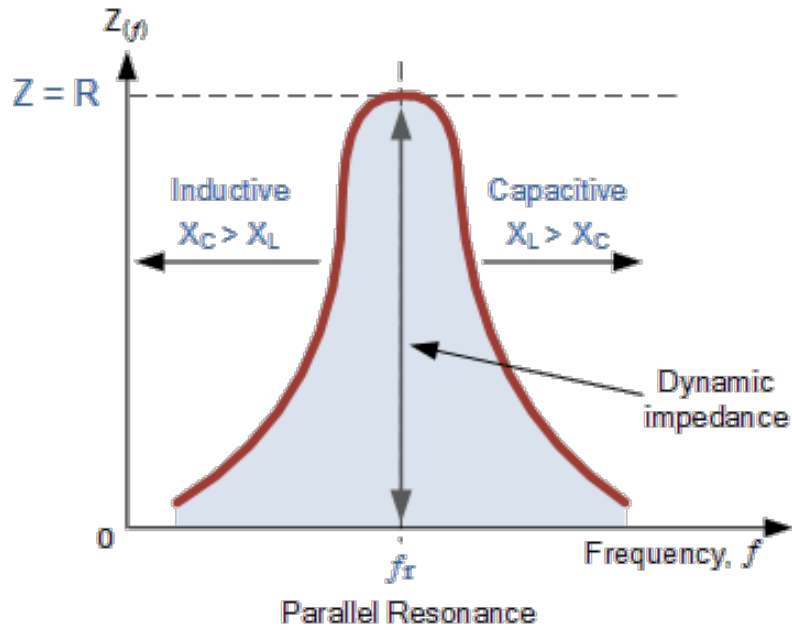


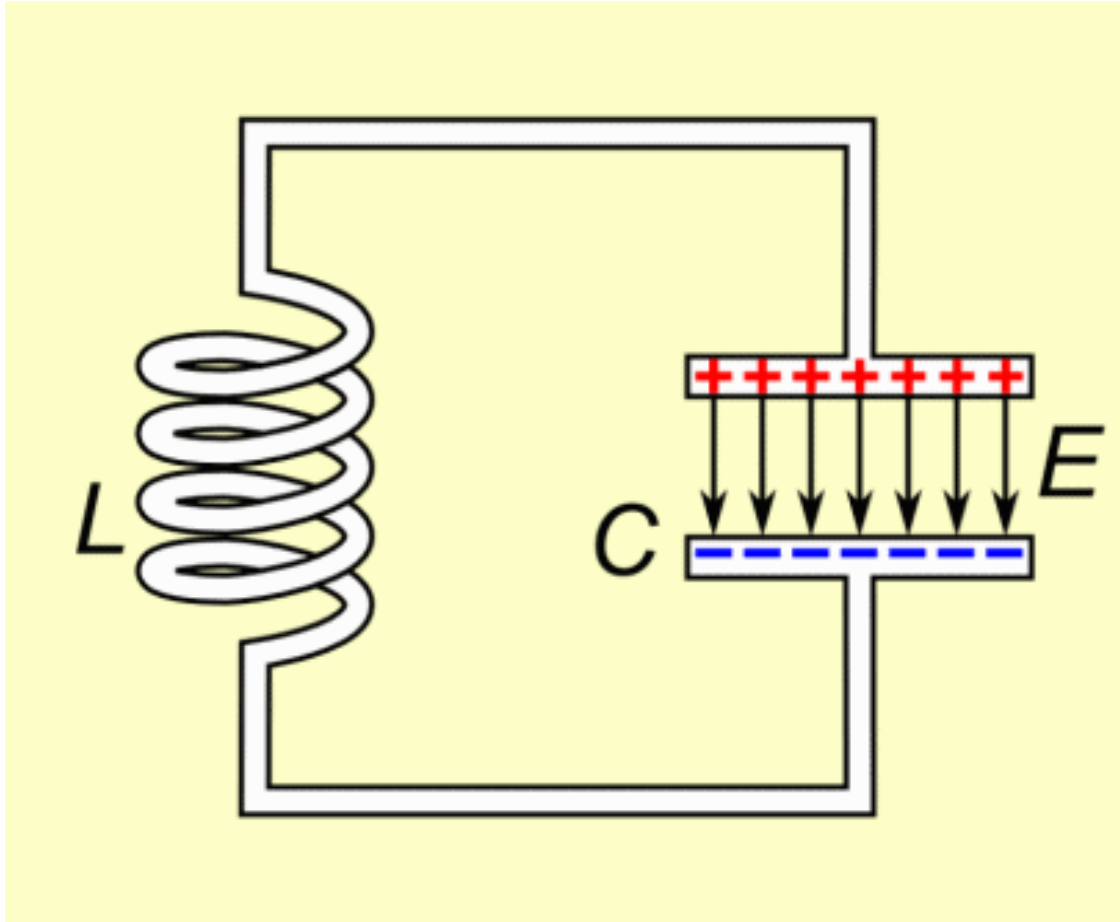
$$f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{Eqn 4-11}$$





Tank circuit

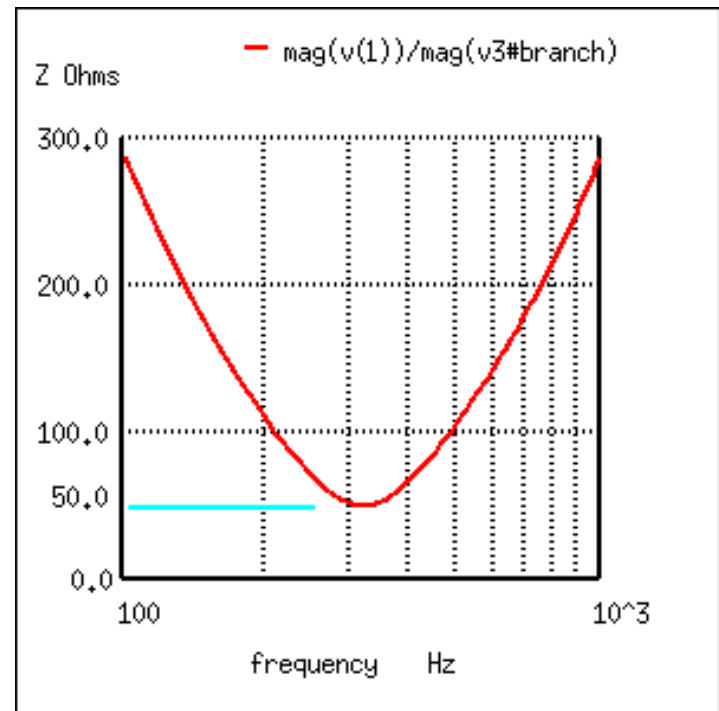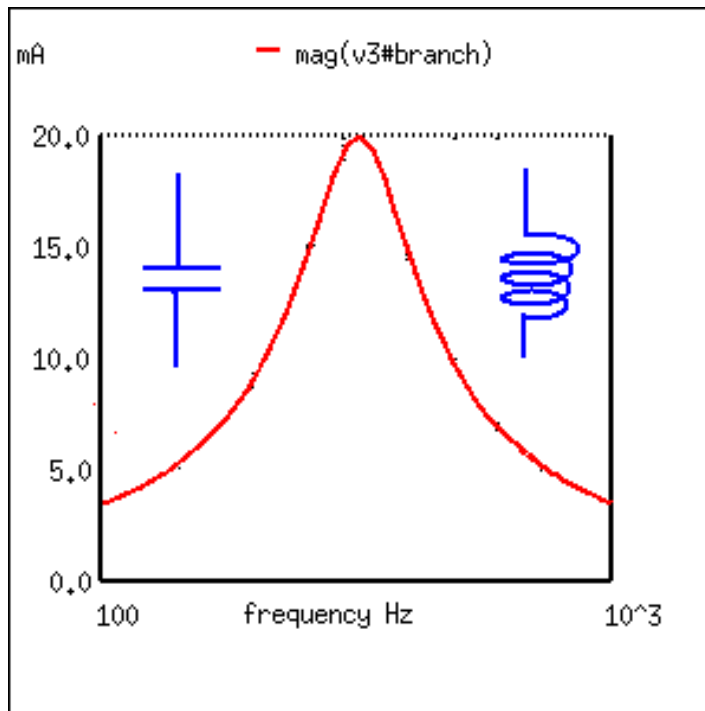


Series resonance

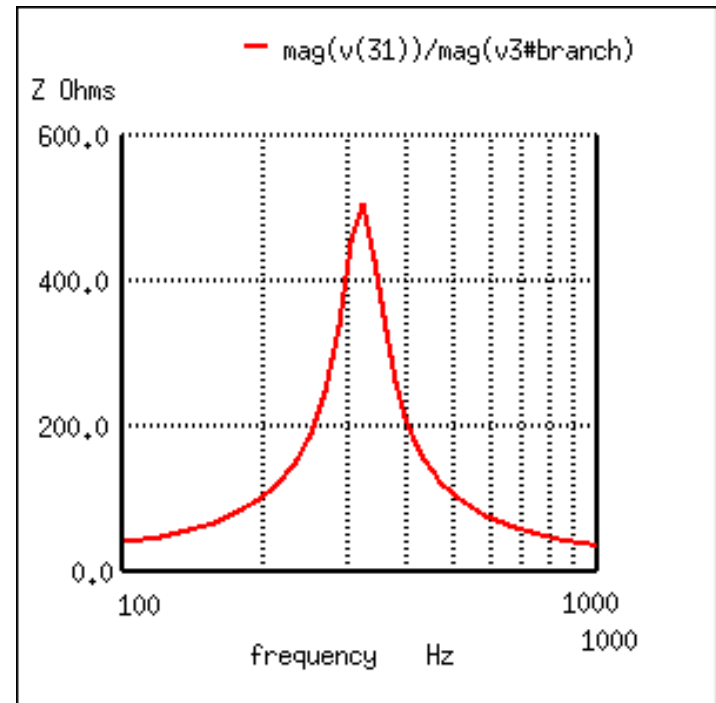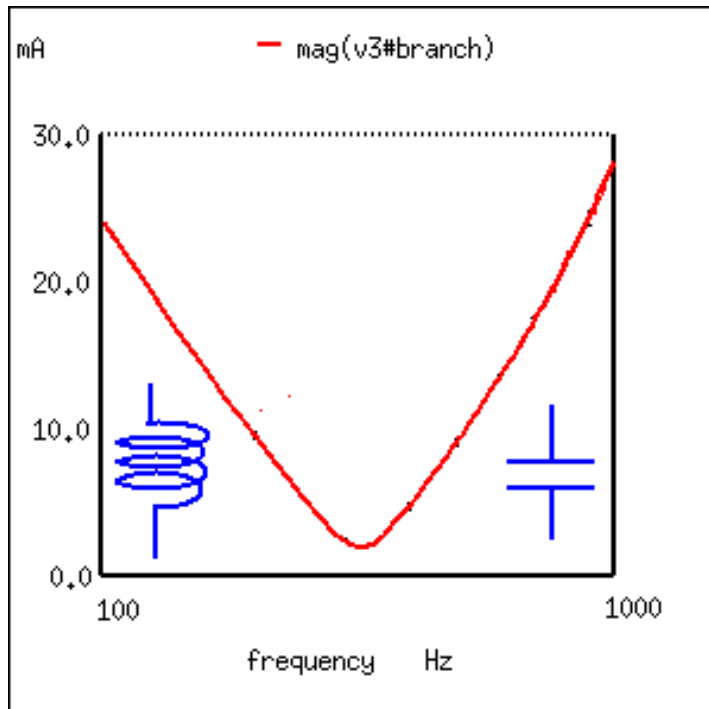



Parallel resonance

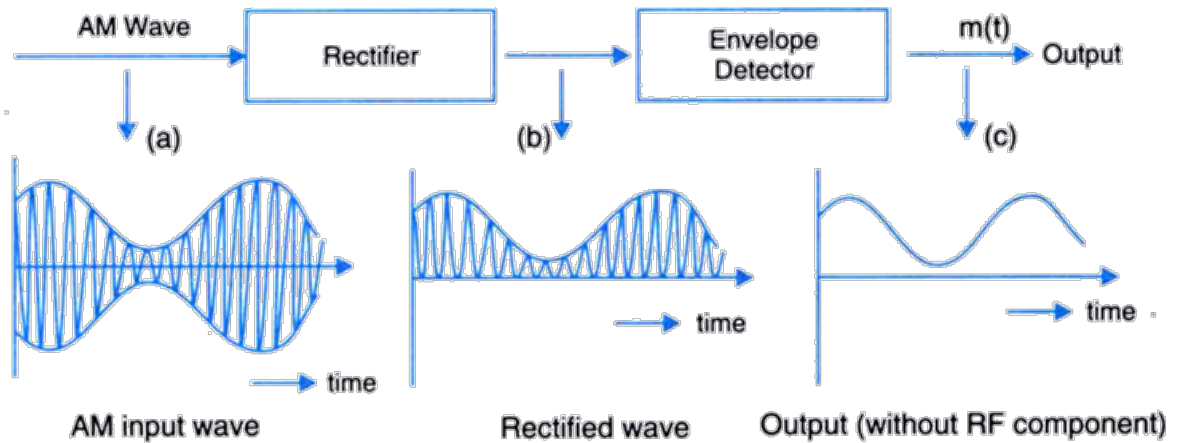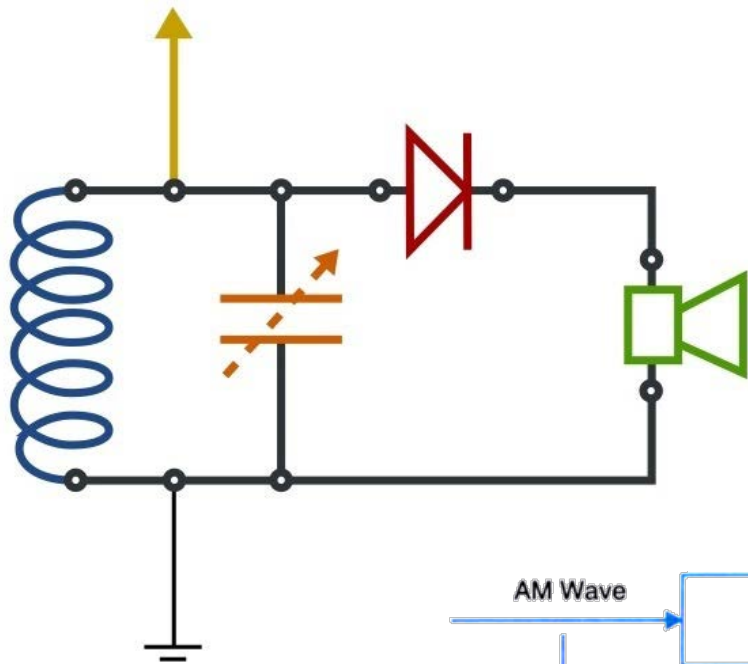


This is a crystal radio

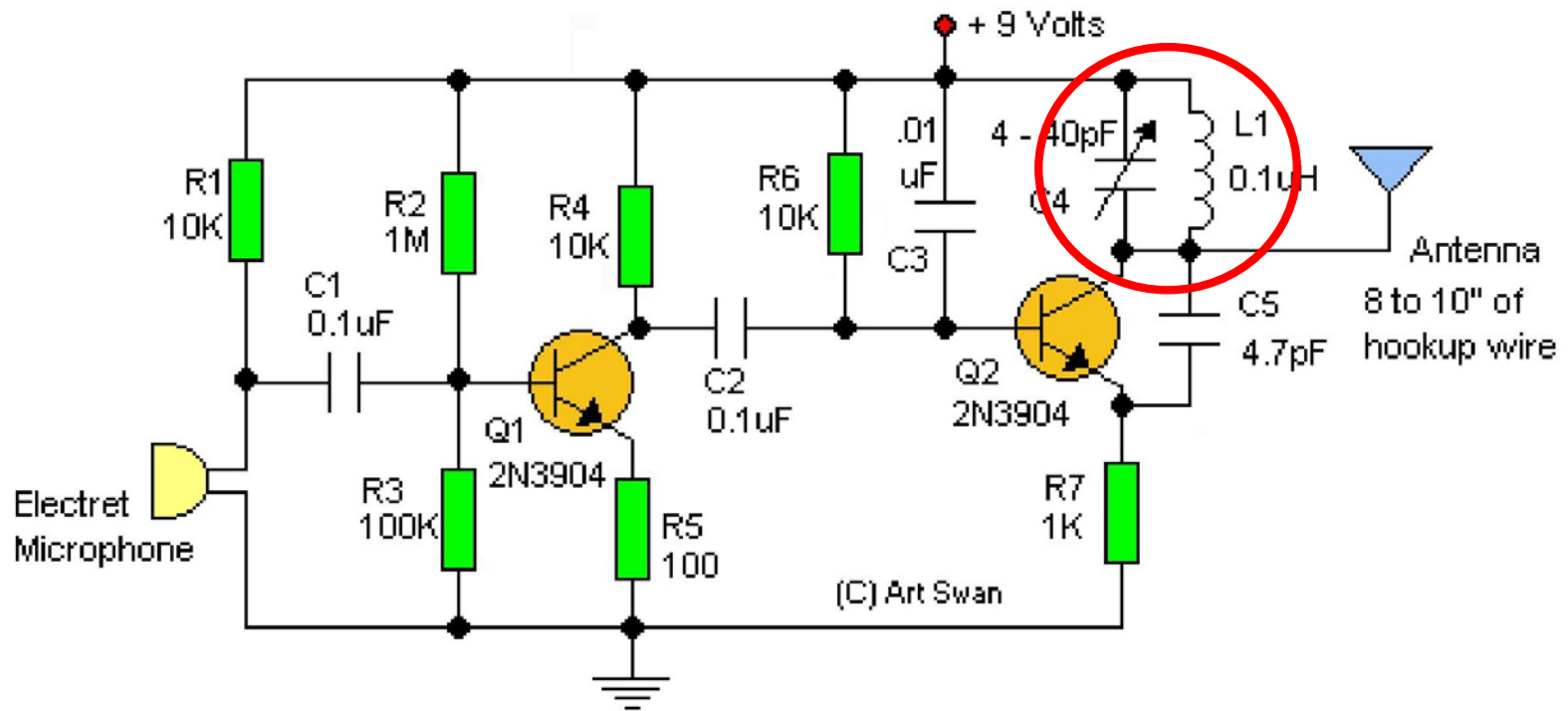



Q

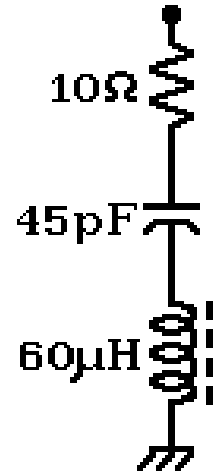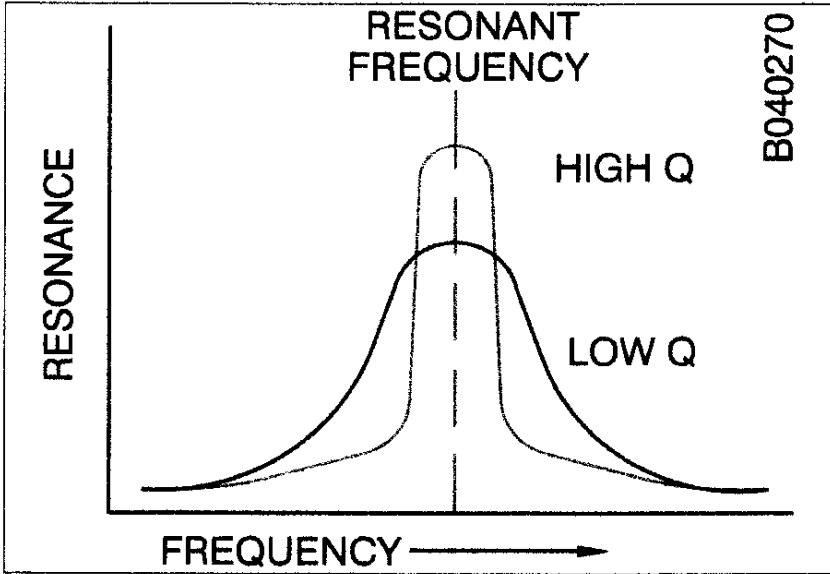
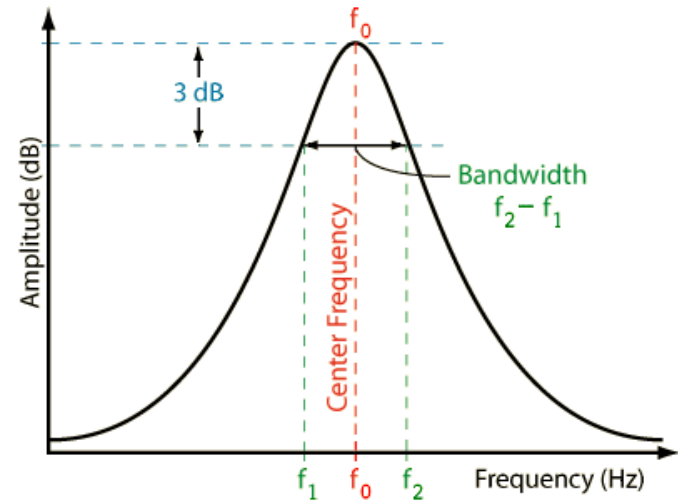
$$BW = \frac{F_R}{Q} = \frac{3.06^6 \text{ Hz}}{115.5} = 26.52 \text{ KHz}$$



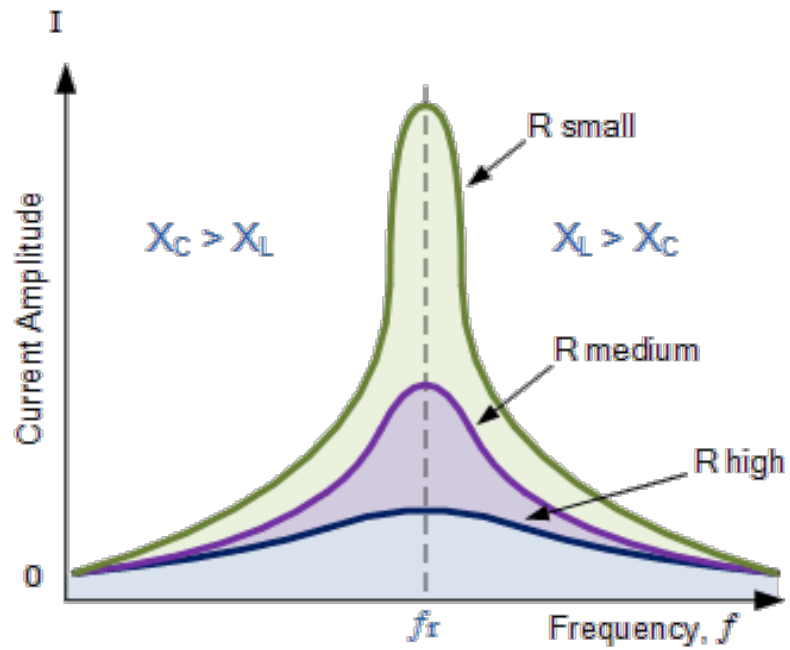

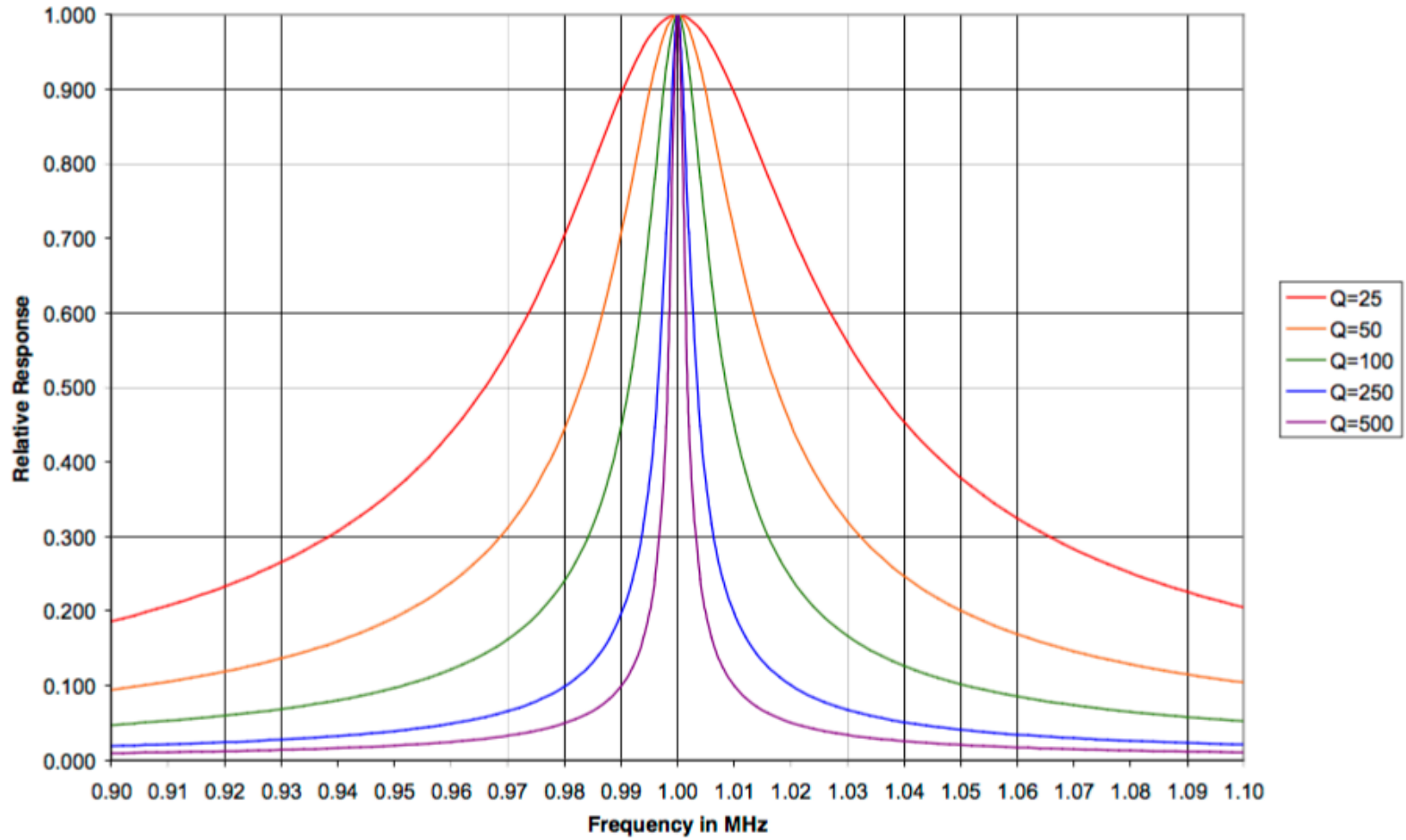

B-005-12-1 Resonance is the condition that exists when:

- 1. inductive reactance and capacitive reactance are equal**
- 2. inductive reactance is the only opposition in the circuit**
- 3. the circuit contains no resistance**
- 4. resistance is equal to the reactance**

B-005-12-7 In a series resonant circuit at resonance, the circuit has:

- 1. low impedance**
- 2. high impedance**
- 3. low mutual inductance**
- 4. high mutual inductance**

B-006-6-5 What happens when the impedance of an electrical load is equal to the internal impedance of the power source?

- 1. The electrical load is shorted**
- 2. The source delivers maximum power to the load**
- 3. No current can flow through the circuit**
- 4. The source delivers minimum power to the load**

Next time: Waves and Propagation

